

CE433 Quiz 2 (40 points)

1. What are the floating point representations of the following decimal numbers? (20 points)

(a) 5.25

(b) -8.5

(a) 5.25

$X = SEF$ \downarrow

$5.25 = 101.01 = 1.0101 \times 2^2$

$E = 15 + 2 = 17 = 10001$

$F = 0101000000$

$X = SEF = \frac{0}{0 \times 4} \frac{10001}{5} \frac{0101}{4} \frac{000000}{0}$

2. Design the gate-level schematic of an Odd Parity Bit Generator (data length is 2 bits). Write the Verilog code for this module. (20 points)



a	b	P
0	0	1
0	1	0
1	0	0
1	1	1


$$\rightarrow P = \bar{a}\bar{b} + ab = a \odot b$$

$$= \overline{a \oplus b}$$


verilog


$P = \sim(a \wedge b);$
assign

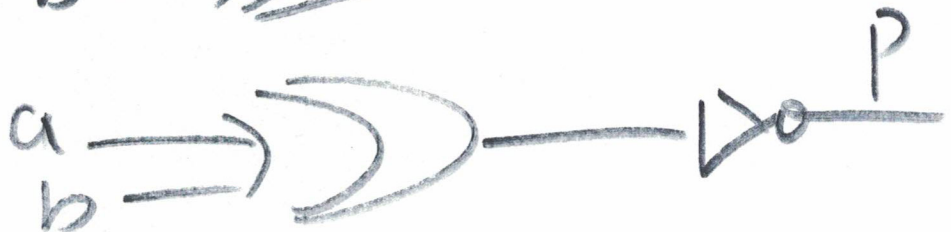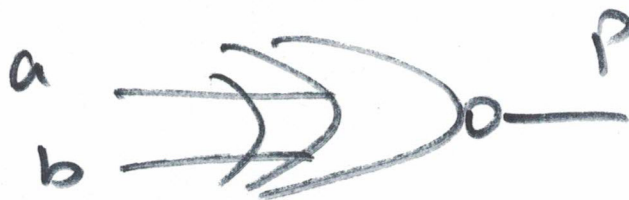

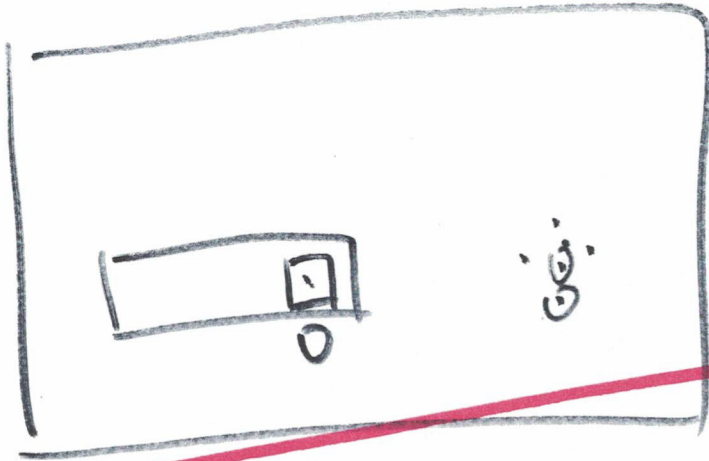

$if(state == 1)$

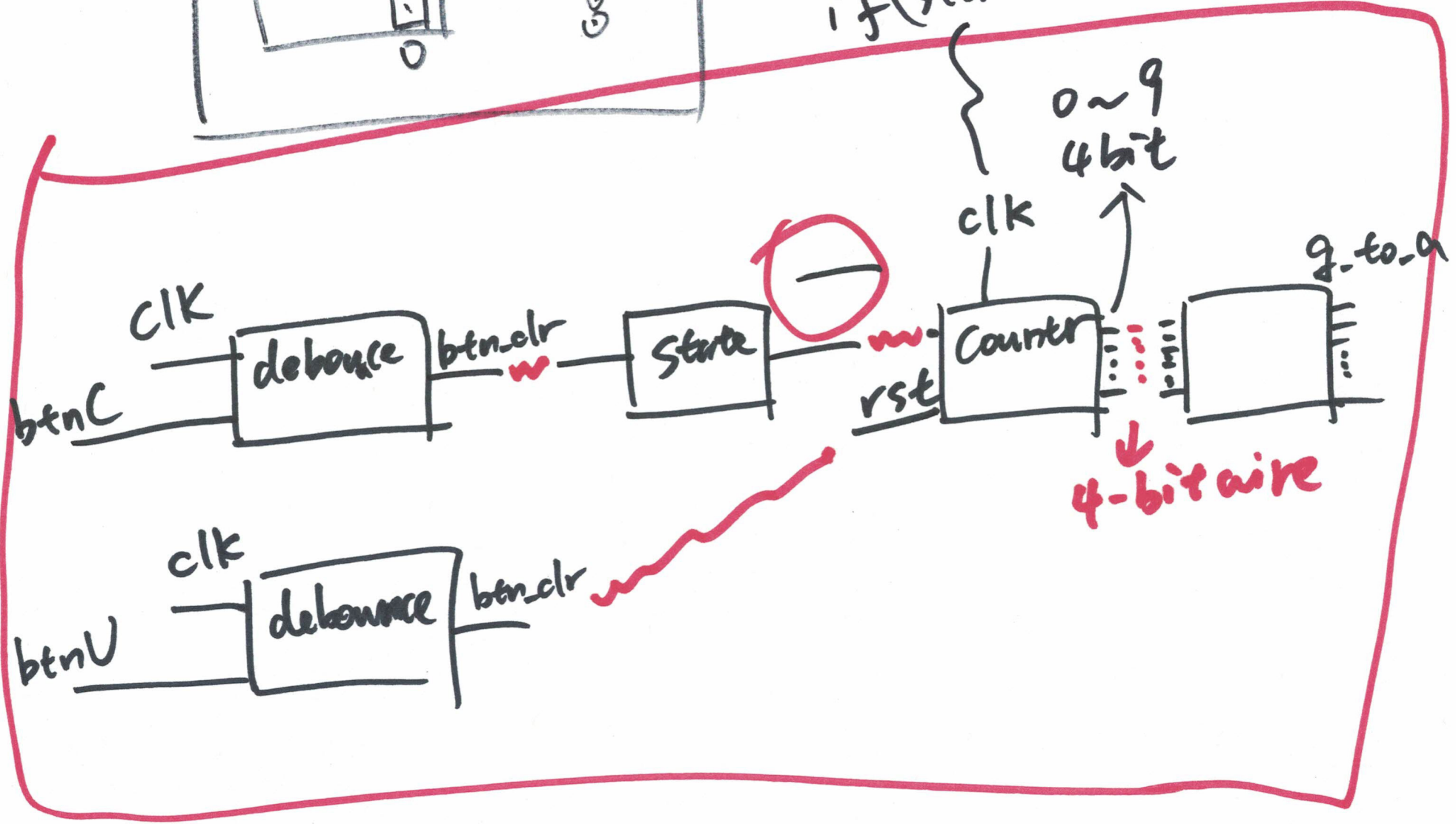

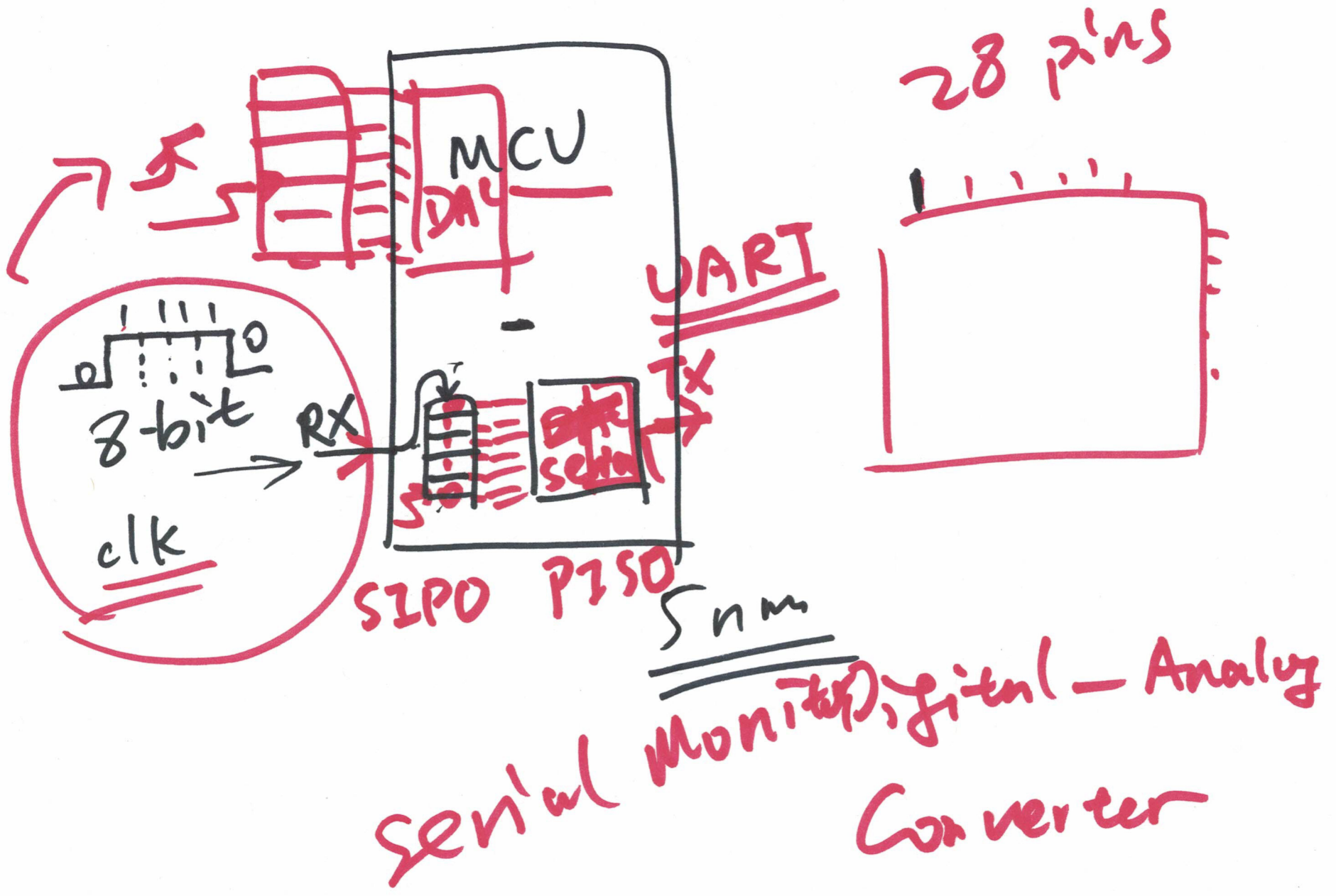

5nm

Serial Monitor, Digital - Analog Converter