

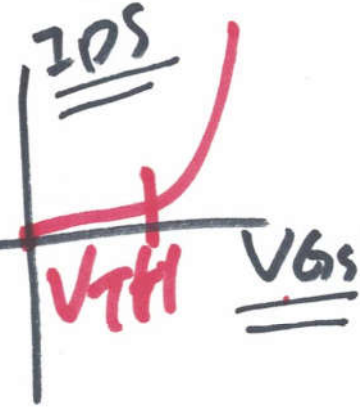
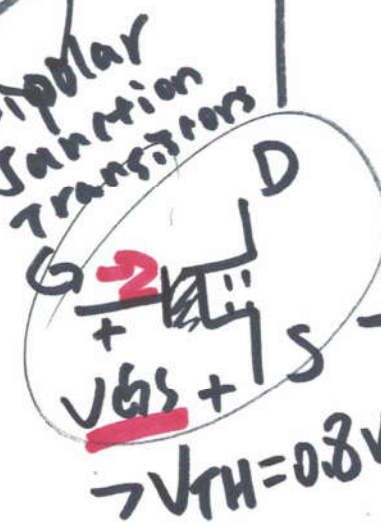
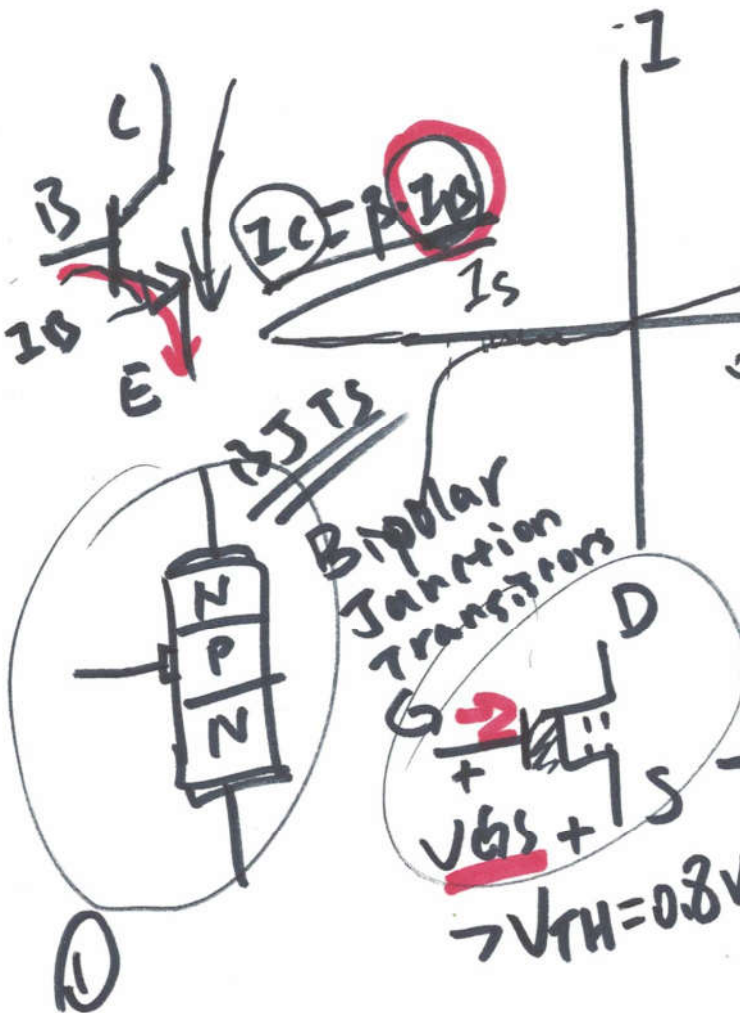
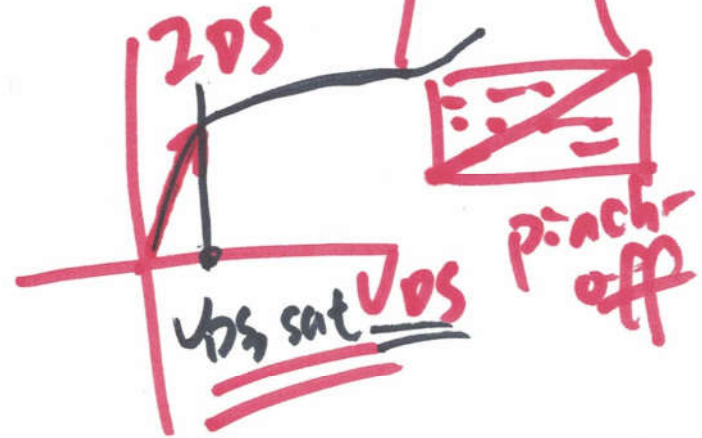




Zener diode

$V_{ZS} \text{ sat}$

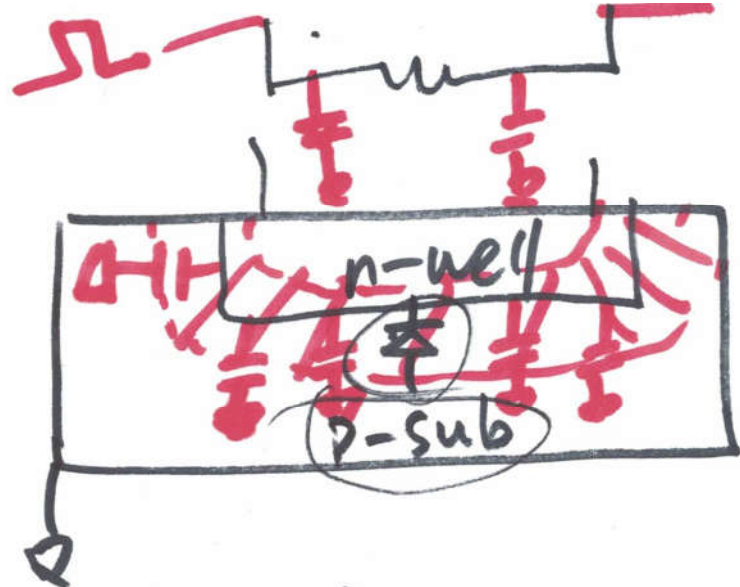

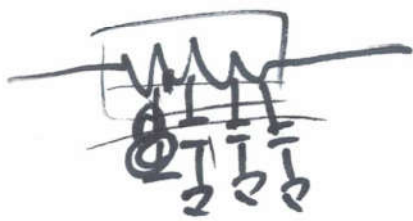

Distributed RC Delay

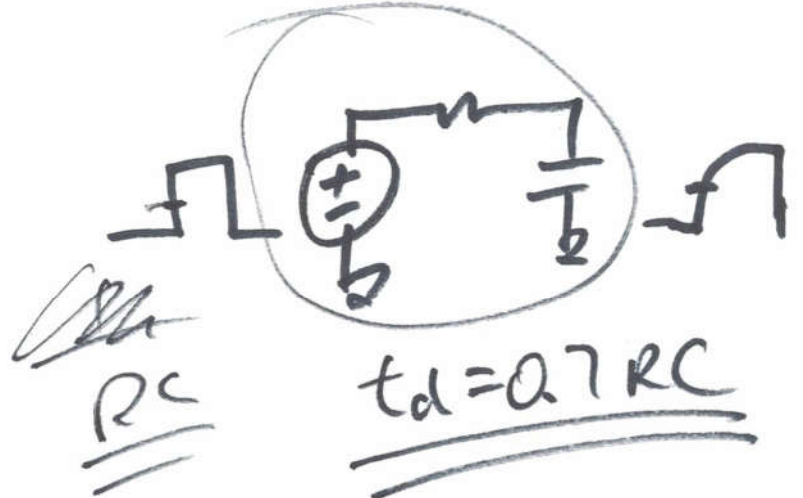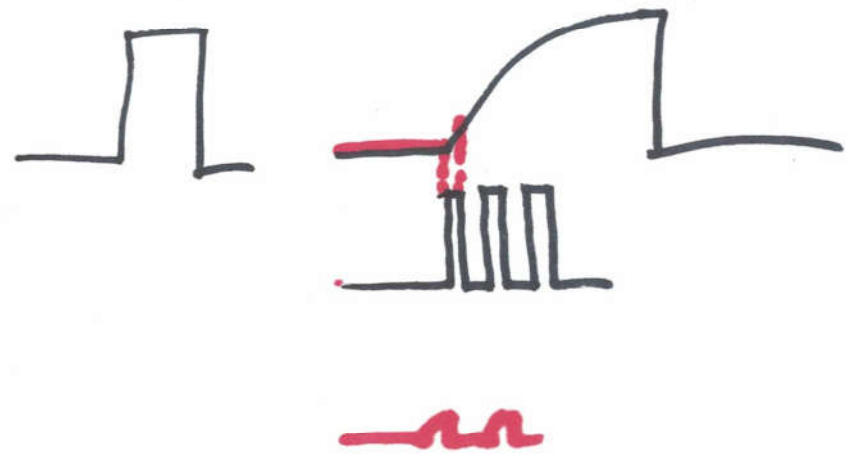



$t_d = 0.7RC$

$f = \frac{1}{2.2RC}$

$C = \epsilon \frac{A}{d}$


$A_0 = A_1 + A_2 + A_3$

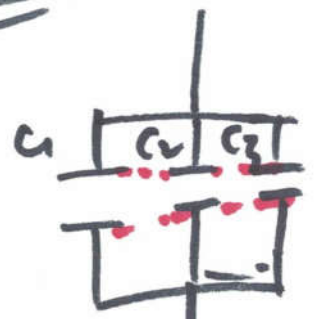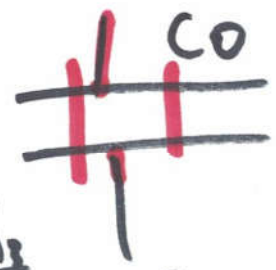$C_0 = C_1 + C_2 + C_3$   
 $= \epsilon \frac{A_1}{d} + \epsilon \frac{A_2}{d} + \epsilon \frac{A_3}{d}$




$C_0 = C_1 + C_2 + C_3$

2

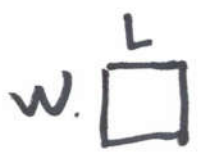

$$C = \epsilon \frac{A}{d}$$

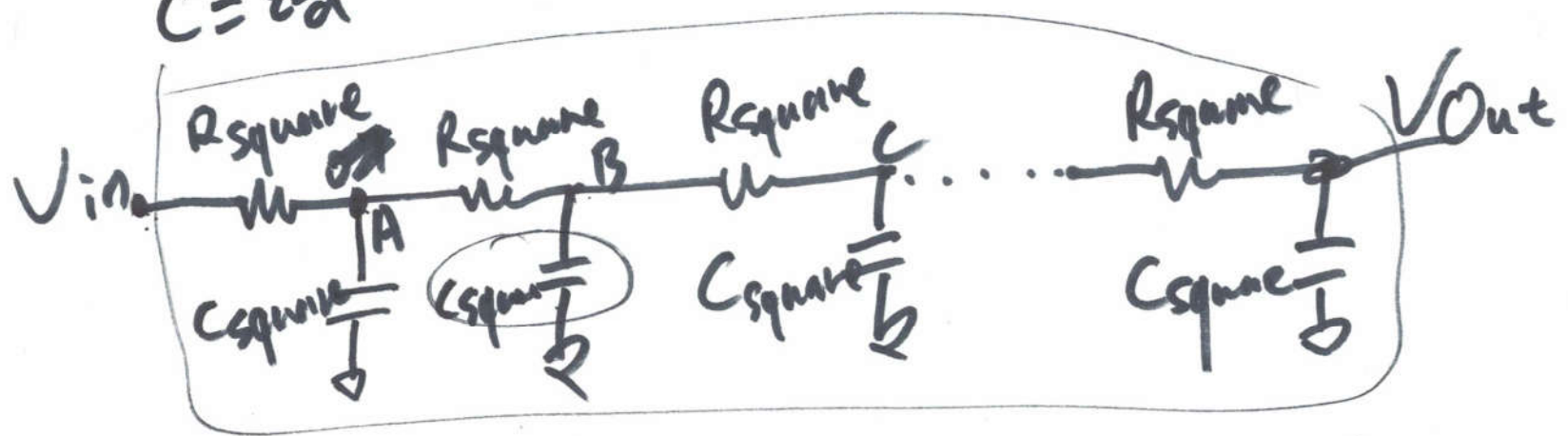

$$t_{dA} = 0.7 R_{square} C_{square}$$

$$t_{dB} = 0.7 \cdot 2 R_{square} \cdot C_{square}$$

$$t_{dC} = 0.7 \cdot 3 \cdot R_{square} \cdot C_{square}$$


⋮

$$t_{dout} = 0.7 \cdot l \cdot R_{square} \cdot C_{square}$$

$$t_d = t_{dA} + t_{dB} + t_{dC} + \dots + t_{dout}$$


$$= 0.7 R_{square} C_{square} (1 + 2 + 3 + \dots + l) = 0.7 R_{square} C_{square} \frac{l(l+1)}{2}$$

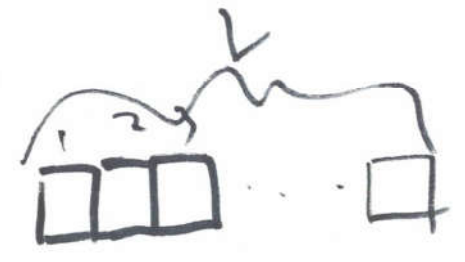$\frac{l(l+1)}{2}$   
 $\frac{l(l+1)}{2}$   
 $\frac{l(l+1)}{2}$



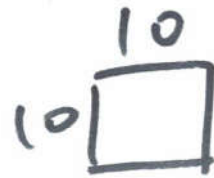(3)

$$t_d = 0.35 R_{\text{square}} C_{\text{square}} \quad \downarrow^2$$



Example.  
 Estimate the time delay through ~~250~~<sup>250</sup> k $\Omega$  resistor made using an n-well with a width of 10 and length of 500. Assume a 10x10 square of n-well has 5 fF of capacitance.

$$R_{\text{square}} = \frac{250 \text{ k}\Omega}{500/10} = 5 \text{ k}\Omega$$

Farad

$$t_d = 0.35 \times 5 \times 10^3 \Omega \times 5 \times 10^{-15} \text{ F} \times \frac{50^2}{10}$$

$$= 21.875 \text{ ns} = 21.875 \times 10^{-9} \text{ s}$$

MOSIS 2018

NMOS N-14

MUSE

\$6500

TSMC ~~170nm~~ mtf

→ CS

SUN  
Solaris 8

(5)