

ENGR338 Quiz 3

1. Draw the complex CMOS schematics and the stick diagrams of the following logic expressions.
(50 points for each)




a. $\overline{(AB + CD)E} + AB$

b. $\overline{AB} + \overline{CDE} + \overline{BC}$

$$= \overline{\underline{ABE} + \underline{CDE} + \underline{AB}}$$

$$= \overline{AB} \cdot (\overline{1+E}) + CDE$$

$$= \overline{AB} + CDE$$

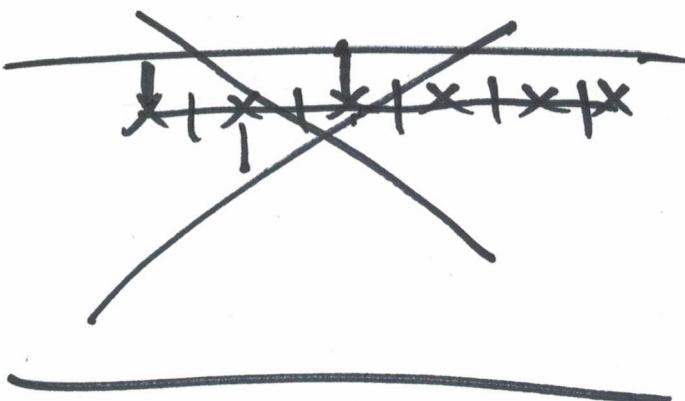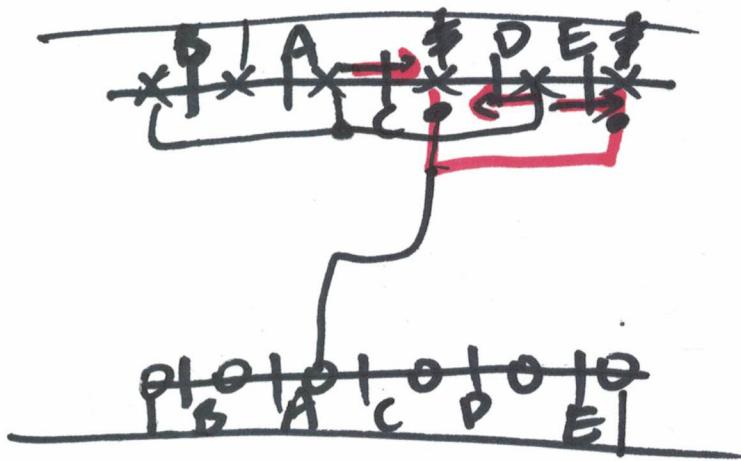
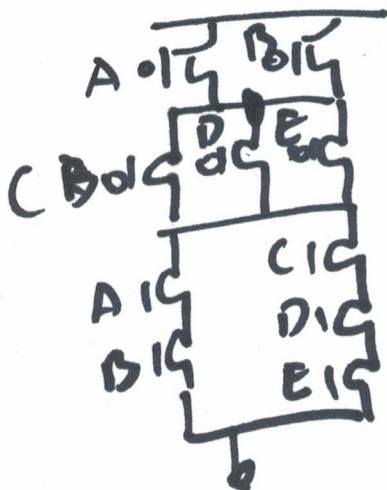


①

Quiz 3



1. b. $AB + cDE + BC$

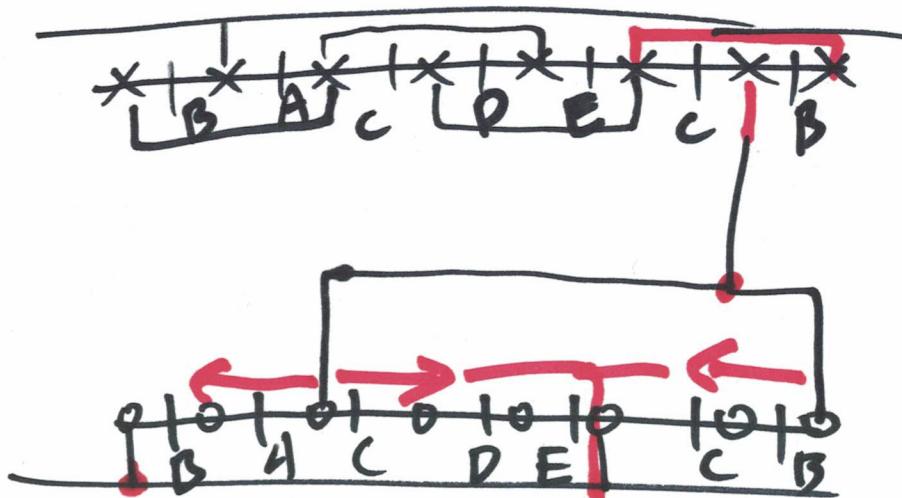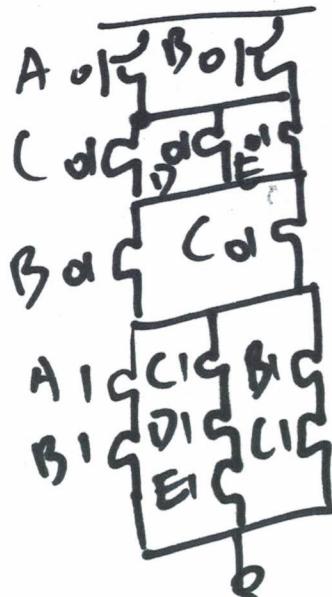

Static Logics Gates, AOIs, and Stick Diagrams

1. Convert the following logic expressions to CMOS AOI circuits and hand-draw the stick diagrams of the layouts. (100 points)

(a) $G = \bar{A}$

(b) $G = \overline{(A \cdot B)}$

(c) $G = \overline{(A + B)}$

(d) $G = A \cdot B$



(e) $G = \overline{(A + B) \cdot (C + D) \cdot E}$

(f) $G = \overline{(A \cdot B) + (C \cdot D)}$

(g) $G = \overline{(A \cdot B + C)} \cdot \bar{D}$

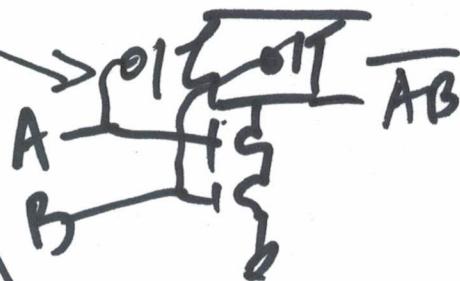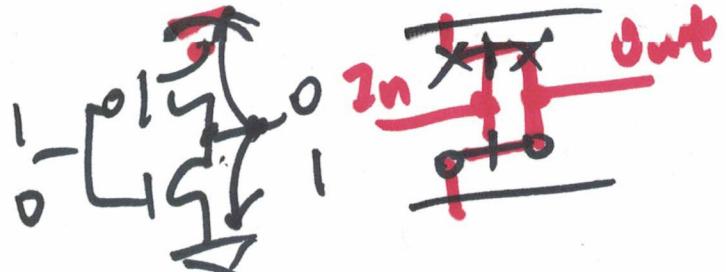(h) $G = \overline{(\bar{A} \cdot B)} + A \cdot B$

$$\rightarrow AB = \overline{\overline{AB}} \\ = \overline{\overline{A} + \overline{B}}$$







NOR

$AB \neq \overline{A+B}$
demorgan's law

$\overline{AB} = \overline{A} + \overline{B}$
$\overline{A+B} = \overline{A} \cdot \overline{B}$





(e) $(A+B) \cdot (C+D) \cdot E$

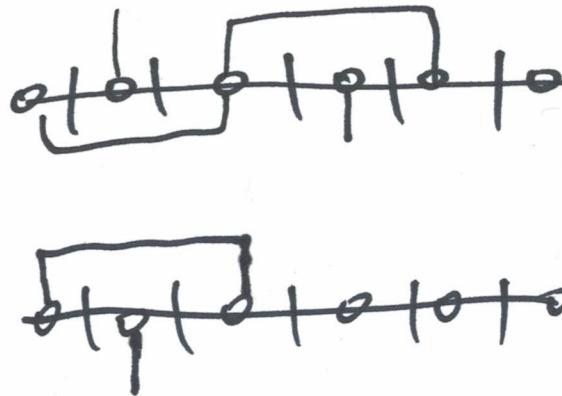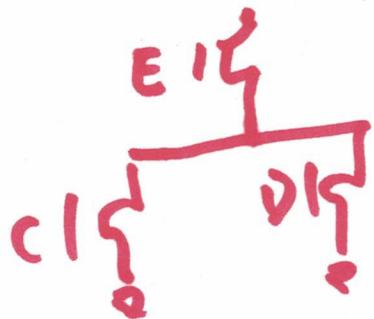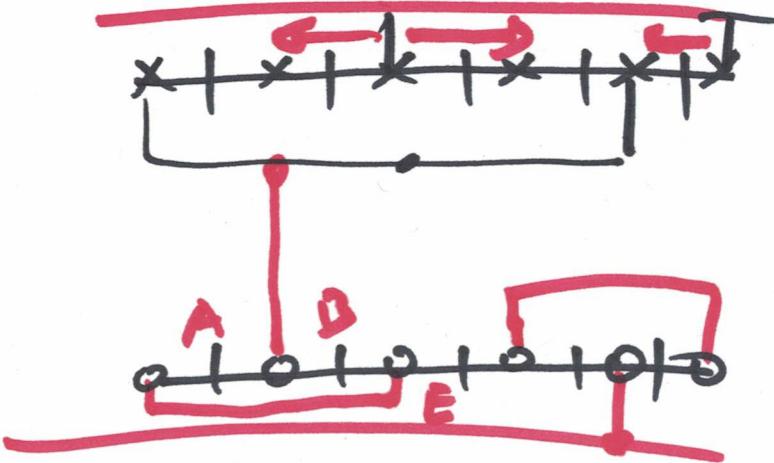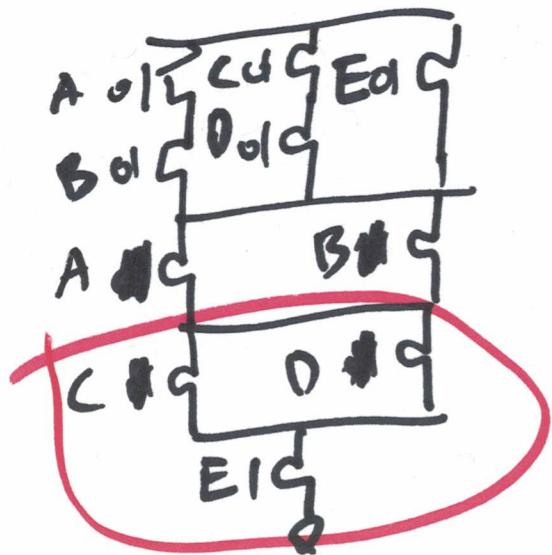


$$(f) G = \overline{AB + CD}$$
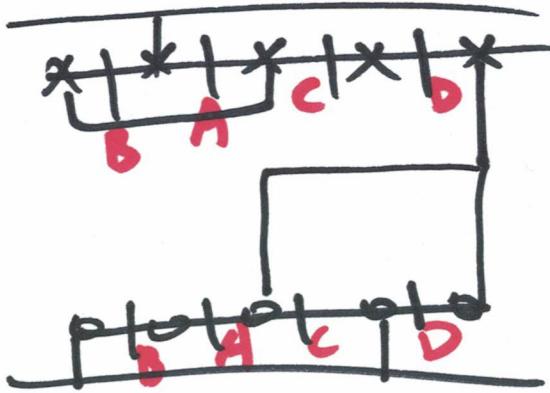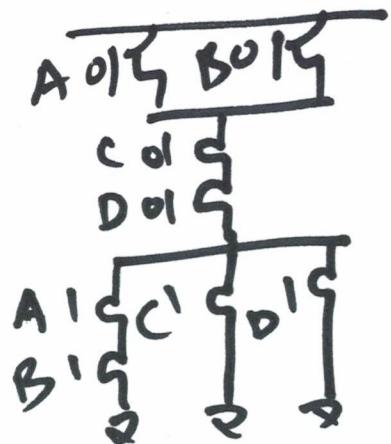
$$(g) G = \overline{\overline{AB + C} \cdot \overline{D}}$$
$$= \overline{AB + C + D}$$




$$(h) G = \overline{AB} + AB = 1$$


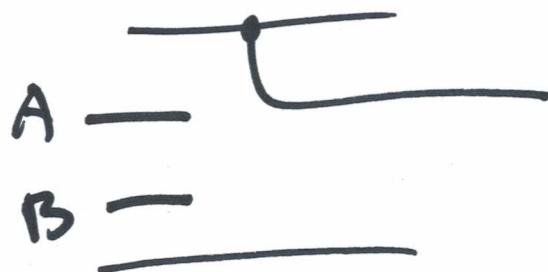


5

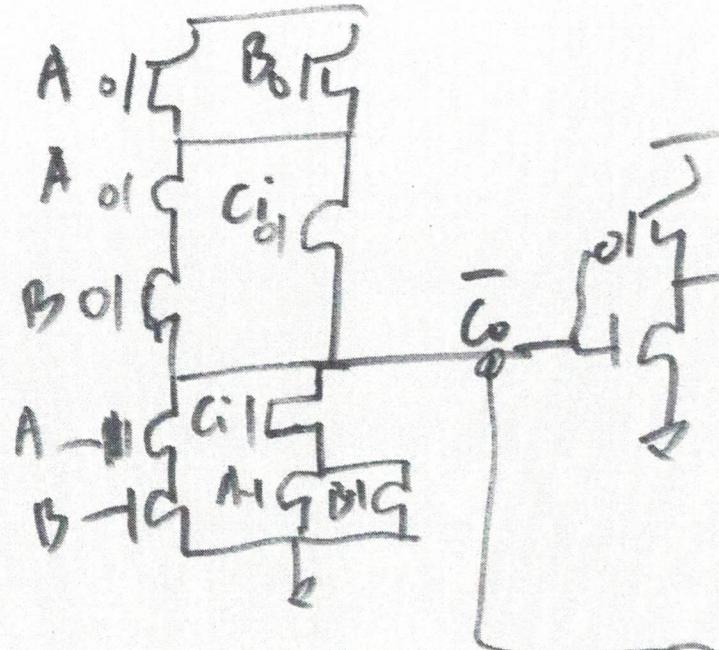
- ③ ① FreeRTOS ↴
- ② ② FPGAs (ASIC) ↴
- ① ③ Algorithms — LeedCode



$$Co = (A+B)C_i + AB$$

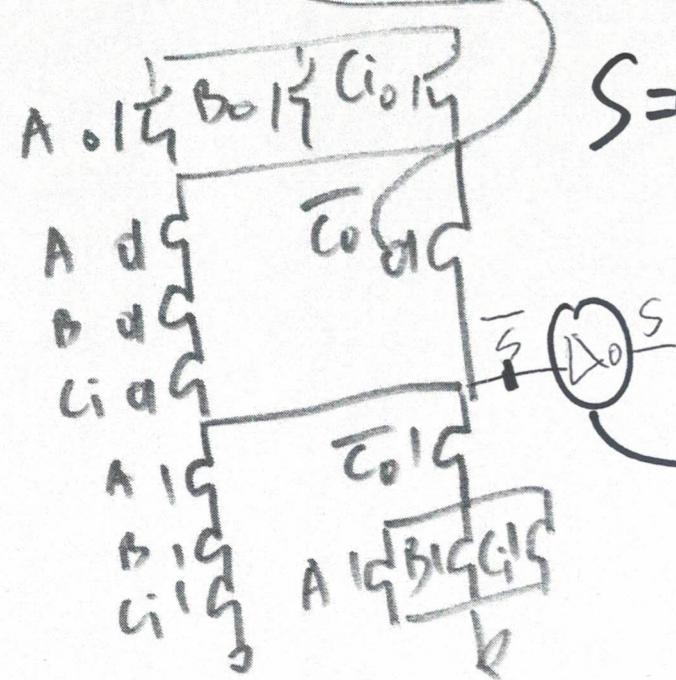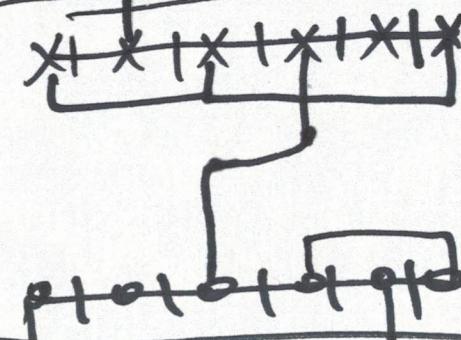

$$S = (A+B+C_i)\bar{C}_o + ABC$$

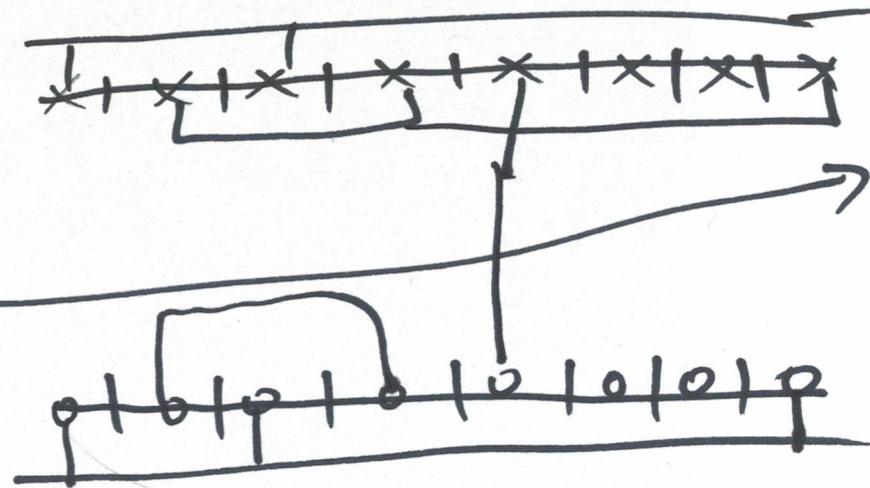

(4)