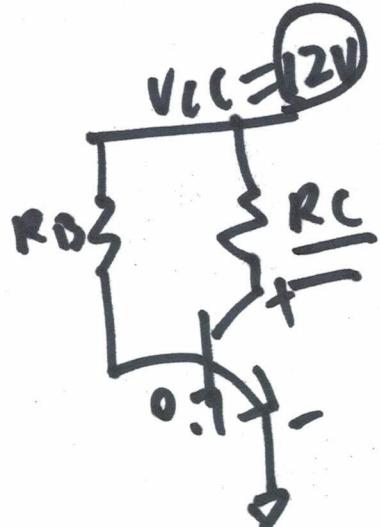


$\beta = 10^2$

Example: Determine whether the transistor is biased in cutoff, saturation, or linear region

(a) $R_B = 75\text{ k}\Omega$, $R_C = 1\text{ k}\Omega$





$$I_{CSAT} = \frac{12 - ?}{R_C}$$

$$= \frac{12}{1\text{ k}\Omega} = 12\text{ mA}$$

$$I_{CBQ} = \frac{12 - 0.7}{R_B} \cdot \beta$$

$$= 15\text{ mA} > I_{CSAT}$$

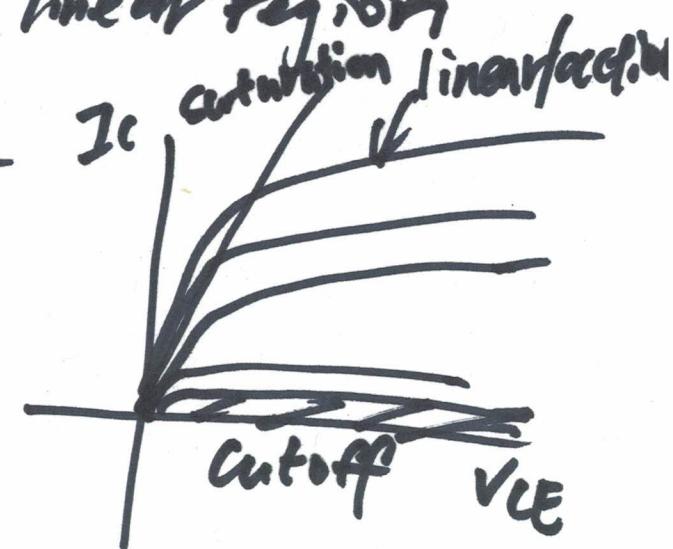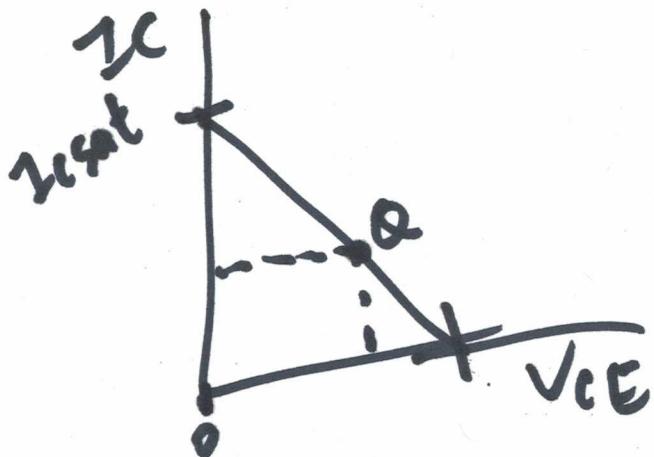

Impossible.
So it is operated in the saturation
region



Δ When $R_B = 150\text{ k}\Omega$, $R_C = 1\text{ k}\Omega$

$V_{out} = V_{in} \cdot \frac{R_2 || R_L}{R_1 + R_2 + R_L}$

$I = V_{in} \cdot \frac{R_2 || R_L}{R_1 + R_2 + R_L}$

$I_{CSAT} = \frac{12 - 0}{1\text{ k}\Omega} = 12\text{ mA}$

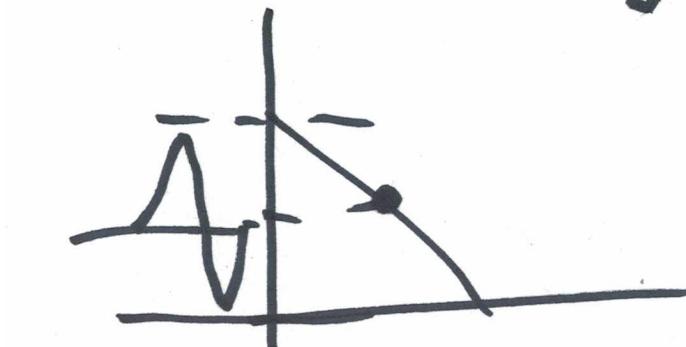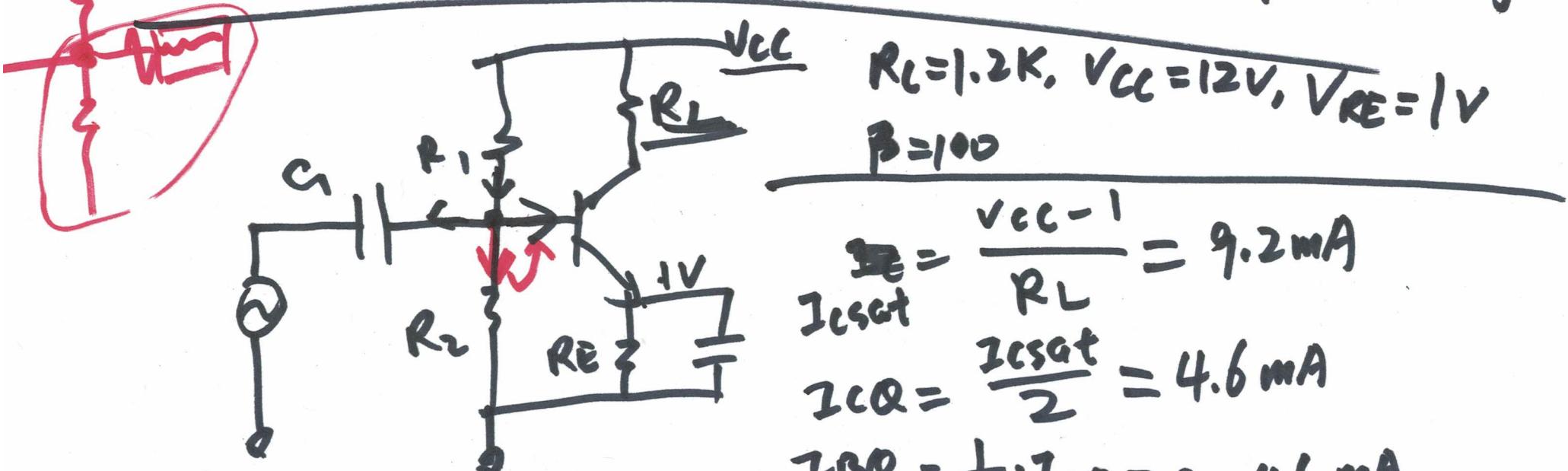$I_C = \beta \cdot \frac{12 - 0.7}{150\text{ k}\Omega} = 7.5\text{ mA} < 2\text{ mA} \Rightarrow \text{linear region/active region}$



②

$I_{R2} = 10 I_{BQ} = 460\text{ }\mu\text{A}$

$I_{R1} = I_{R2} + I_{BQ} = 506\text{ }\mu\text{A}$

$V_B = 0.7\text{ V} + 1\text{ V} = 1.7\text{ V}$

$$R_{R1} = \frac{V_{CC} - V_B}{I_{R1}} = \frac{12 - 1.7V}{506mA} = 20.45k\Omega$$

$$R_2 = \frac{V_B}{I_{R2}} = \frac{1.7V}{460mA} = 1.2k\Omega$$

$$R_E = \frac{1V}{I_C + I_B} = \frac{1V}{46mA + 4.6mA} = 216\Omega$$


BJTs

current controlled current source




Cmos

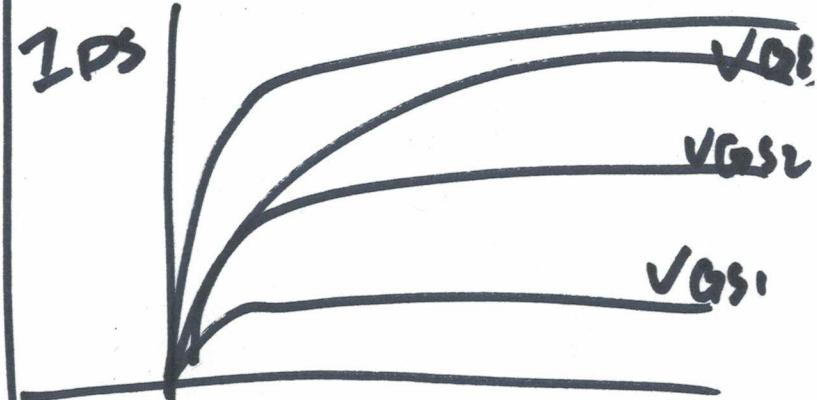voltage controlled
voltage
current source




$$I_{DS} = \frac{k_p}{2} \frac{W}{L} (V_{GS} - V_{TH})^2$$

Latch-up

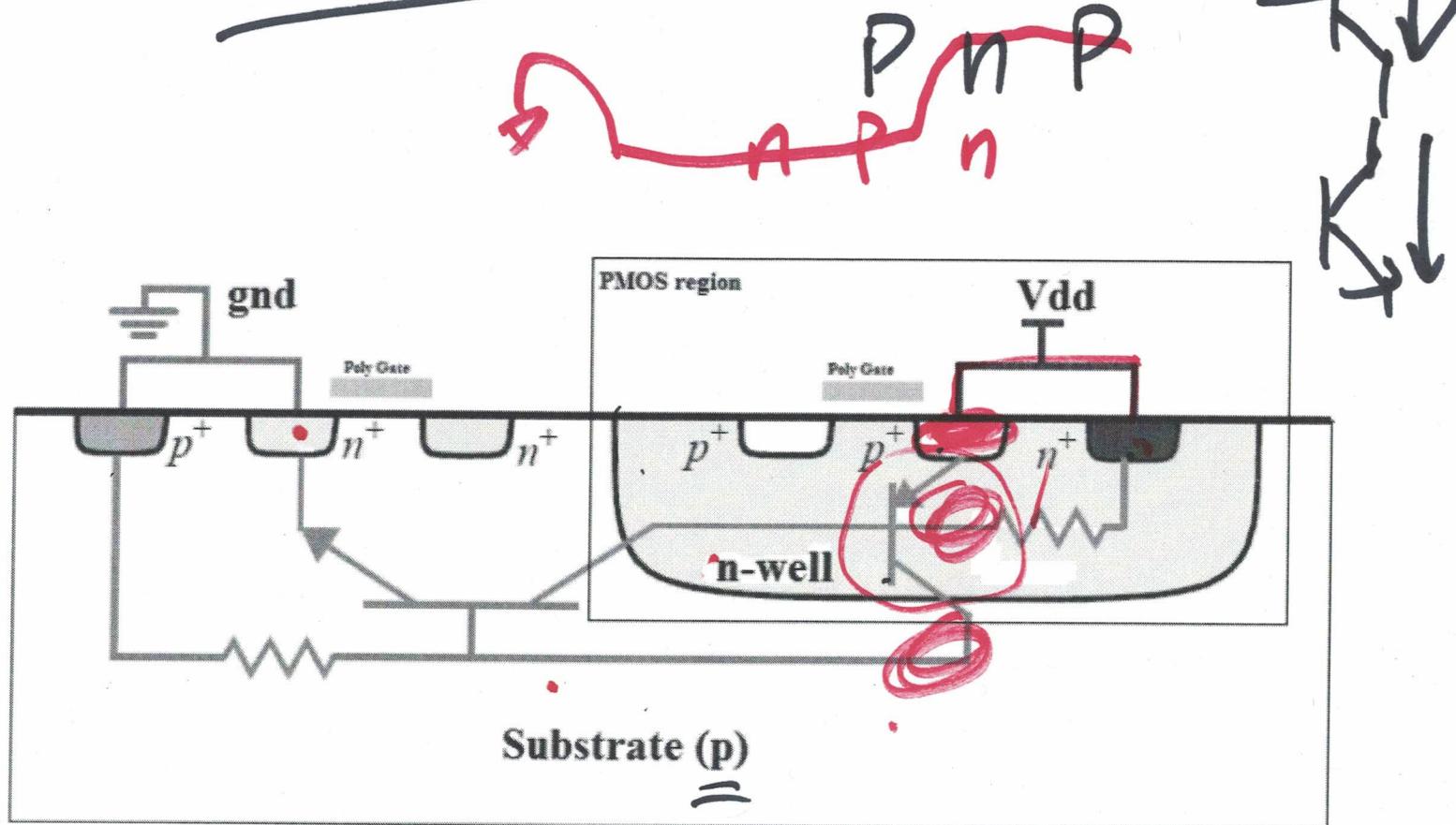


Shallow Trench Isolation Technology

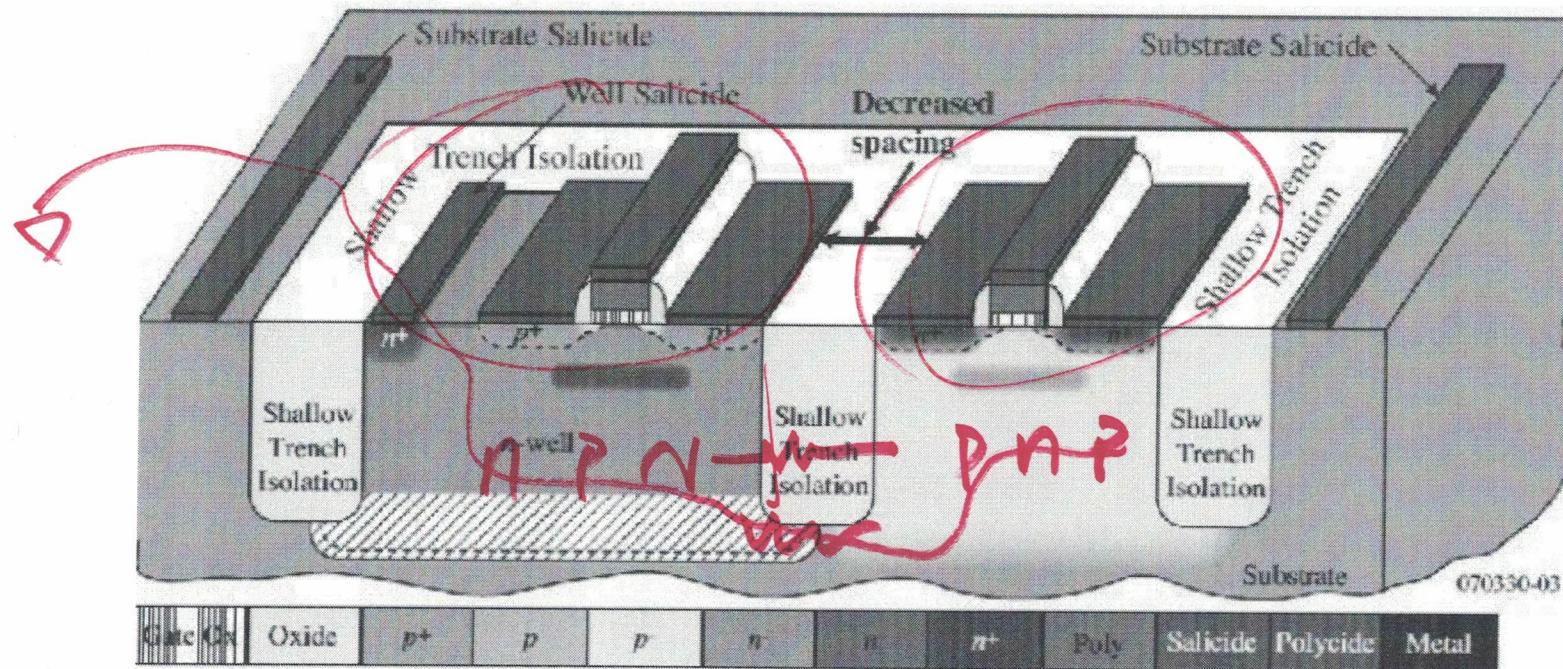- Allowing transistors to be spaced closer






Pinch-off

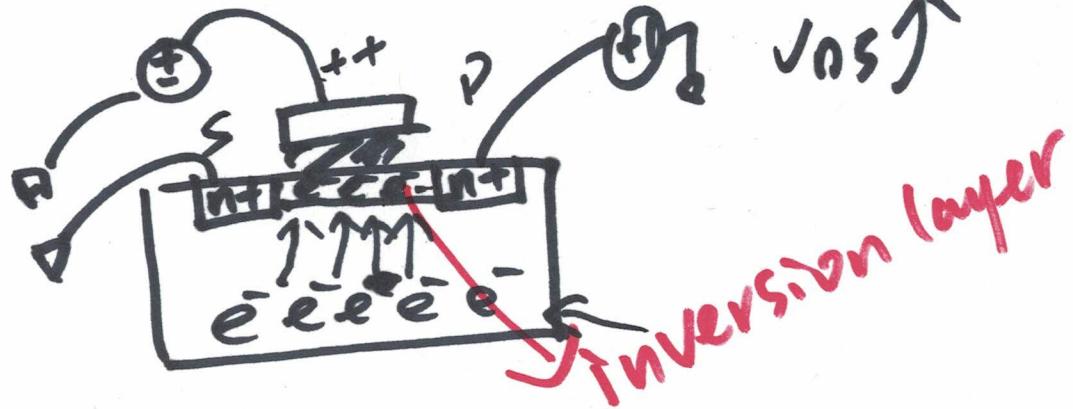

$$\sqrt{V_{GS} - V_{THN}} = V_{DS, \text{sat}}$$

pinch-off

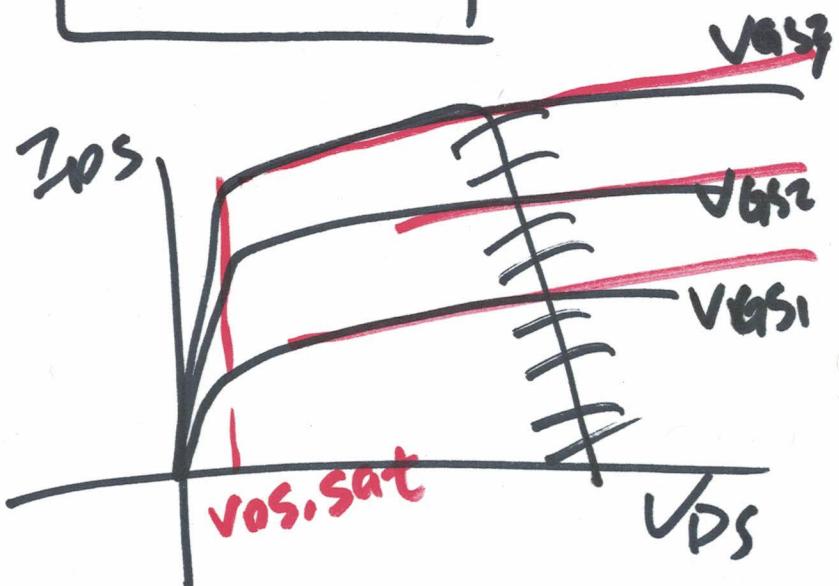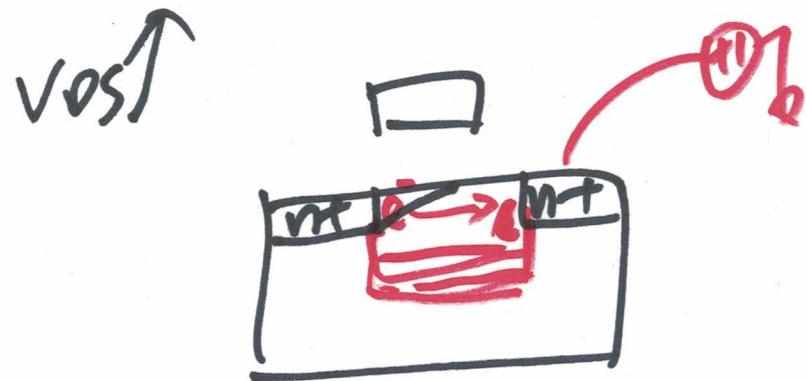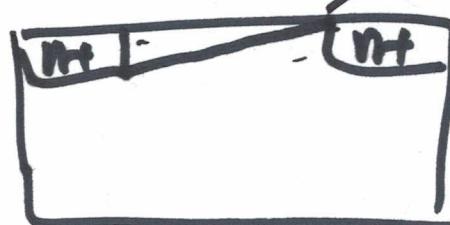

channel-length Modulation

CLM

more significant for smaller technologies



500nm 2nm

Body Effect

