
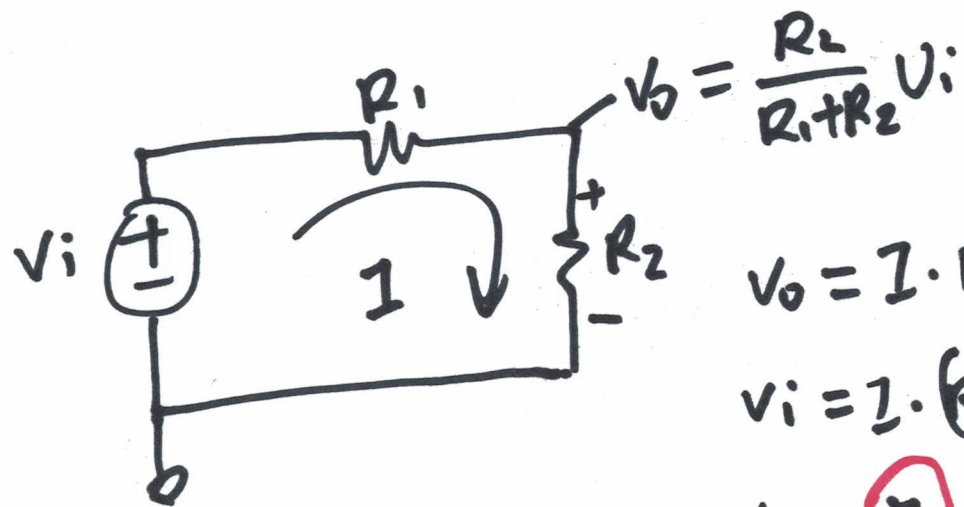


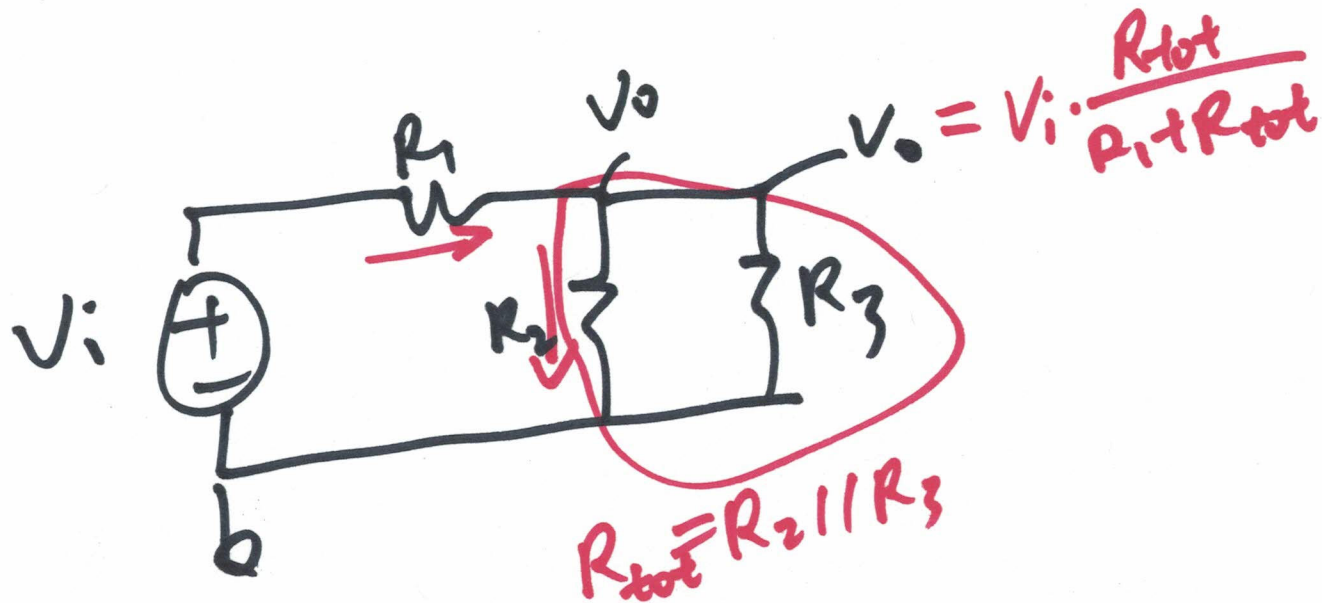


$$\frac{V_o}{V_i} = \frac{I \cdot R_2}{I \cdot (R_1 + R_2)}$$

$$V_o = V_i \cdot \frac{R_2}{R_1 + R_2}$$




①

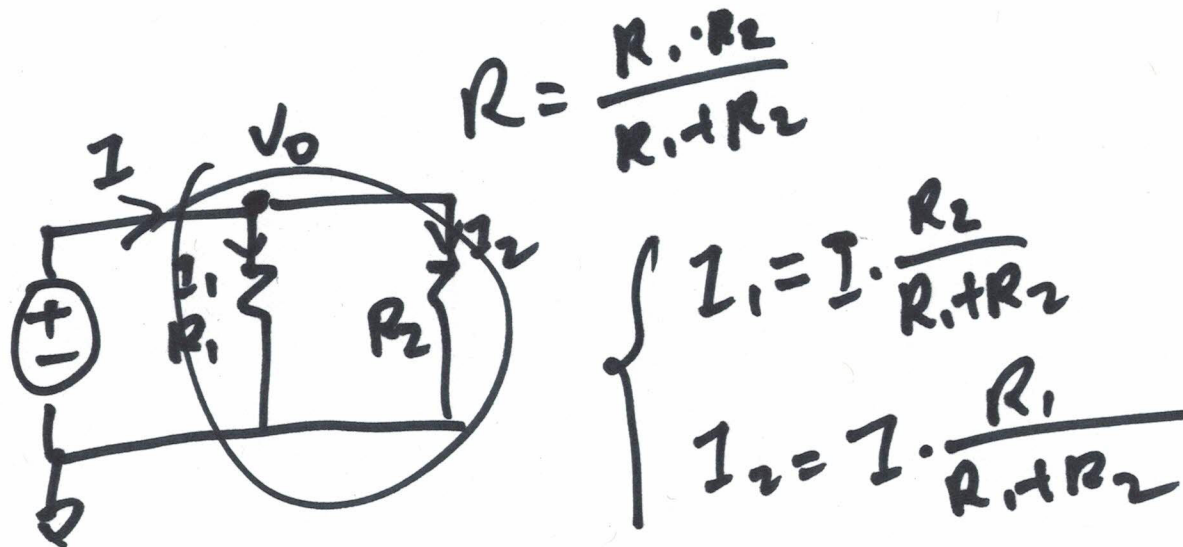

$$I \cdot R = I_1 \cdot R_1$$

$$I \cdot \frac{R_1 \cdot R_2}{R_1 + R_2} = I_1 \cdot R_1$$
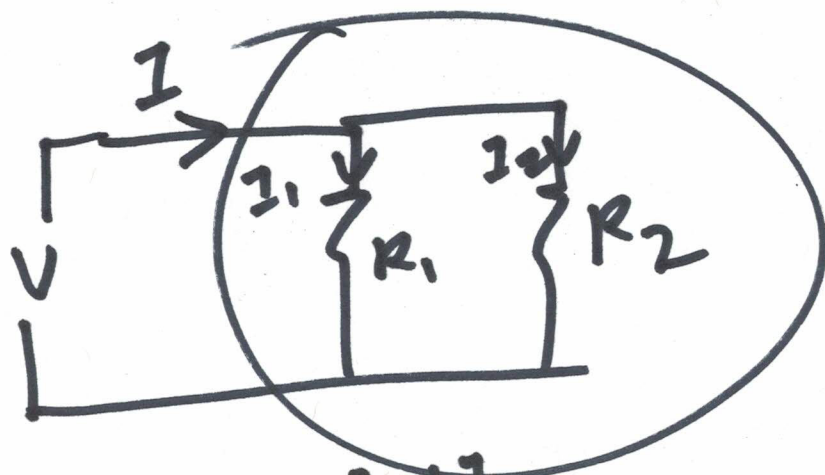
$$I \cdot \frac{R_1 \cdot R_2}{R_1 + R_2} = I_2 \cdot R_2$$



$$R = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$I = I_1 + I_2$$

$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2}$$





$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$




$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$= \frac{R_1 \cdot R_2}{R_1 + R_2}$$

(3)

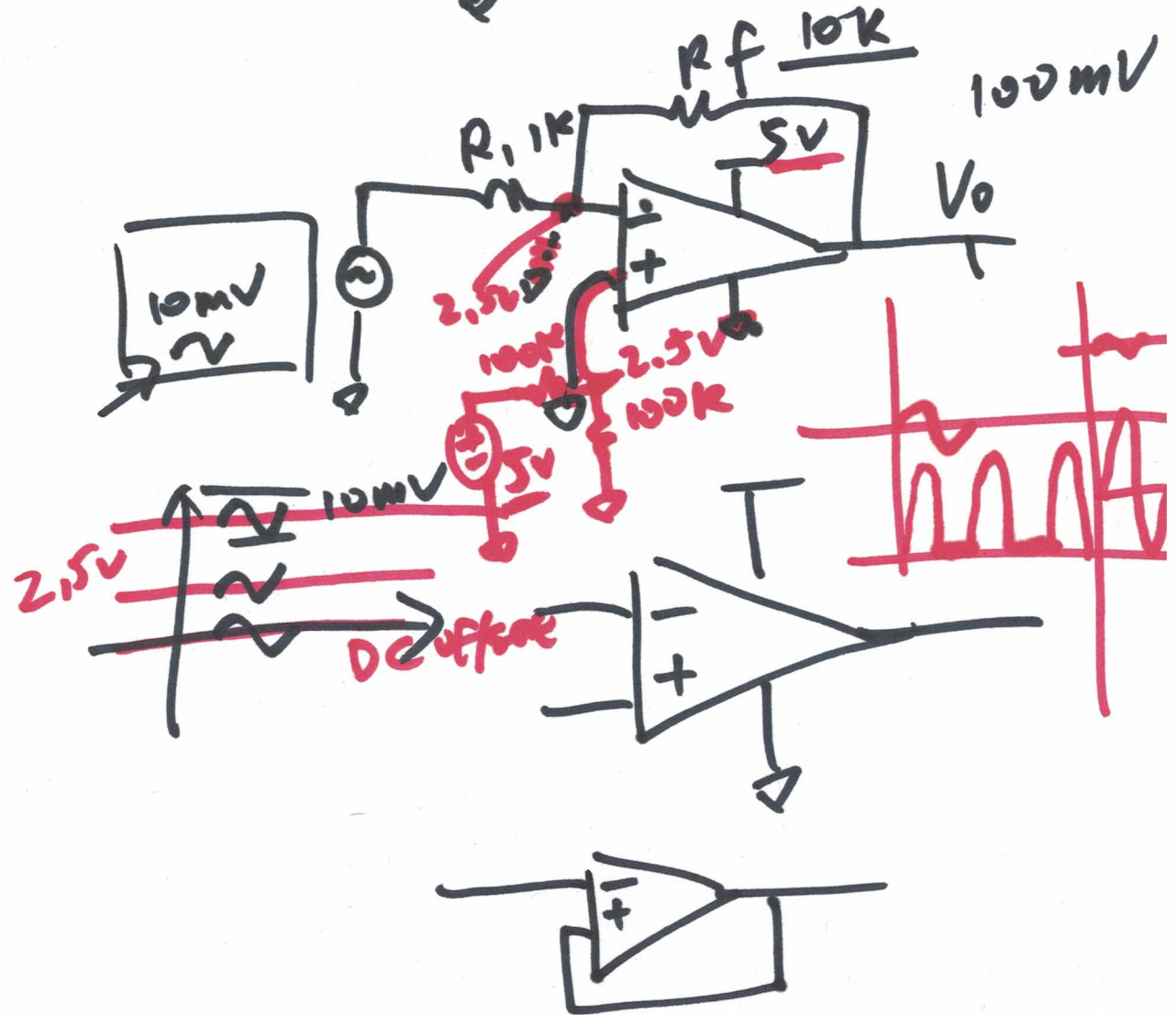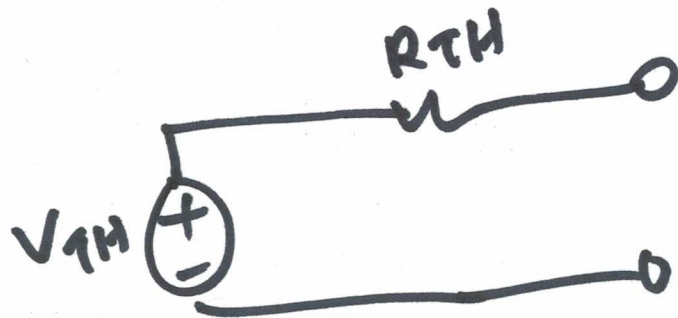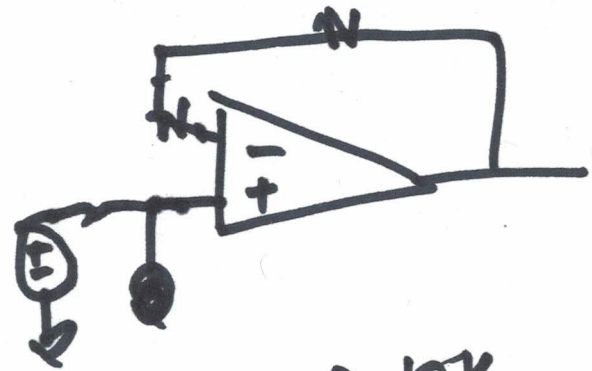
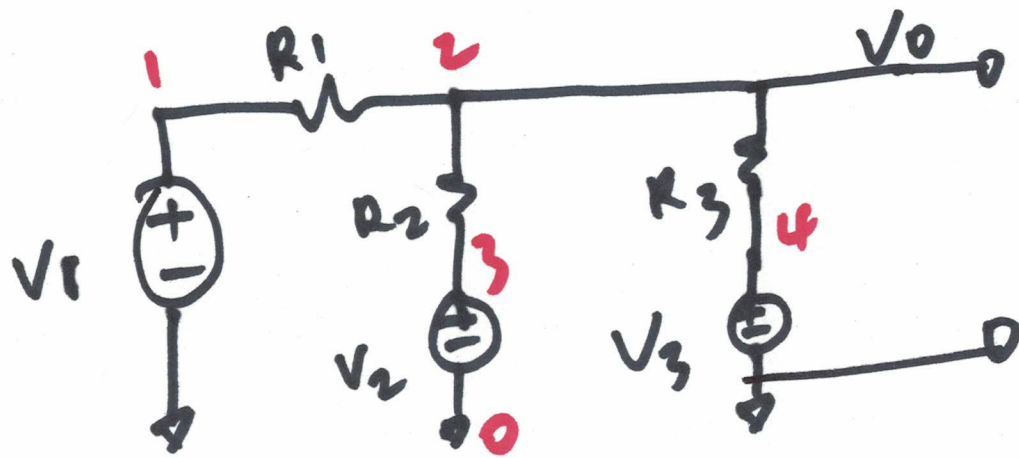


(4)

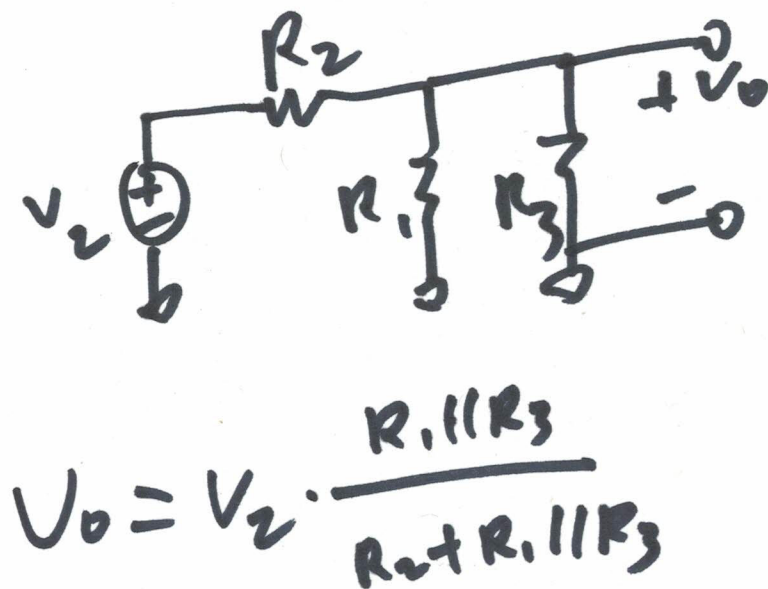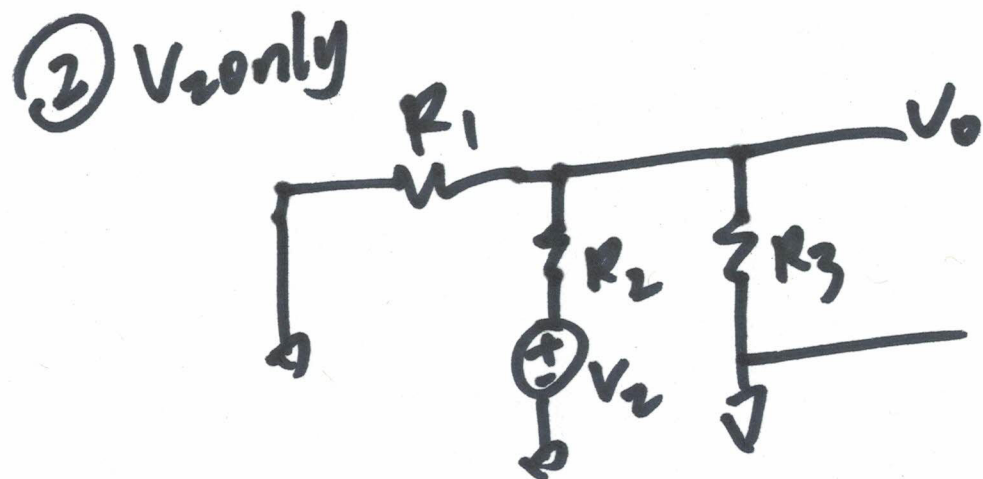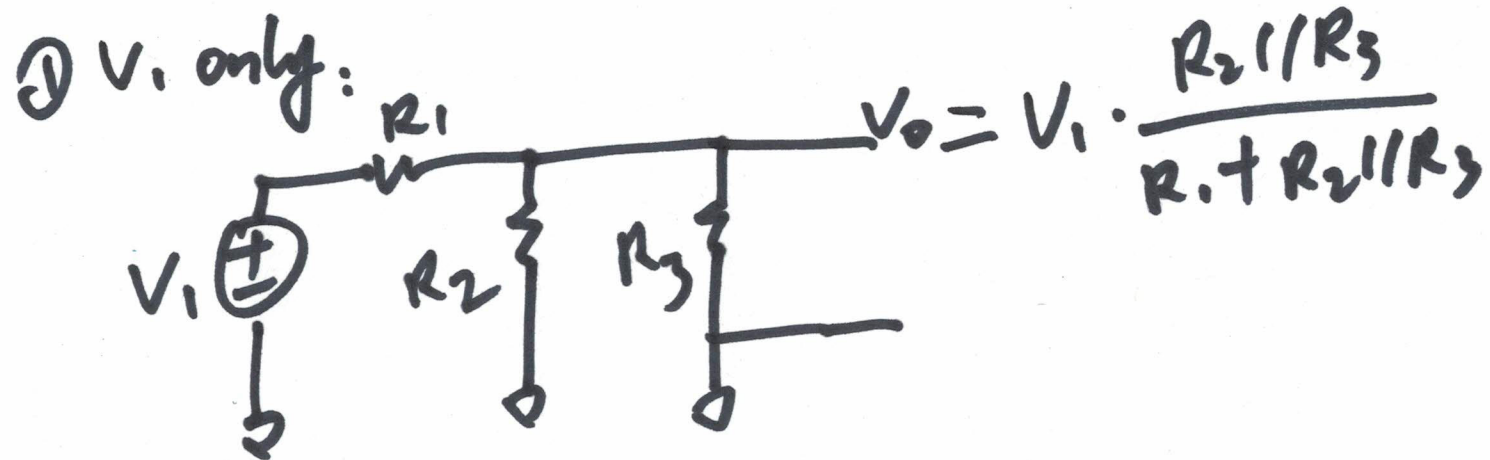

③

③ V_3 only

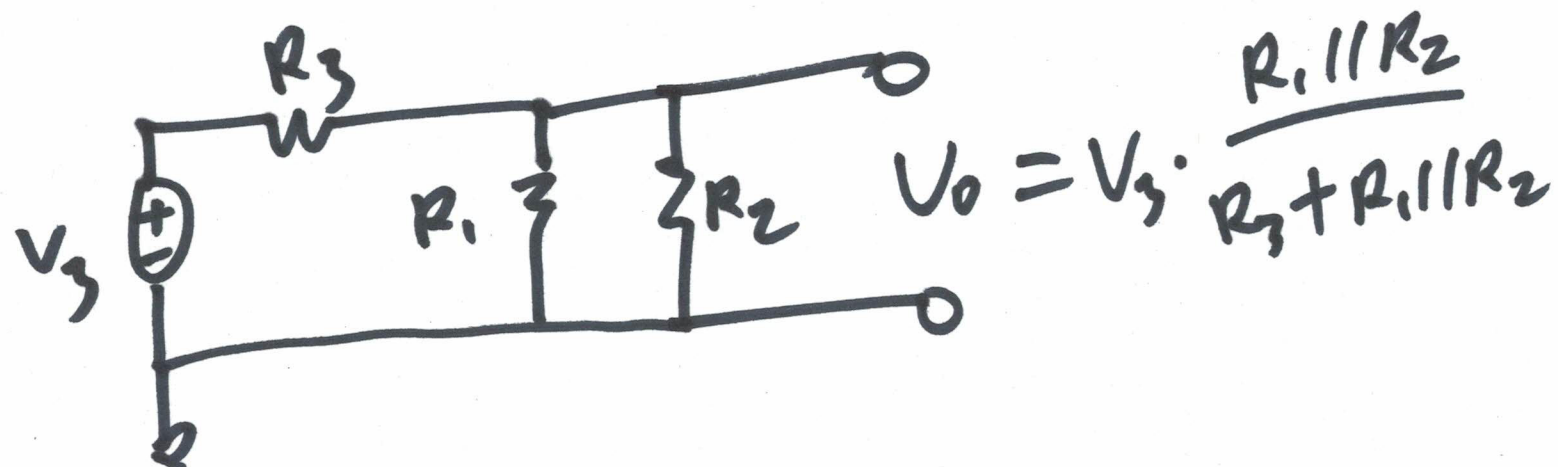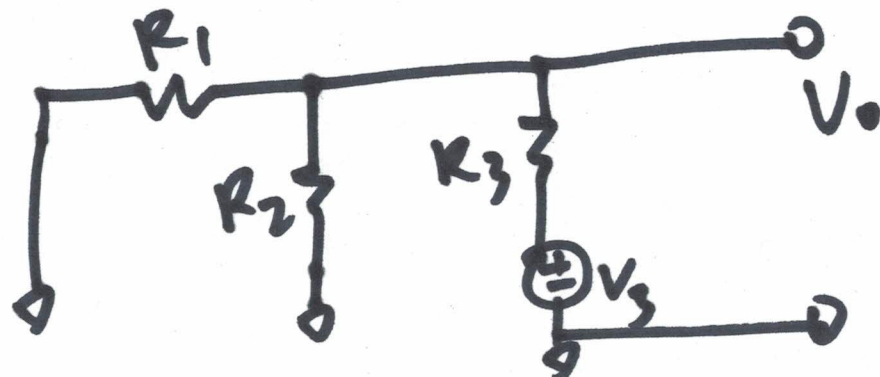

$$V_0 = V_1 \cdot \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} + V_2 \cdot \frac{R_1 \parallel R_3}{R_2 + R_1 \parallel R_3} + V_3 \cdot \frac{R_1 \parallel R_2}{R_3 + R_1 \parallel R_2}$$


$$R_1 = 2k \quad R_2 = 4k \quad R_3 = 6k \quad V_1 = 2V \quad V_2 = 4V \quad V_3 = 6V$$

④


$$V_0 = 3.27 \text{ V.}$$

Digital to Analog Converter (DAC)

① Block Diagram

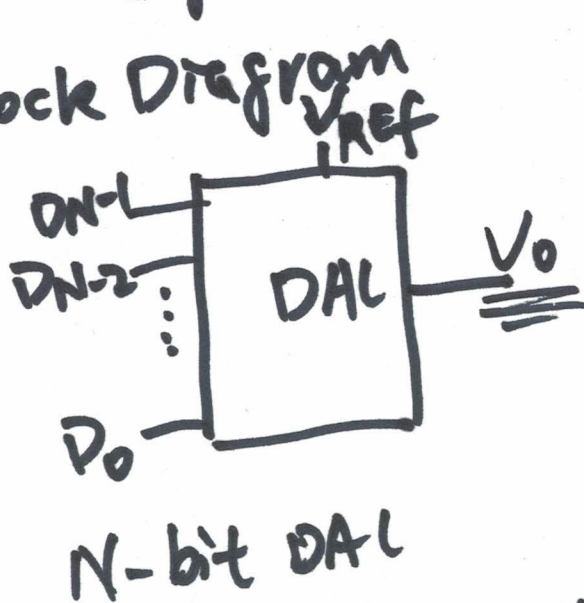
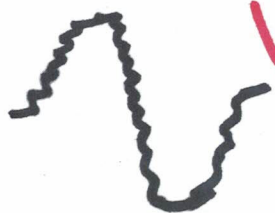
$$V_{FS} = \frac{2^N - 1}{2^N} \cdot V_{REF}$$



② N-bit DAC $\rightarrow 2^N$ input combinations

$$F = \frac{D}{2^N} \quad V_0 = V_{REF} \cdot \frac{D}{2^N} \quad (D \text{ is the input word})$$

③ 3-bit DAC, input is 100 (2), $V_{REF} = 5 \text{ V}$

$$F = \frac{100(2)}{2^3} \cdot 5 \text{ V} = \frac{4}{8} \cdot 5 \text{ V} = 2.5 \text{ V.}$$

①