

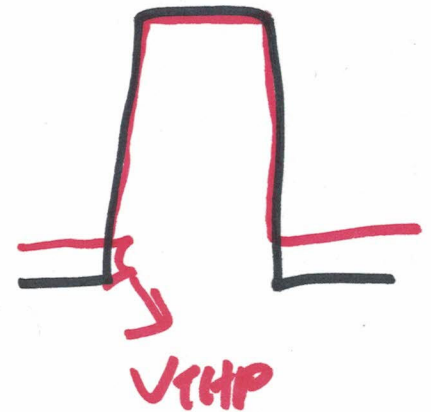
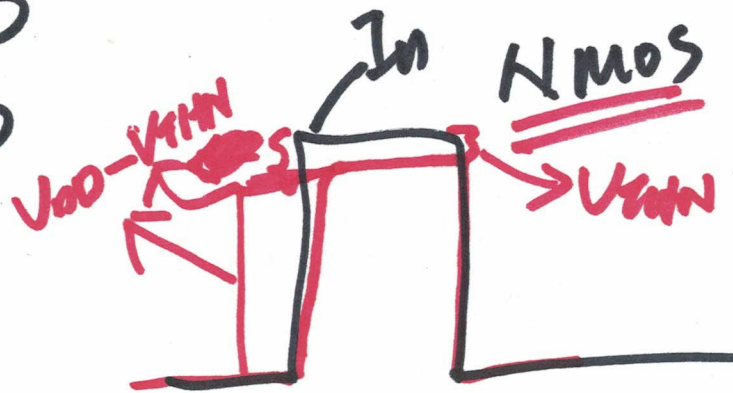
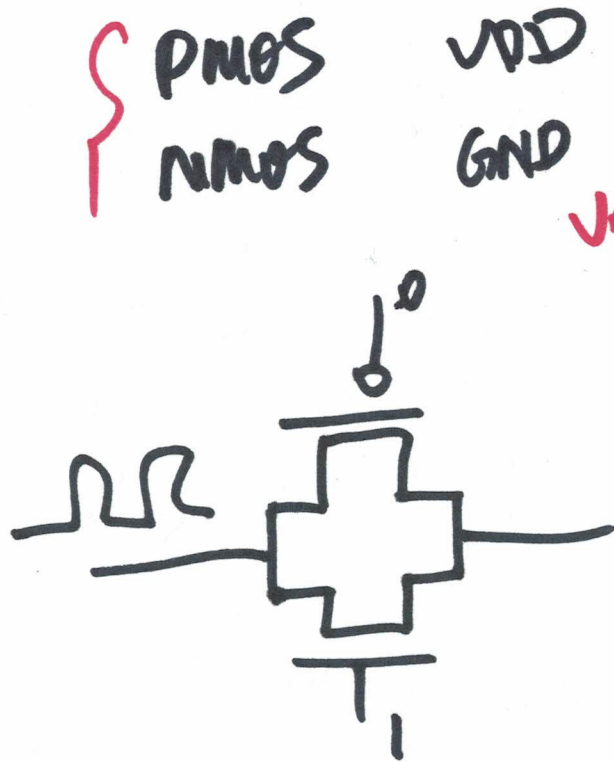

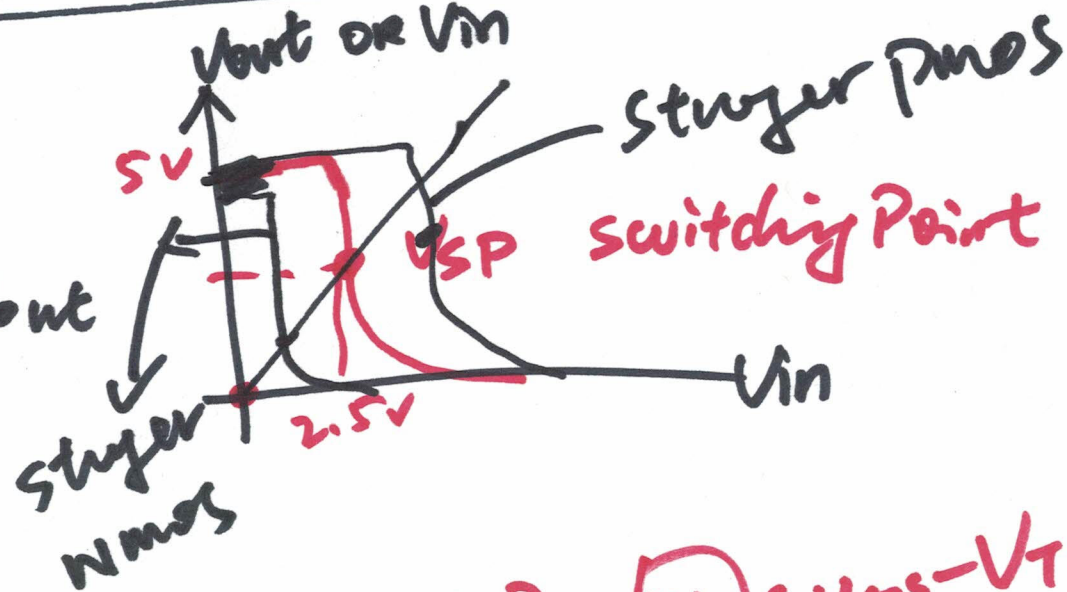
# (TG) Transmission Gates / Pass Gates (PG)




# The Inverter Switching Point

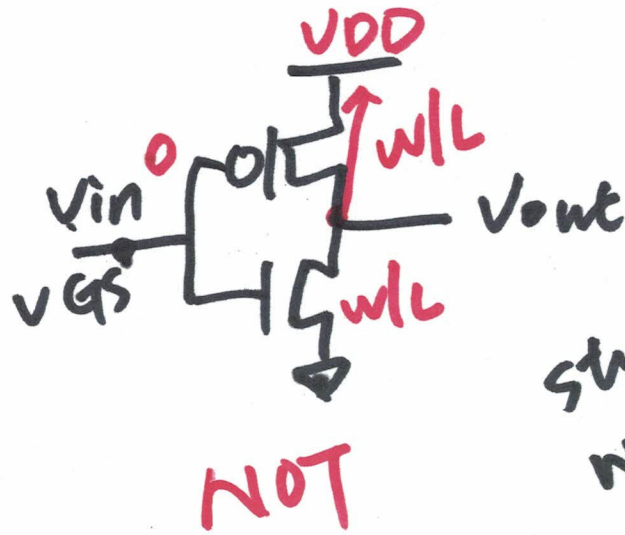

$$I_{DS} = \frac{K_{PMOS}}{2} \left( \frac{W}{L} \right) (V_{GS} - V_{THM})^2$$

larger  $W/L$ , stronger

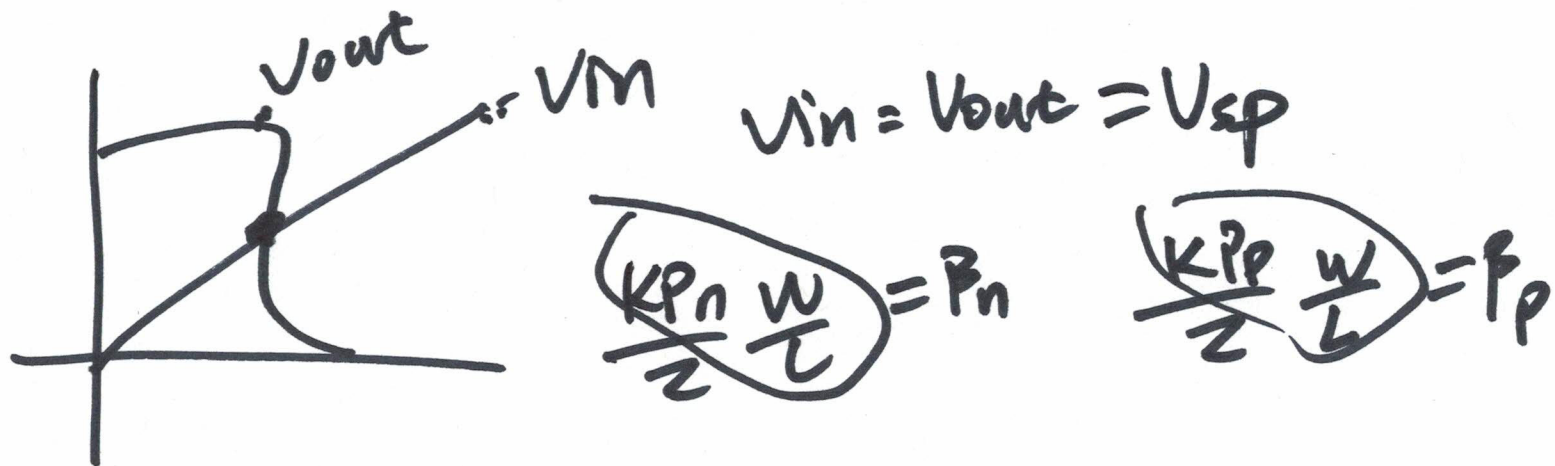

$$\frac{P_n}{2} (V_{GS} - V_{THN})^2 = \frac{P_p}{2} (V_{SG} - V_{THP})^2$$

$$\frac{P_n}{2} (V_{sp} - V_{THN})^2 = \frac{P_p}{2} (V_{DD} - V_{sp} - V_{THP})^2$$

$$\frac{P_n}{P_p} = \frac{(V_{DD} - V_{sp} - V_{THP})^2}{(V_{sp} - V_{THN})^2}$$

$$\sqrt{\frac{P_n}{P_p}} = \frac{V_{DD} - V_{sp} - V_{THP}}{V_{sp} - V_{THN}}$$

$$\sqrt{\frac{\beta_n}{\beta_p}} V_{sp} - \sqrt{\frac{\beta_n}{\beta_p}} V_{THN} = V_{DD} - \underline{V_{sp}} - V_{THP}$$

$$\left(1 + \sqrt{\frac{\beta_n}{\beta_p}}\right) \underline{V_{sp}} = V_{DD} + \sqrt{\frac{\beta_n}{\beta_p}} V_{THN} - V_{THP}$$

$$V_{sp} = \frac{V_{DD} + \sqrt{\frac{\beta_n}{\beta_p}} V_{THN} - V_{THP}}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$

$$= 2.5V$$

$$\sqrt{\frac{\beta_n}{\beta_p}} \approx 1$$

$$\begin{aligned} \beta_n = \beta_p &= K_P \frac{W_n}{L_n} \\ &= K_P \frac{W_p}{L_p} \end{aligned}$$

④

$K_{pP} = 40 \mu A/V^2$   
 $K_{pN} = 120 \mu A/V^2$  Because  $K_{pN} = 3 K_{pP}$

$$\frac{W_n}{L_n} = \frac{W_p}{L_p}$$

15