
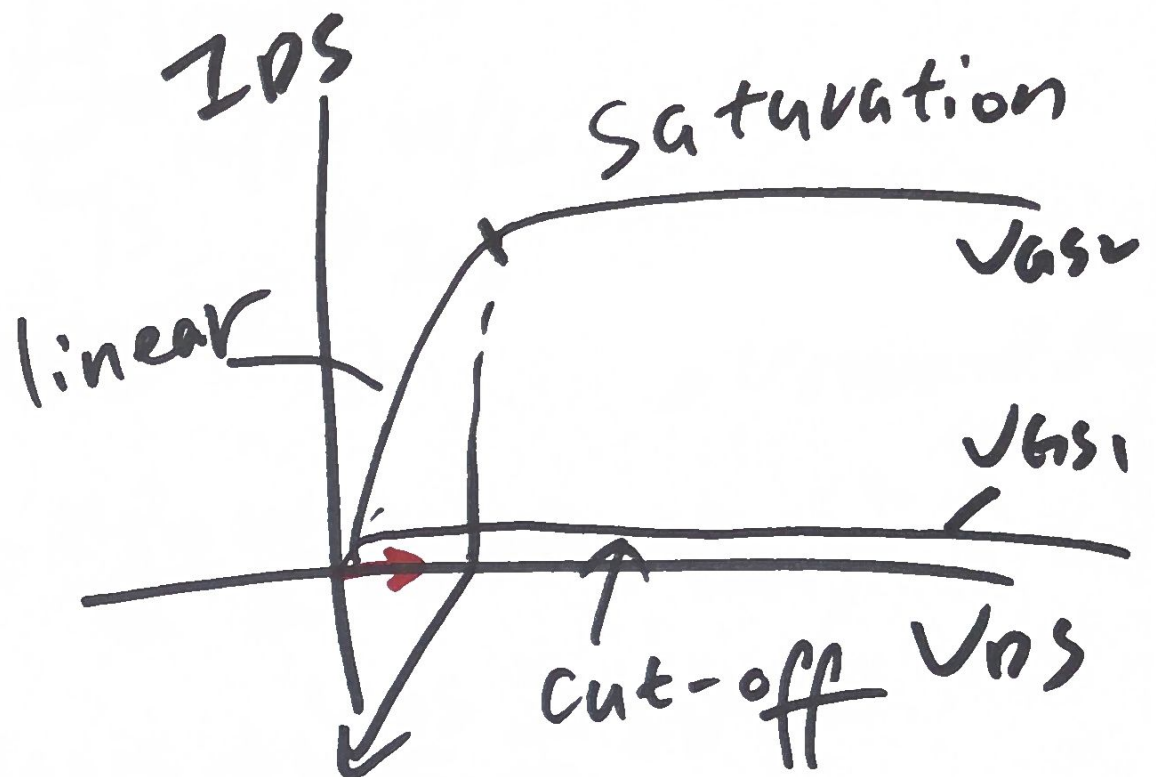


pinch-off

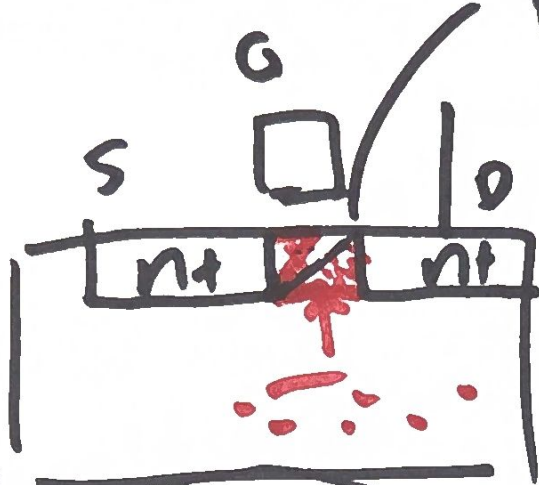

$$V_{DS} = V_{DS,sat}$$

$$V_{GS1} < V_{TH1}$$


Square Law Equation

$$I_{DS} = \frac{k_p n}{2} \frac{w}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

saturation region




①

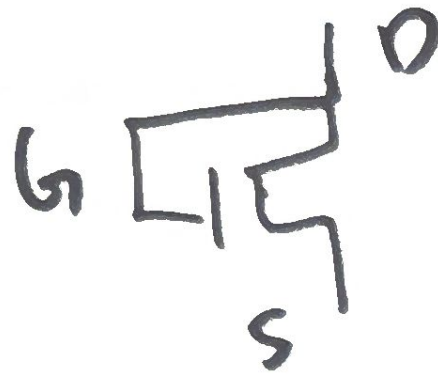

in ~~sat~~ saturation


$$V_{DS} > V_{DS,sat} = V_{GS} - V_{THN}$$

$\parallel$
 V_{GS}

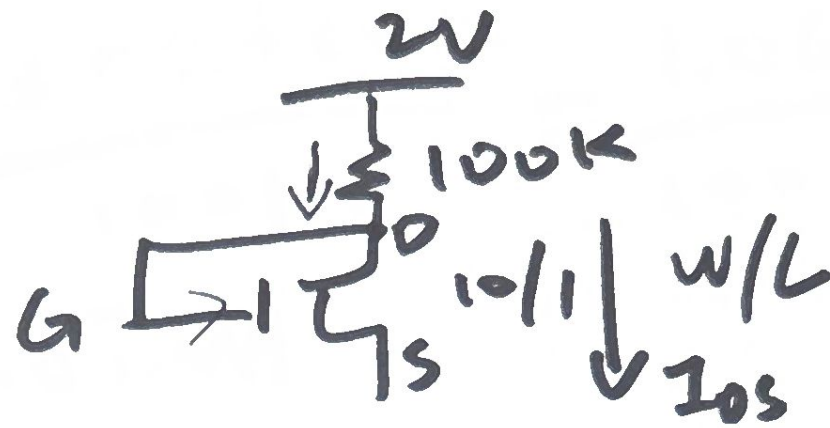

$$V_{THN} = 0.8V$$

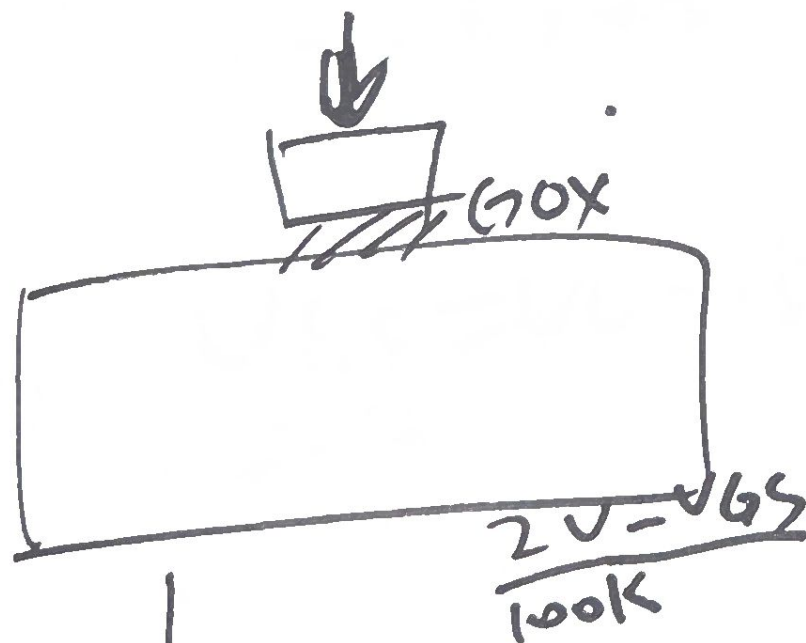
$$\begin{cases} I_{DS} = \frac{K_P n}{2} \frac{W}{L} (V_{GS} - V_{THN})^2 \\ I_{DS} \cdot 100k + \frac{V_{GS}}{10} = 2V \end{cases}$$



$$\begin{cases} K_P n = 120 \mu A/V^2 \\ \frac{W}{L} = 10 \end{cases}$$


$$\begin{aligned} &= 60 \mu A/V^2 \cdot 10 (V_{GS}^2 + 0.64 - 1.6V_{GS}) \\ &= 60 \cdot 10^{-6} / V^2 \cdot 10 V_{GS}^2 \end{aligned}$$
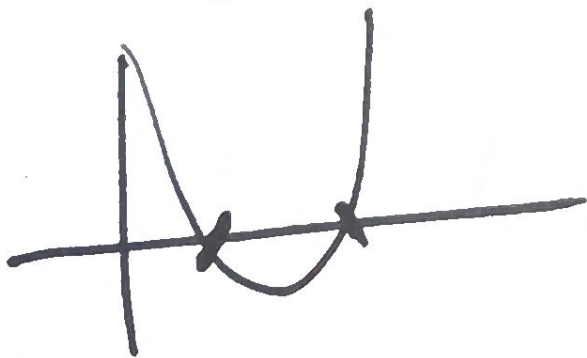
$$\hookrightarrow V_{GS} = \frac{0.933V}{0.65V} \quad (2)$$



$$I_{DS} = \frac{2 - 0.933}{100k} = \frac{1.067V}{100k}$$

$$= 10.67 \mu A$$

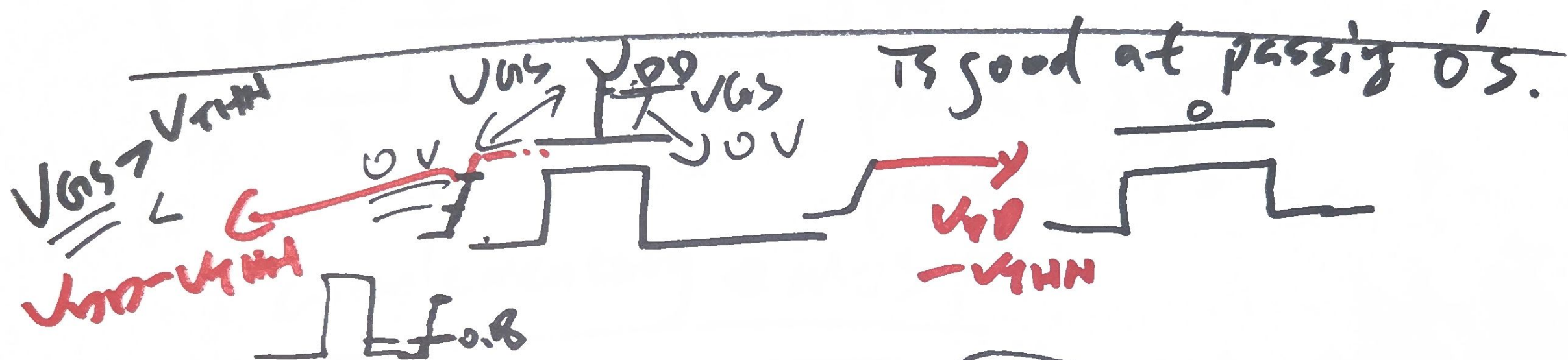


$$\underline{V_{GS}} = V_G - V_S = V_{DD} - V_S$$


$$= V_{thn}$$

$$\Rightarrow V_{DD} - V_{thn} = V_S$$

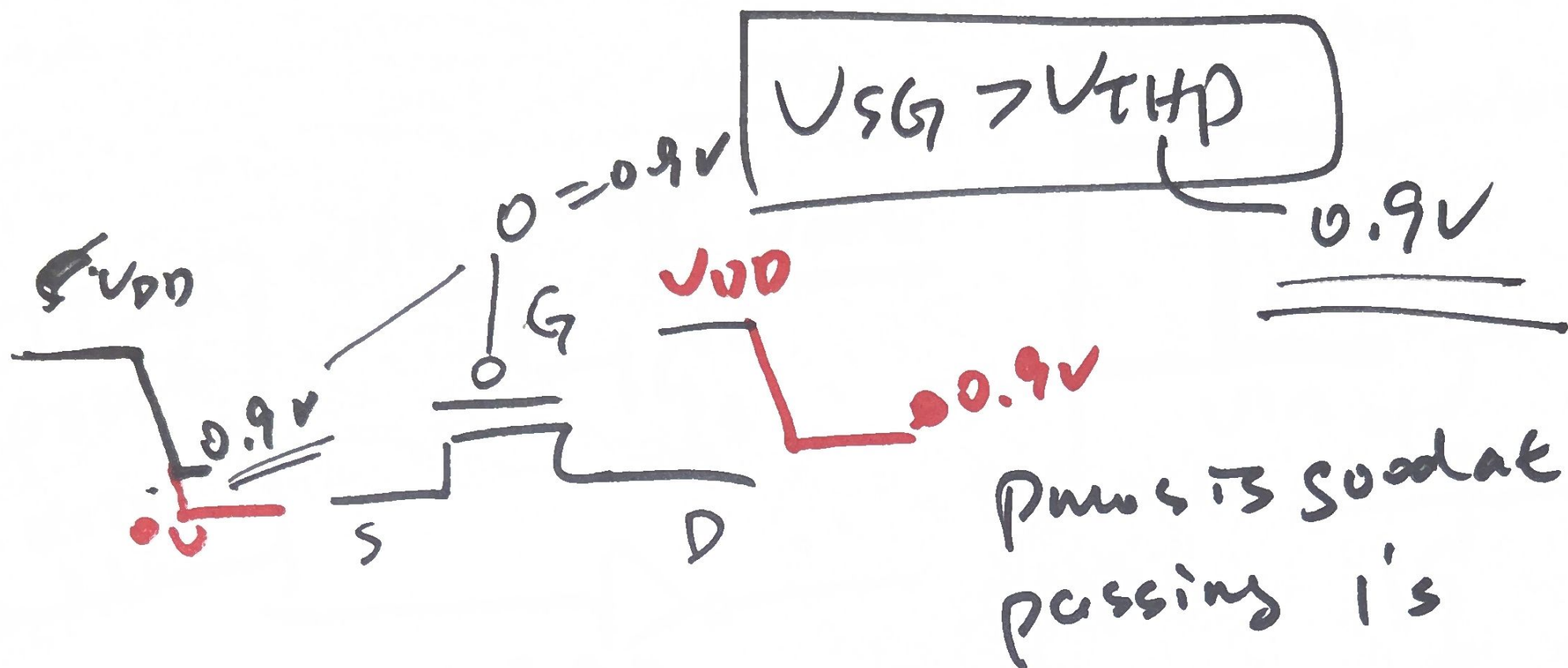
$$V_{GS} = V_{DD} - (V_{DD} - V_{thn}) = V_{thn} \quad (3)$$




Complementary CMOS

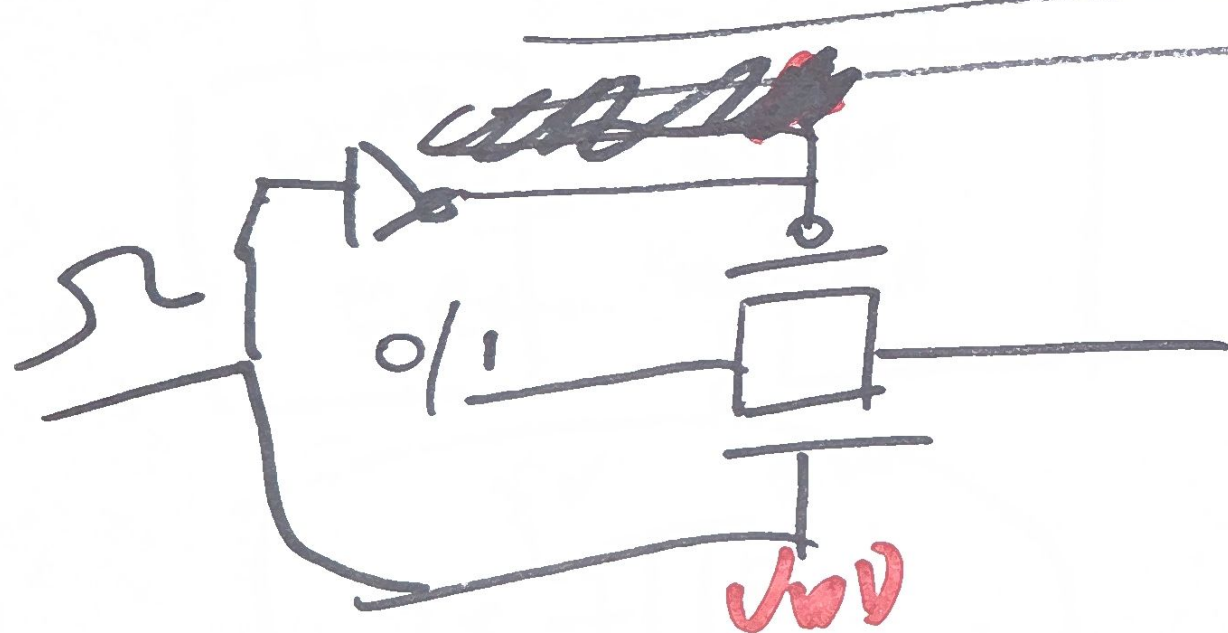



TG : Transmission Gate

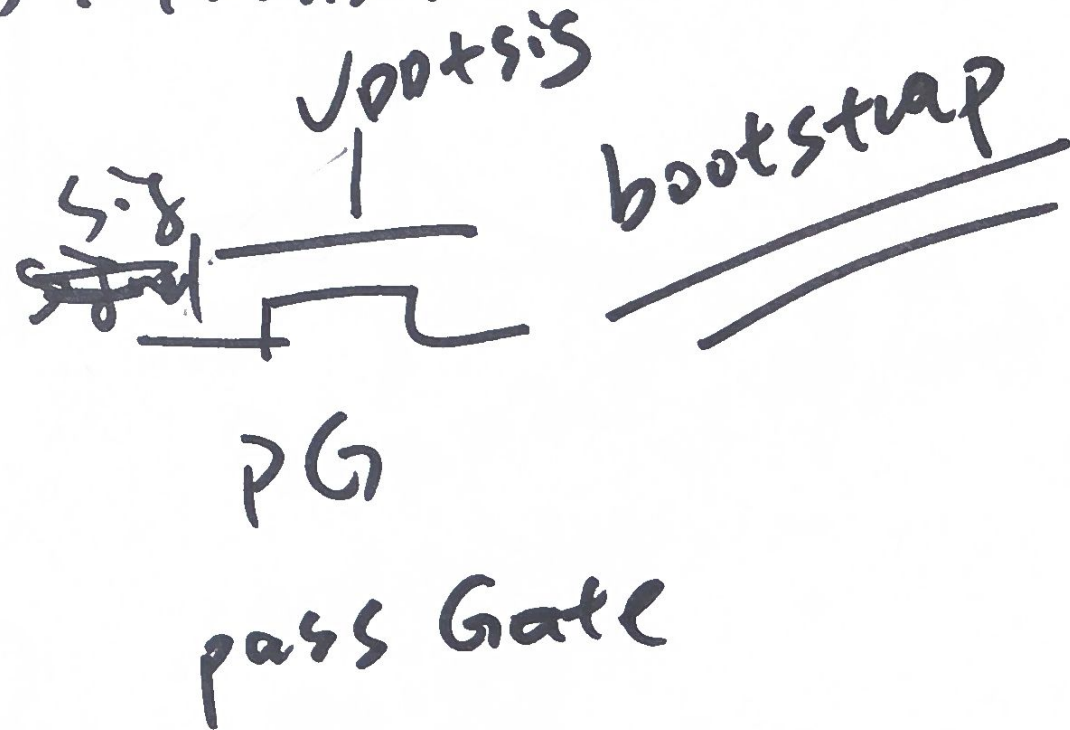



(4)

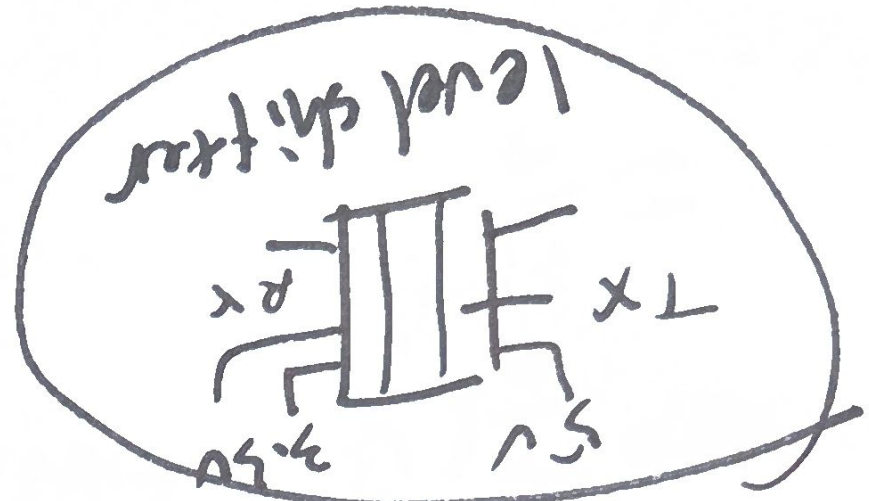

⑤

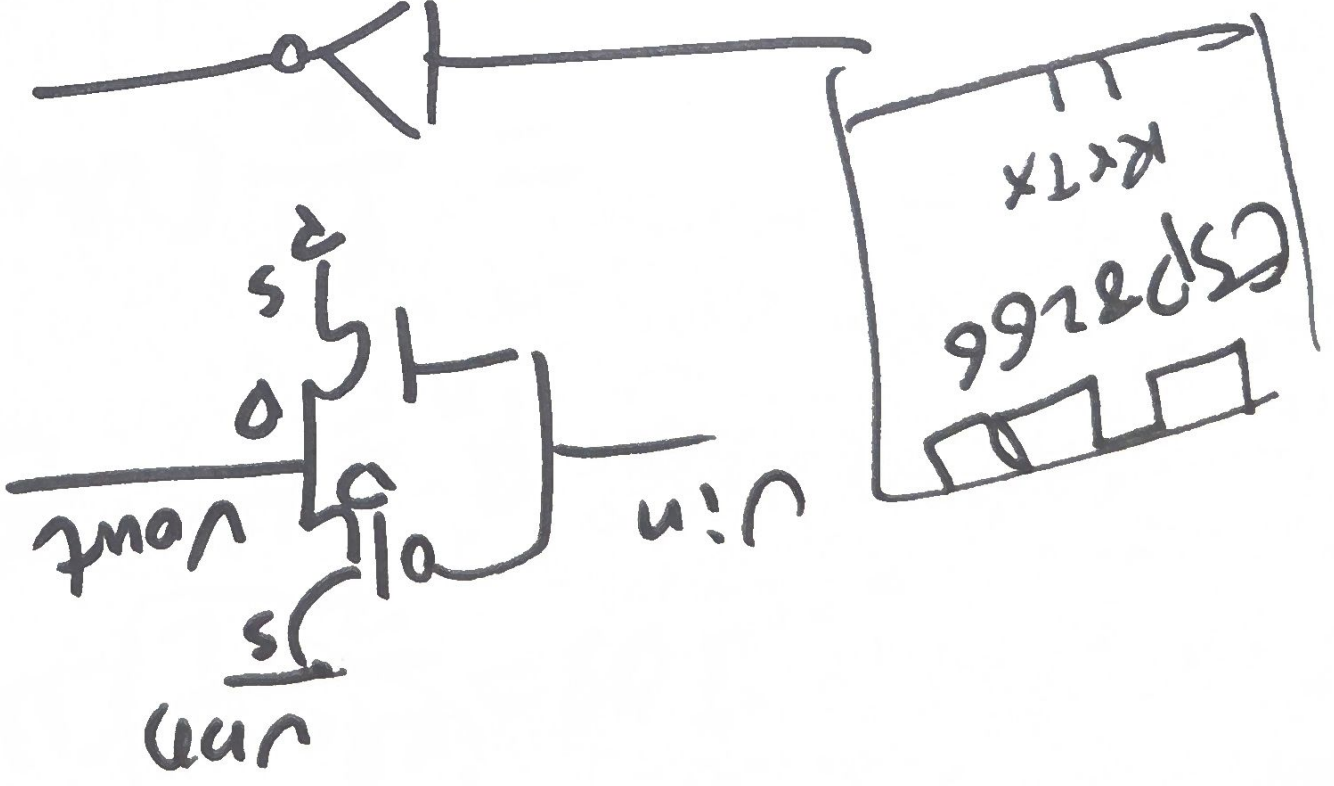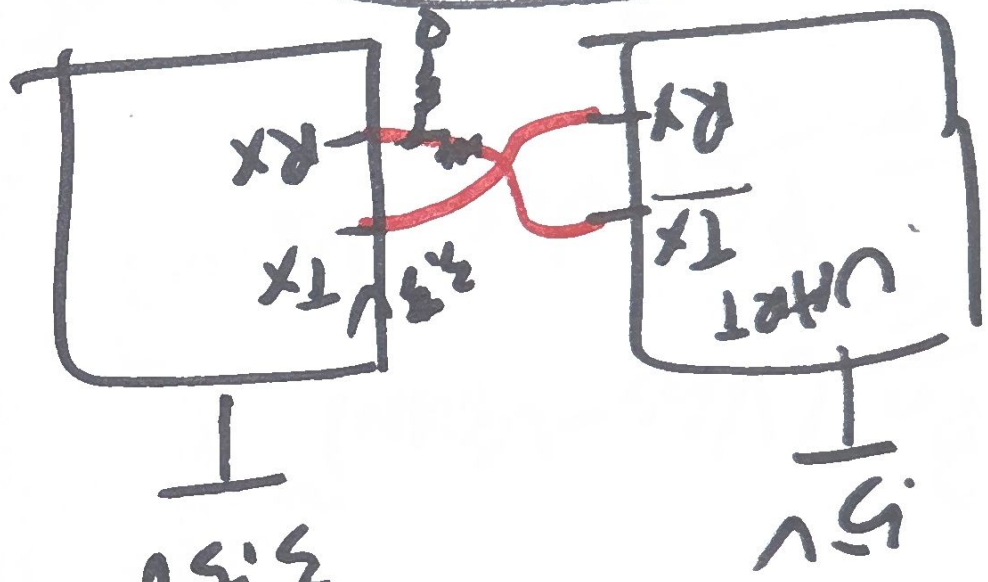

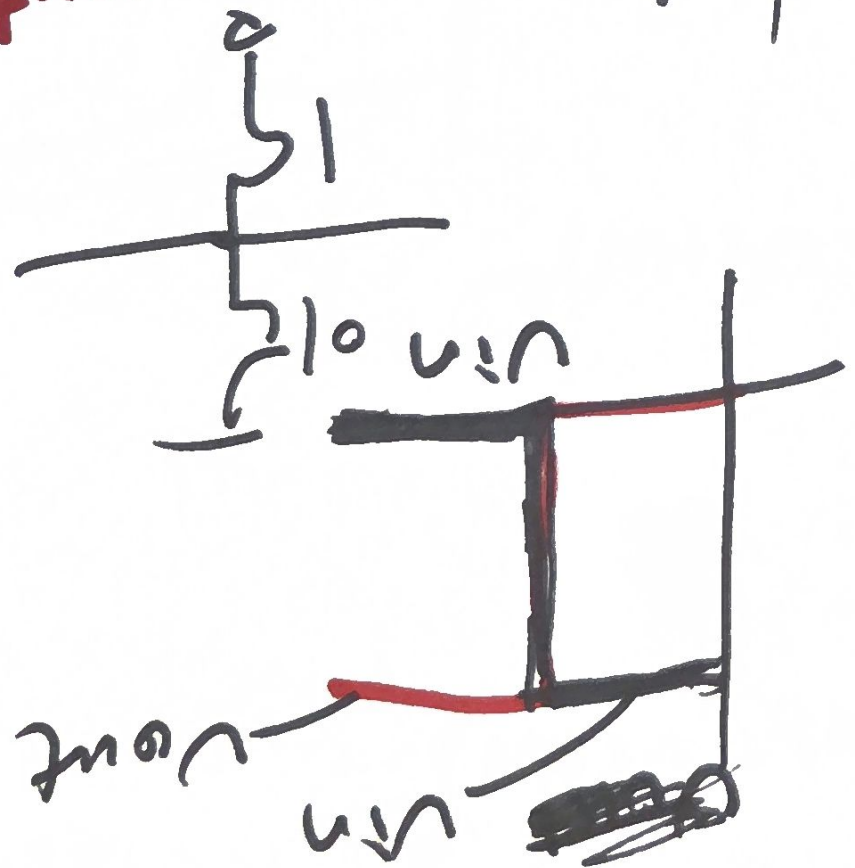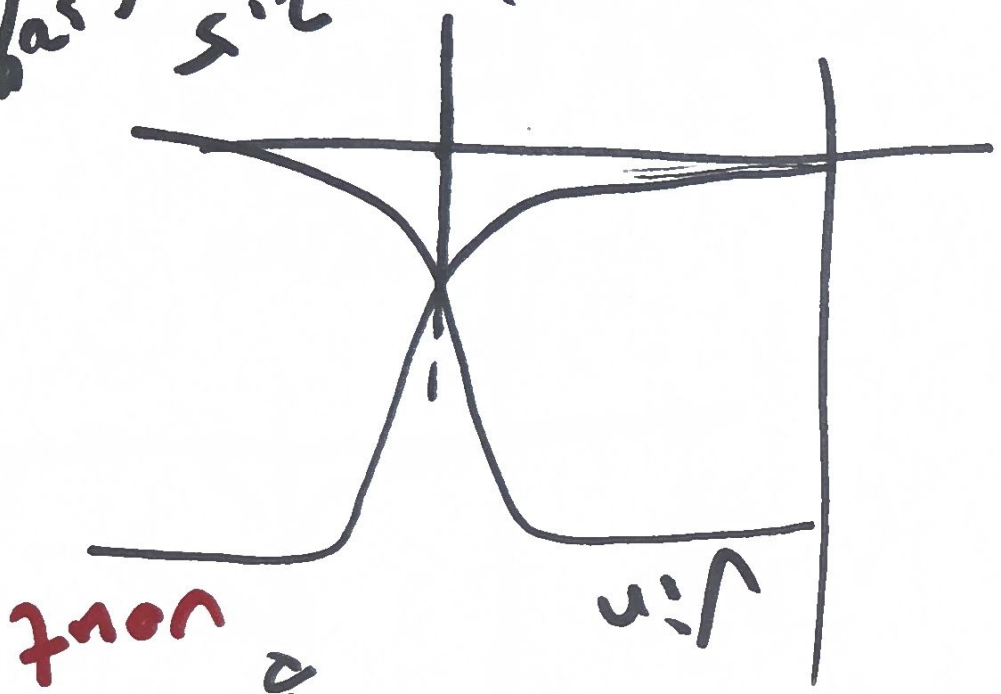switching point
 $V_{SD} = 2.5$
 (can't say)



$$I_{DS} = \frac{\mu_n C_{ox}}{2} \frac{W}{L} (V_{GS} - V_{THN})^2$$

$$\beta_n = \mu_n \cdot \frac{W}{L}$$

$$= \frac{\beta_n}{2} (V_{GS} - V_{THN})^2$$


$$\frac{\beta_n}{2} (V_{GS} - V_{THN})^2$$

$$= \frac{\beta_p}{2} (V_{SG} - V_{THP})^2$$

$$V_{SG} = \frac{\beta_n}{2} (V_{SP} - V_{THN})^2$$

$$= \frac{\beta_p}{2} (V_{DD} - V_{SP} - V_{THP})^2$$

(b)

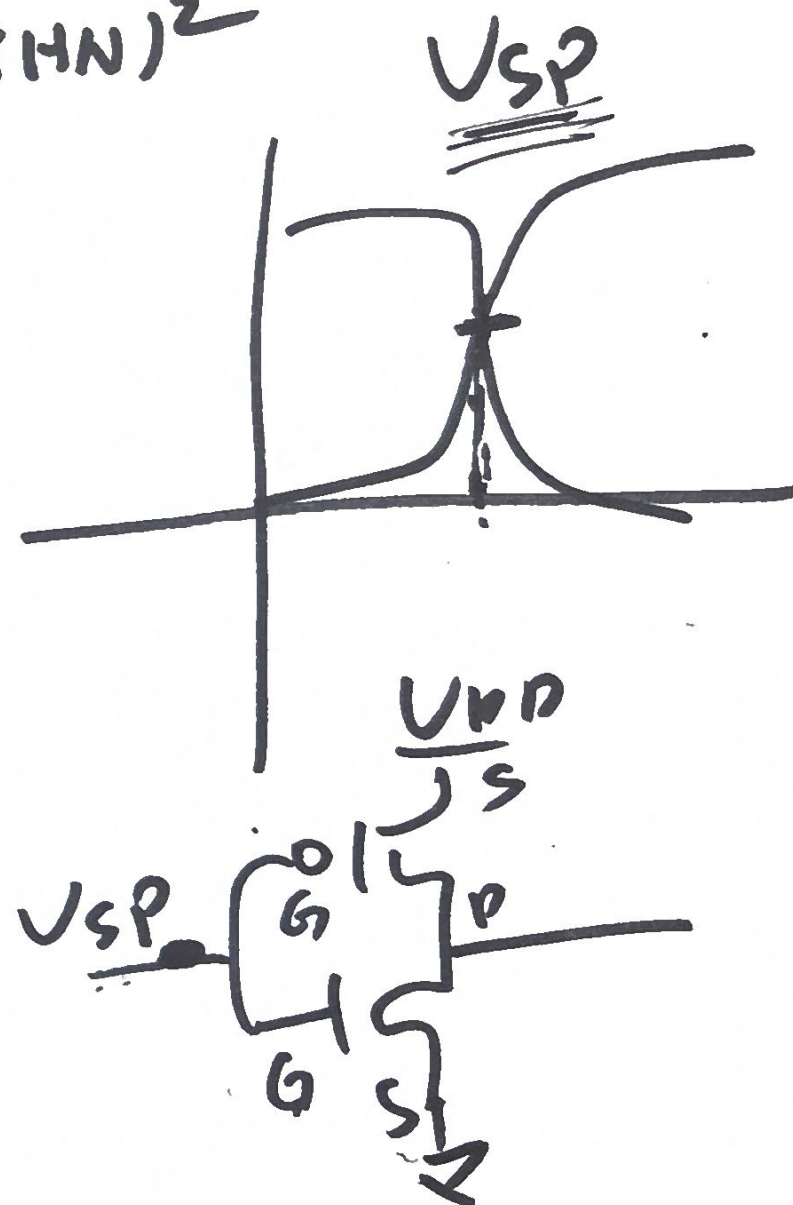

$$V_{SP} = \frac{\sqrt{\frac{\beta_n}{\beta_p}} \times V_{THN} + (V_{DD} - V_{THP})}{1 + \sqrt{\frac{\beta_n}{\beta_p}}}$$

⑦