
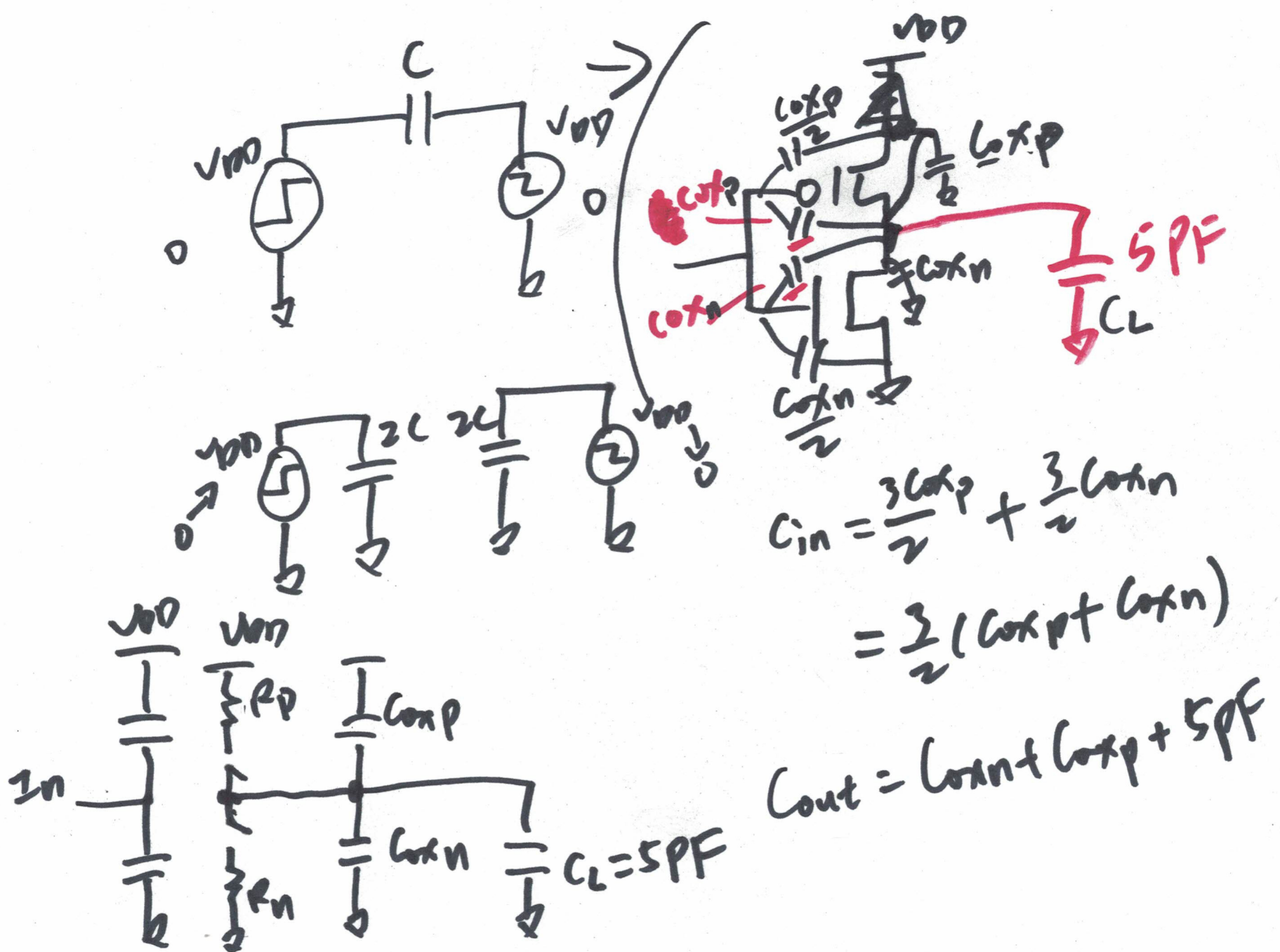


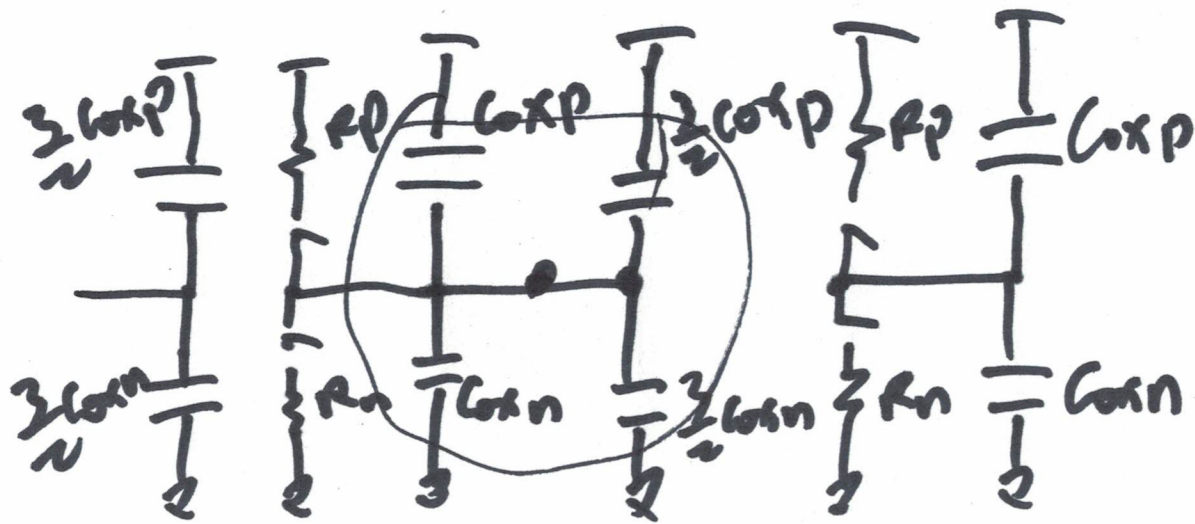




$$C_{tot} = \frac{5}{2} (C_{oxp} + C_{oxn})$$

$$t_{pHL} = 0.7 R_p \cdot C_{tot}$$

$$t_{pHL} = 0.7 R_n \cdot C_{tot}$$

(2)

Dynamic
Average Power

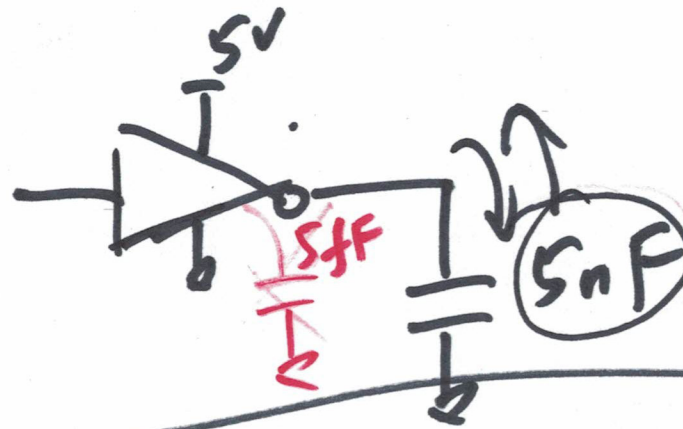



$$I_{avg} = \frac{Q}{t} = \frac{V_{DD} \cdot C}{t}$$

$$P_{avg} = V_{DD} \cdot I_{avg} = \frac{V_{DD}^2}{2} C f$$

PULSE(0 5 0 1p 1p 1μ 2μ)

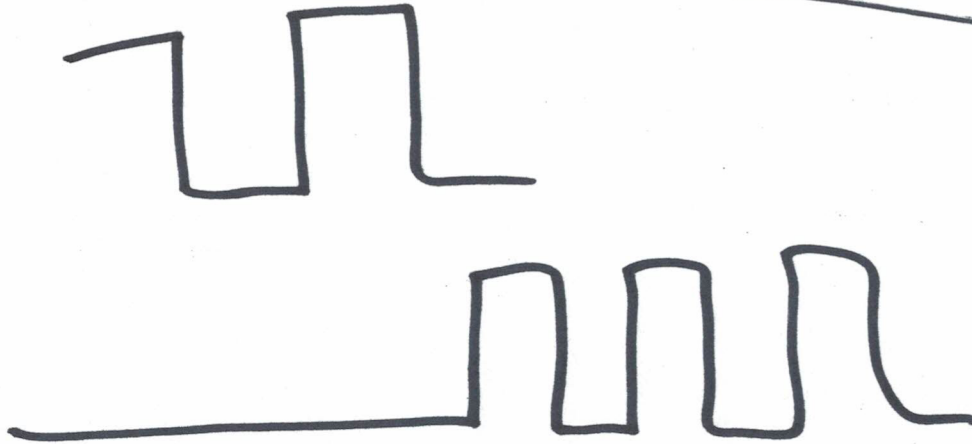↓ ↓ ↓ ↓ ↓ ↓ ↓
 Low High delay rising falling on
 Voltage Voltage edge edge time period





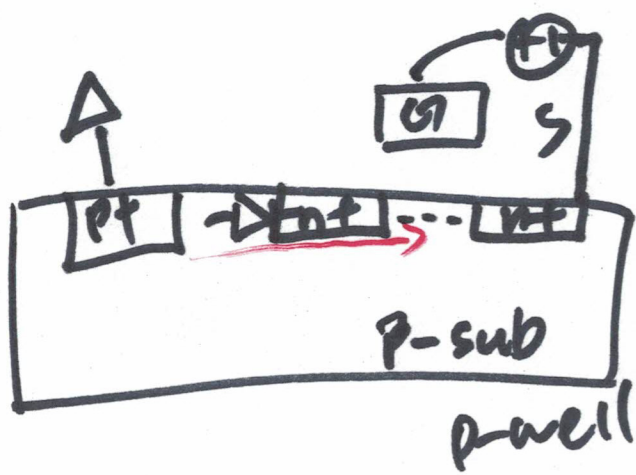

Nmos
 $V_{GS} > V_{TH}$

$V_{CHN} \uparrow$

Body Effect

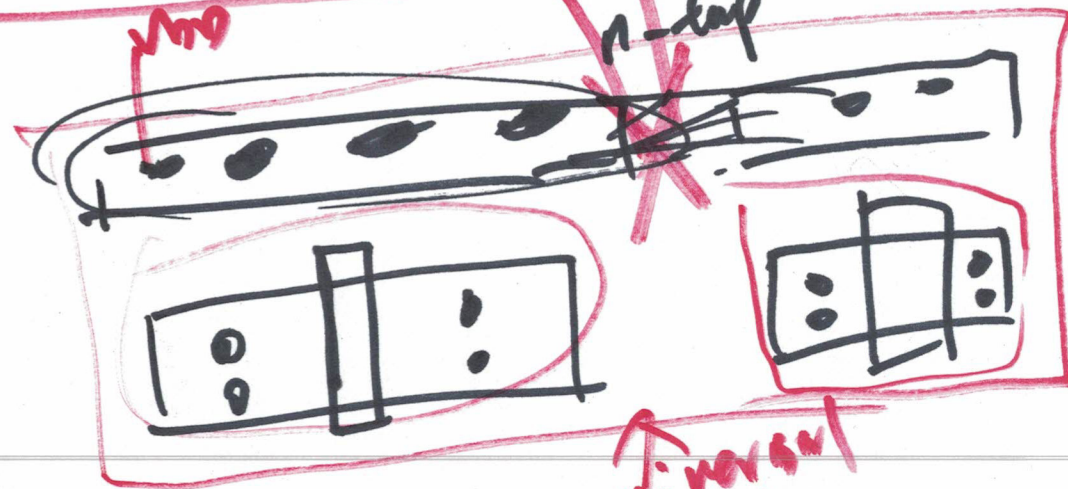
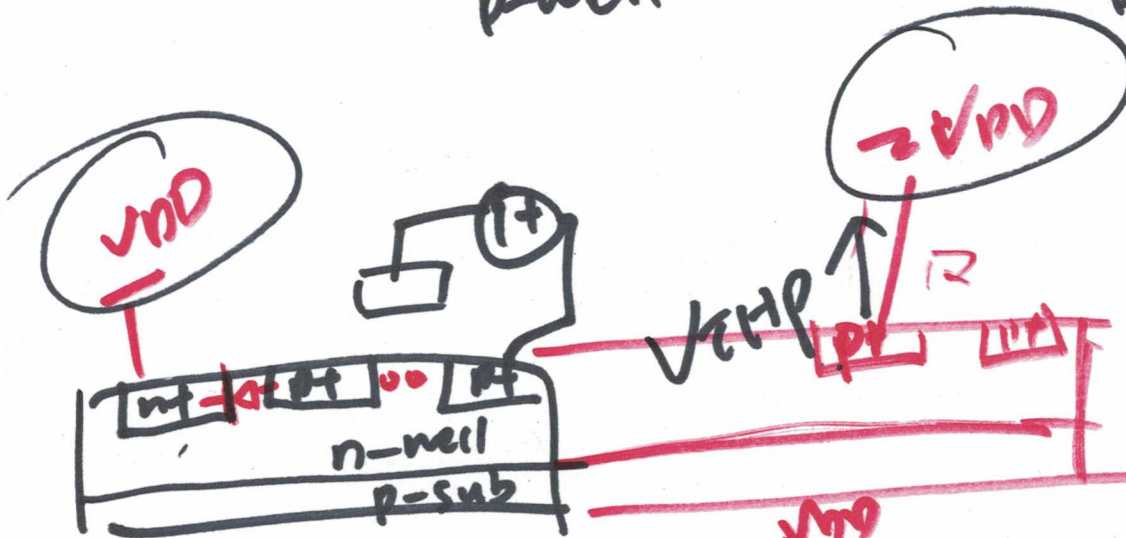


(4)


① no universal
 n-well

Stick Programs

3 in parallel

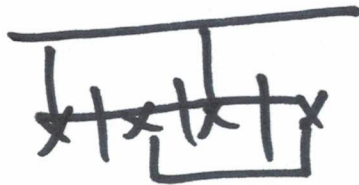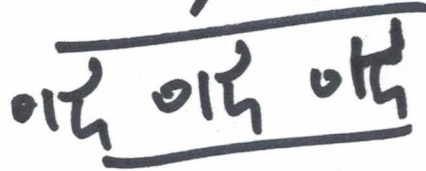


4 in parallel

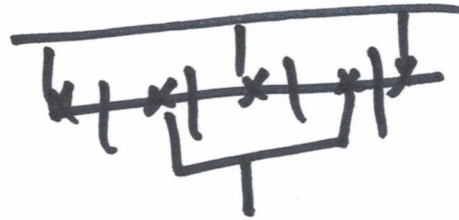

A01

5 in parallel

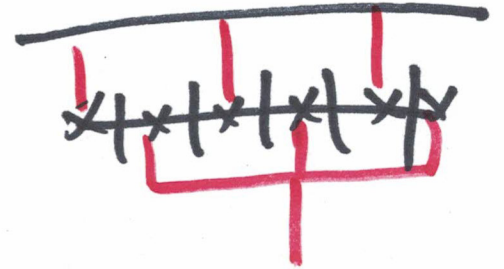


$$Y = AB + CD$$

$$= \overline{\overline{AB + CD}}$$

$$= \overline{\overline{AB} \cdot \overline{CD}}$$

$$= (\overline{A} + \overline{B}) \cdot (\overline{C} + \overline{D})$$

(5)

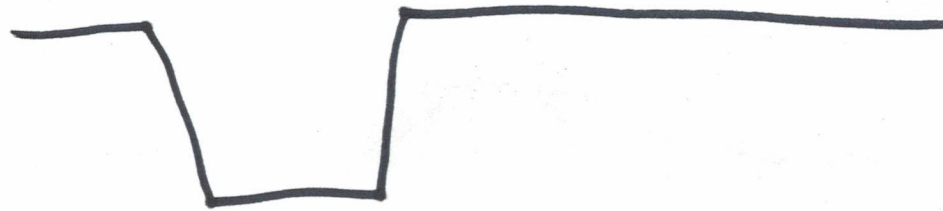

$t_r, t_f, t_{PHL}, t_{PLH}$

△ R-2R DAC
Thevenin's circuit
 V_{out}

△ SAR ADC
Algorithm
State diagrams

Q

△ CS layers

↓
Quit

↓
HW

↓
lecture notes

Miller


90-min

Thur 2:30-4pm

close book

close notes

calculator is allowed

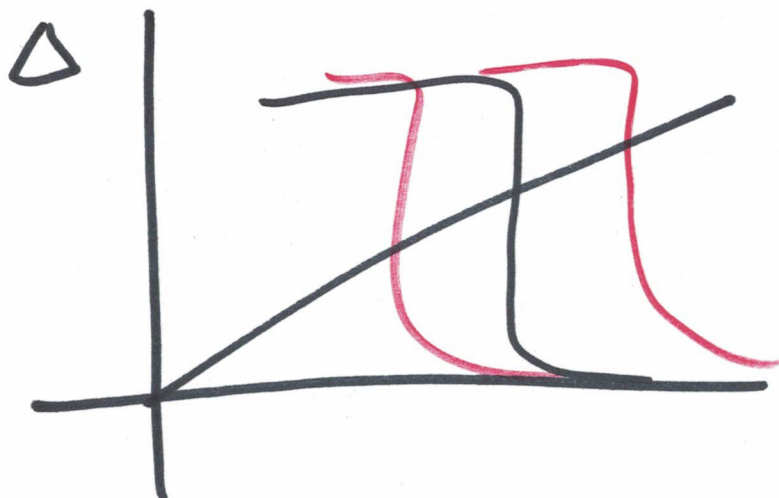

△ Dickson's charge pump circuit.
voltages at different nodes

④