


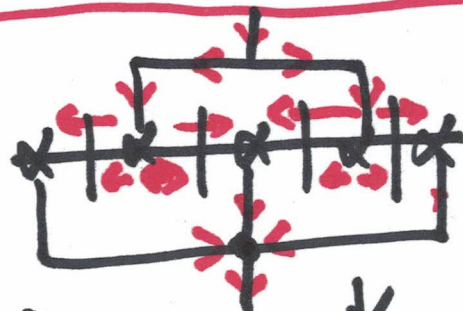


stick diagram


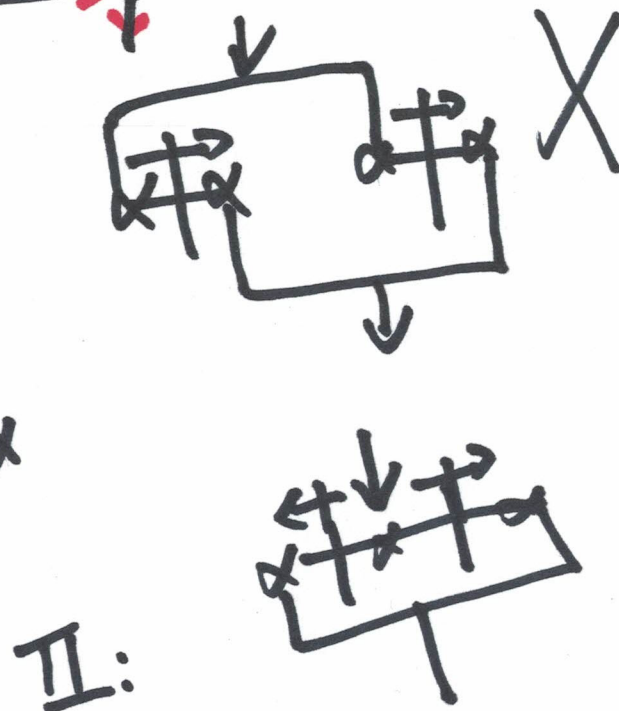


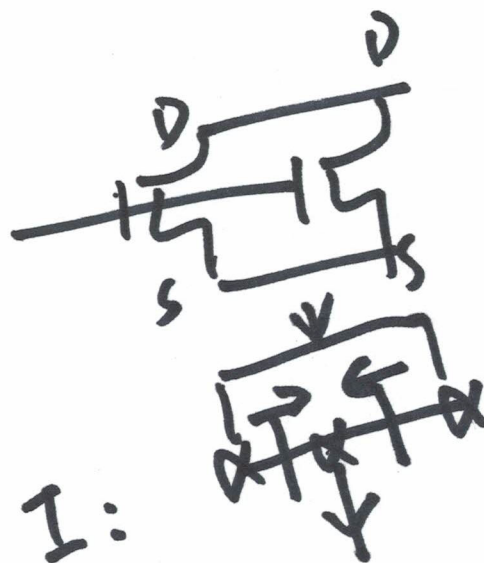series
 $\downarrow$
 $-1g$
 $-1g$
 $-1g$
 $-1g_s$



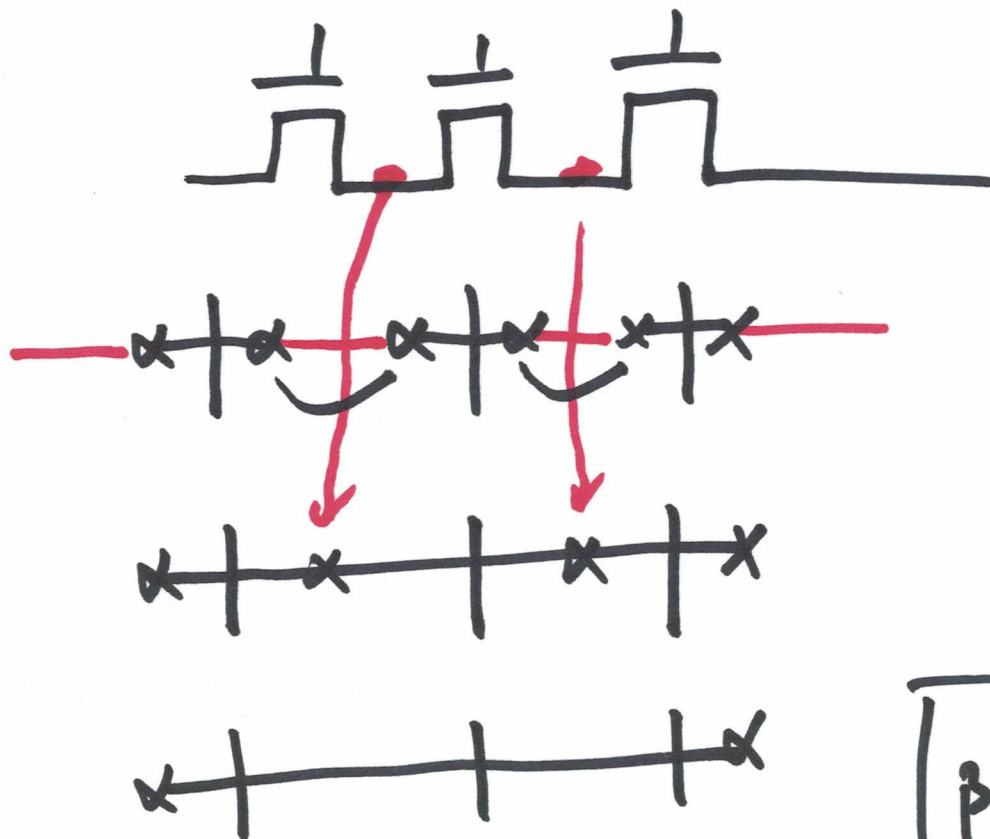

$$\beta = \frac{K_P}{2} \frac{W}{L}$$

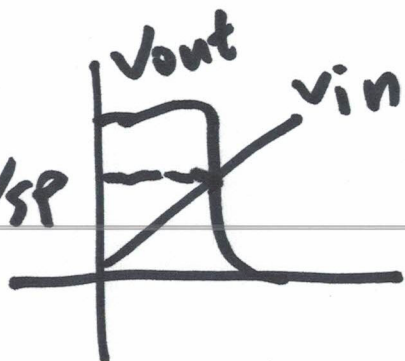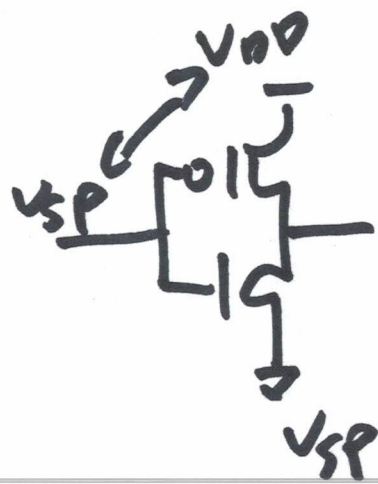

$$\frac{\beta_n}{2} (\underline{\underline{V_{DD} - V_{THN}}})^2 = \frac{\beta_p}{2} (V_{DD} - V_{THP})^2$$

$$\frac{\beta_n}{2} (V_{sp} - V_{THN})^2 = \frac{\beta_p}{2} (V_{DD} - V_{sp} - V_{THP})^2$$

$$\frac{\beta_n}{\beta_p} = \frac{(V_{DD} - V_{sp} - V_{THP})^2}{(V_{sp} - V_{THN})^2}$$

(2)

$$\sqrt{\frac{\beta_n}{\beta_p}} = \frac{V_{DD} - V_{SP} - V_{THP}}{V_{SP} - V_{THN}}$$

$$(V_{SP} - V_{THN}) \sqrt{\frac{\beta_n}{\beta_p}} = V_{DD} - V_{SP} - V_{THP}$$

$$V_{SP} \left(\sqrt{\frac{\beta_n}{\beta_p}} + 1 \right) = V_{THN} \sqrt{\frac{\beta_n}{\beta_p}} + V_{DD} - V_{THP}$$

$$V_{SP} = \frac{V_{THN} \sqrt{\frac{\beta_n}{\beta_p}} + V_{DD} - V_{THP}}{\sqrt{\frac{\beta_n}{\beta_p}} + 1} = 2.5V$$

$$\begin{cases} V_{DD} = 5V \\ V_{THN} = 0.8V \\ V_{THP} = 0.9V \end{cases}$$

$$\Rightarrow \sqrt{\frac{\beta_n}{\beta_p}} \approx 1$$

(3)

μ_n

$$\sqrt{\frac{\beta_n}{\beta_p}} = 1 \quad \beta_n = \beta_p$$



$$\beta_n = \frac{K_p n}{L} \quad \beta_p = \frac{K_p p}{L}$$

$$= 120 \mu\text{A}/\text{V}^2 \cdot \frac{W_n}{L_n} = 40 \mu\text{A}/\text{V}^2 \cdot \frac{W_p}{L_p}$$



$$I_{DS} = \frac{\beta_n}{2} (V_{GS} - V_{TH})^2$$
$$= \frac{\beta_n}{2} (V_{GS} - V_{TH})^2$$



$$\frac{W_n}{L_n} = \frac{1}{3} \frac{W_p}{L_p}$$

Diodes

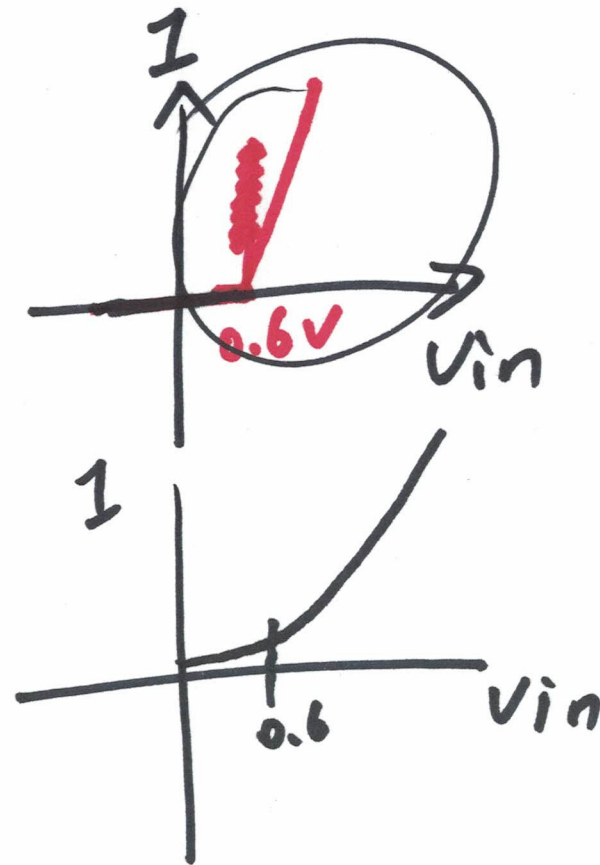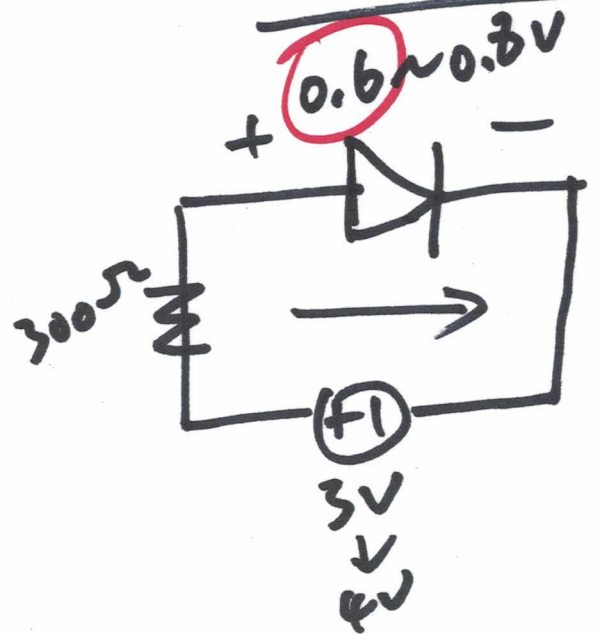

Zener Diode

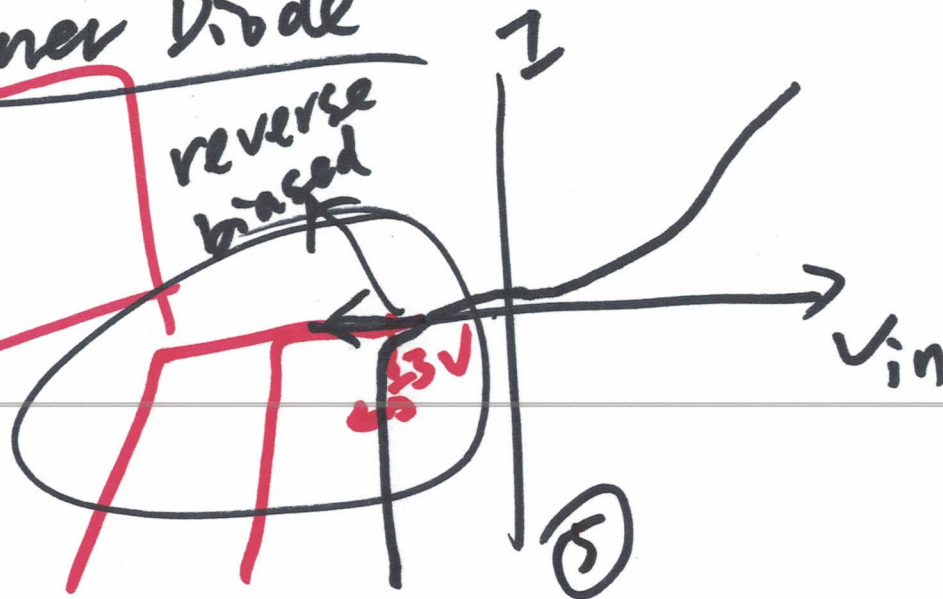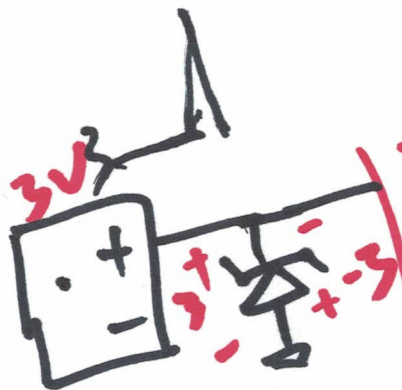

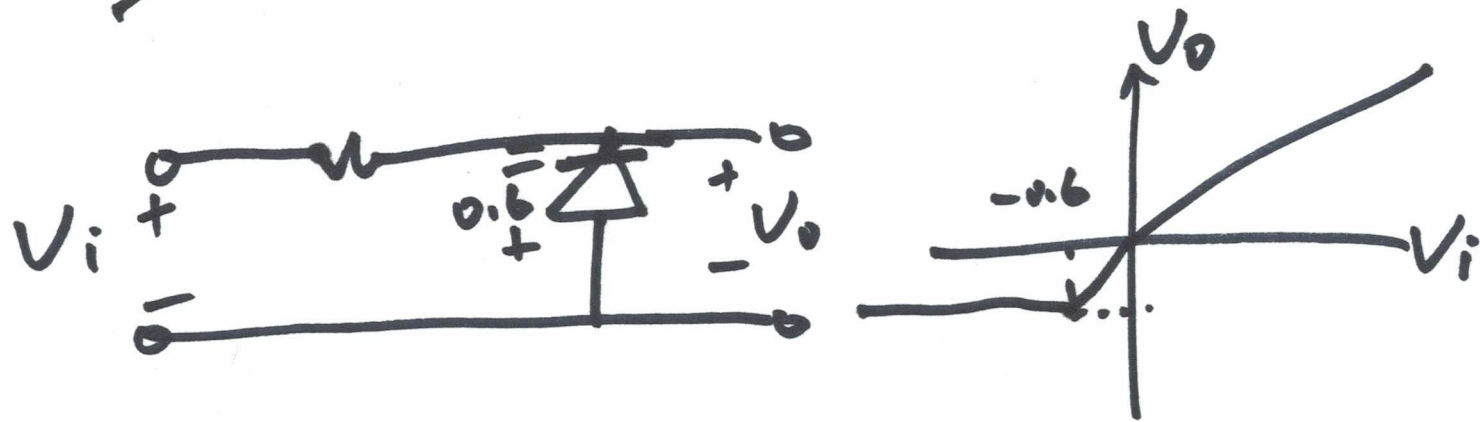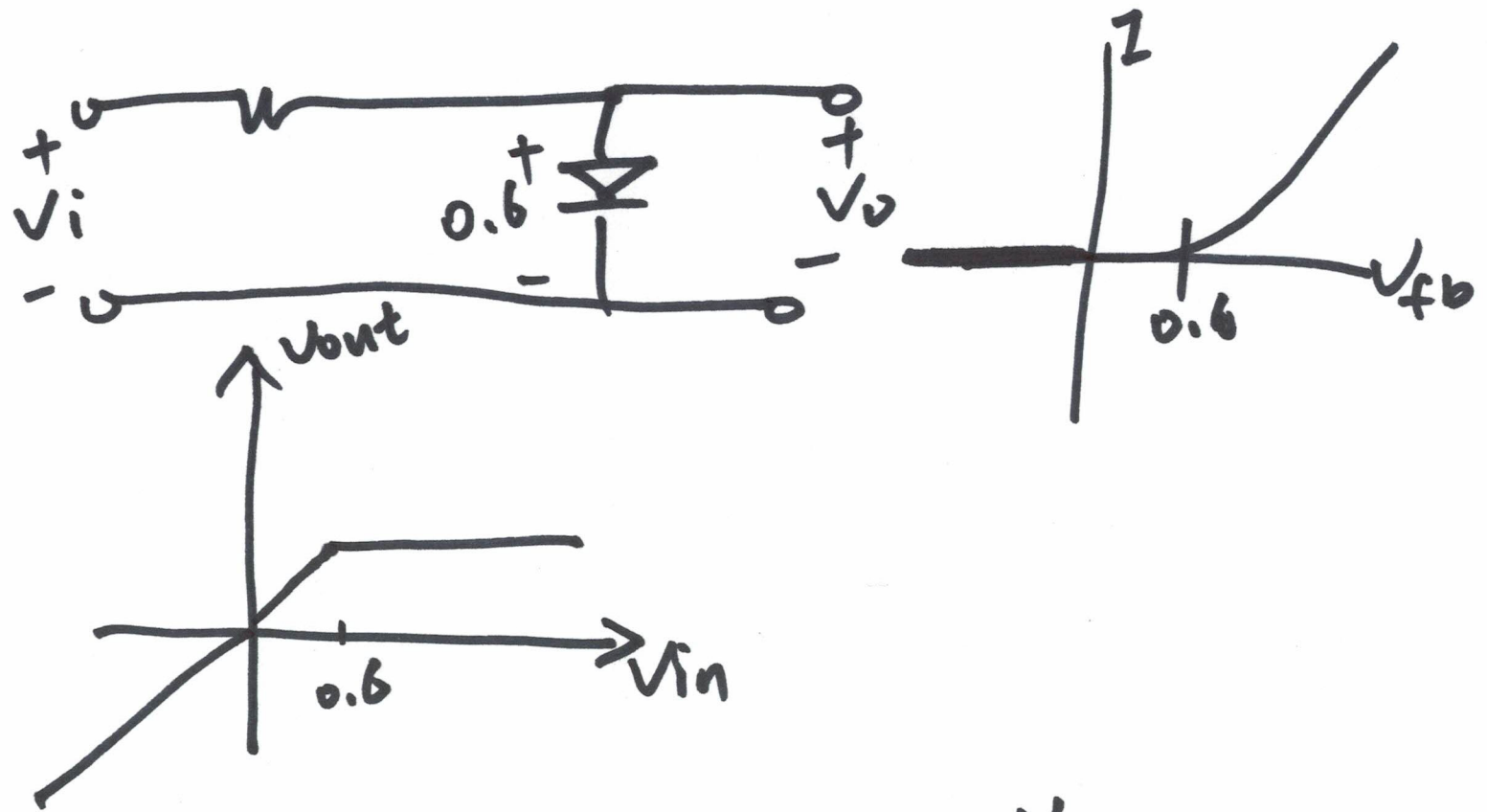

(6)

