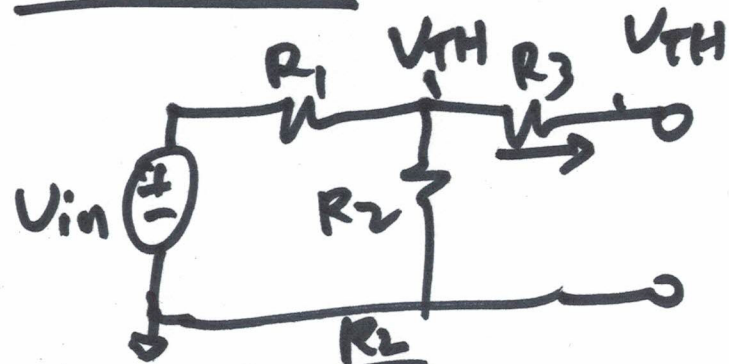



Thevenin:



$$V_{TH} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$


$$R_{TH} = R_3 + R_1 \parallel R_2$$

Voltage Divider

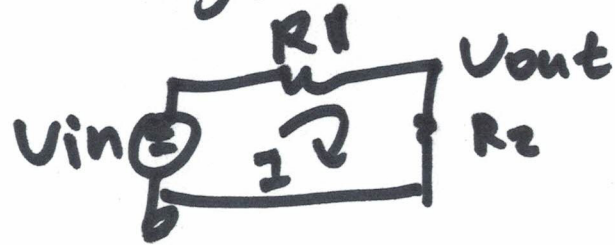

$$\frac{V_{in}}{R_1 + R_2} \cdot R_2 = V_{out}$$

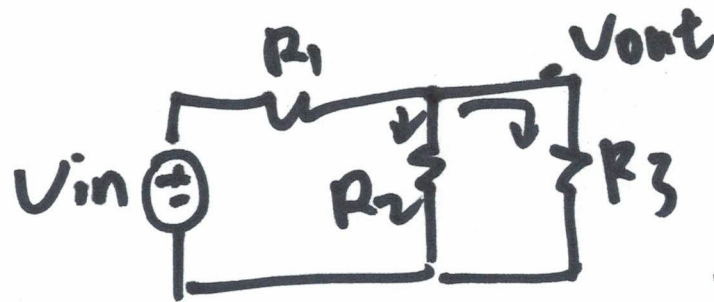
$$V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_{in}$$



$$V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_{in}$$

~~.~~

SPICE:

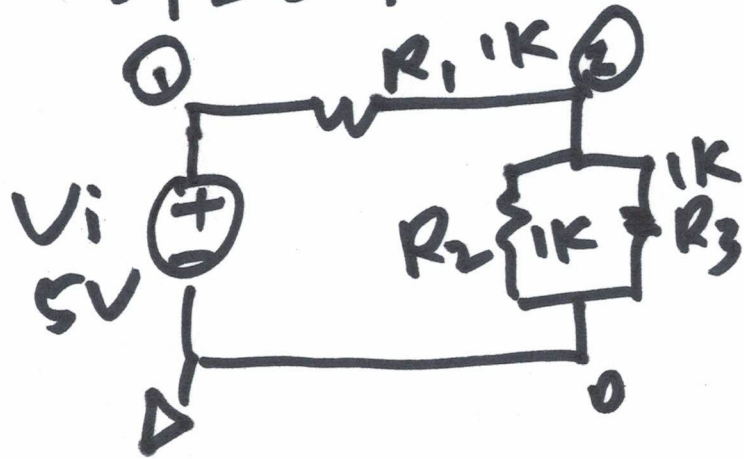




V_i 1 0 5V

R_1 1 2 1K


R_2 2 0 1K

R_3 2 0 1K

.tran 0 1 0.001

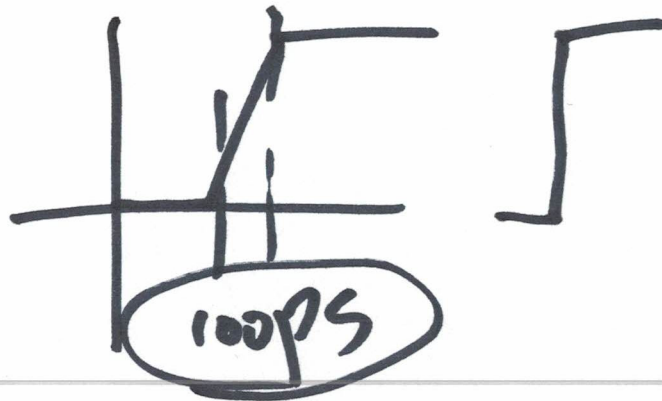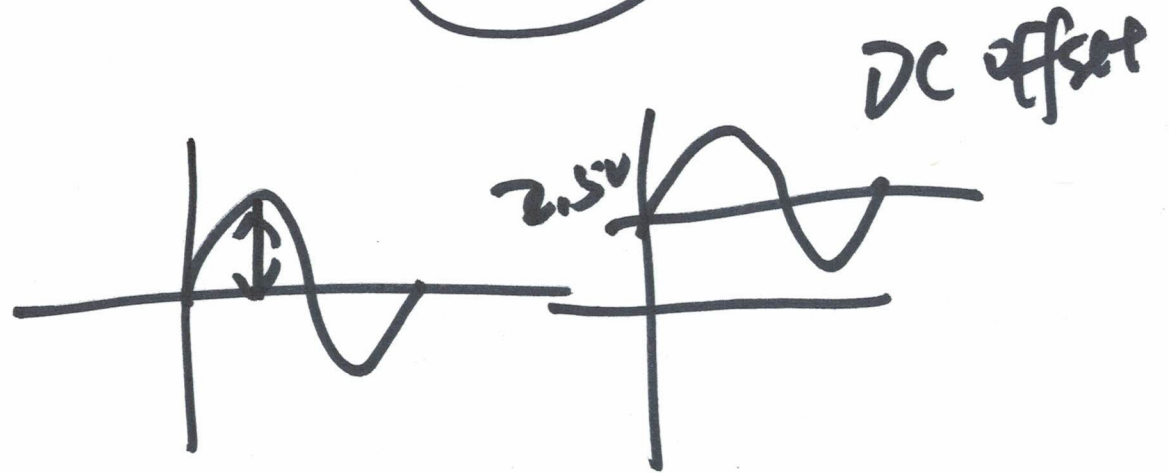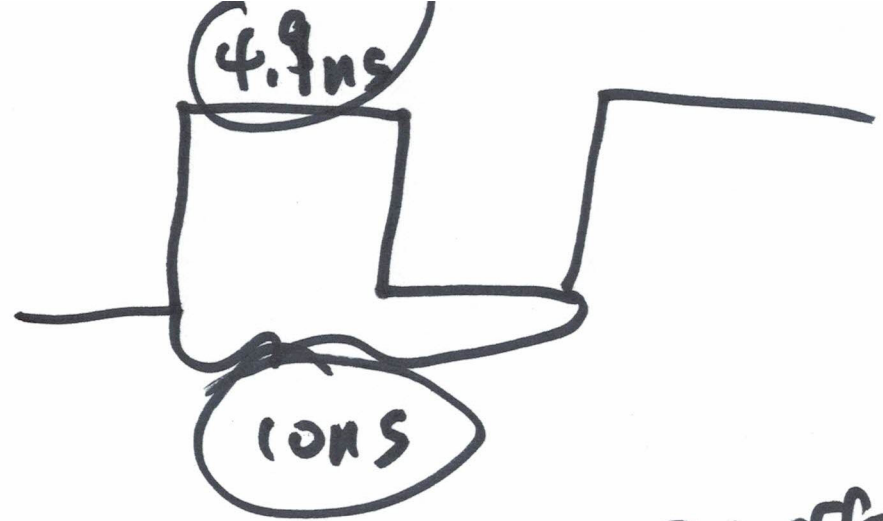

(2)

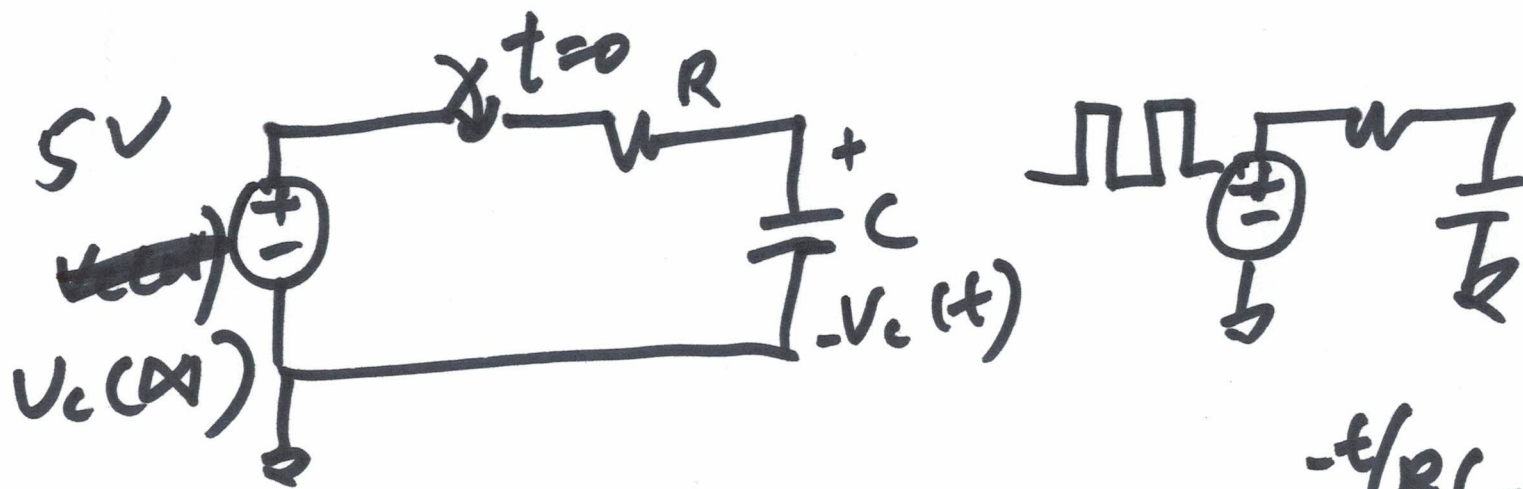

$$V_c(t) = V_c(\infty) + (V_c(0) - V_c(\infty))e^{-t/RC}$$

① $V_c(0) \neq 0$ forced response. Step response

$$V_c(t) = V_c(\infty) + (V_c(0) - V_c(\infty))e^{-t/RC}$$


② $V_c(0) = 0$

$$V_c(t) = V_c(\infty) - V_c(\infty)e^{-t/RC}$$

$$= V_c(\infty)(1 - e^{-t/RC})$$

③



③ $V_C(\infty) = 0$ natural response

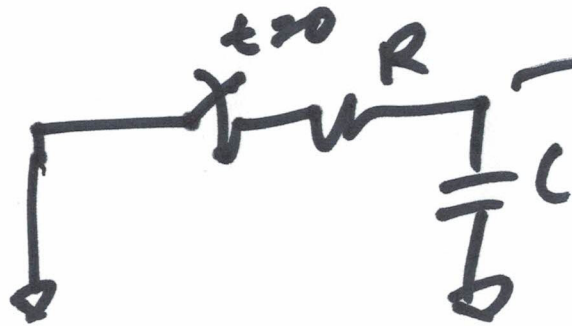

$$V_C(t) = V_C(0) e^{-t/RC}$$

$$\underline{\underline{V_C(t) = V_C(\infty) (1 - e^{-t/RC})}}$$

$$= \cancel{V_{in}} (1 - e^{-t/RC})$$

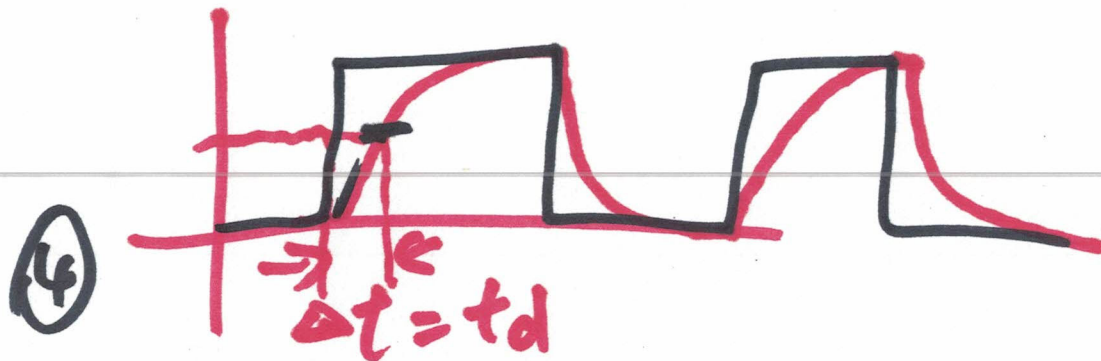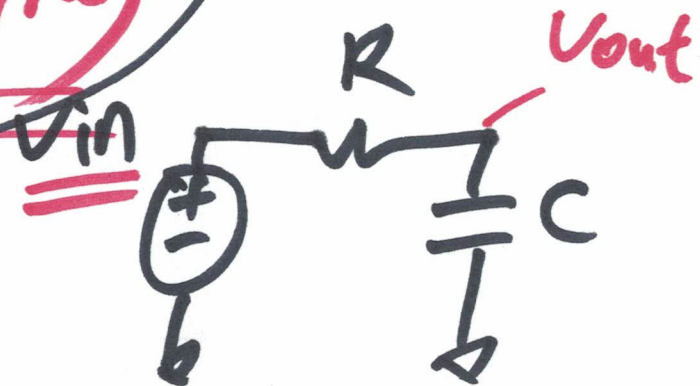


$$\frac{1}{2} V_{in} = \underline{\underline{V_{in}}} (1 - e^{-t/RC})$$

$$e^{-t/RC} = 0.5$$



$$\ln e^{-t/RC} = \underline{\underline{\ln 0.5}}$$

$$\frac{-t}{RC} = -0.7$$

$$\boxed{t_0 = 0.7 RC}$$

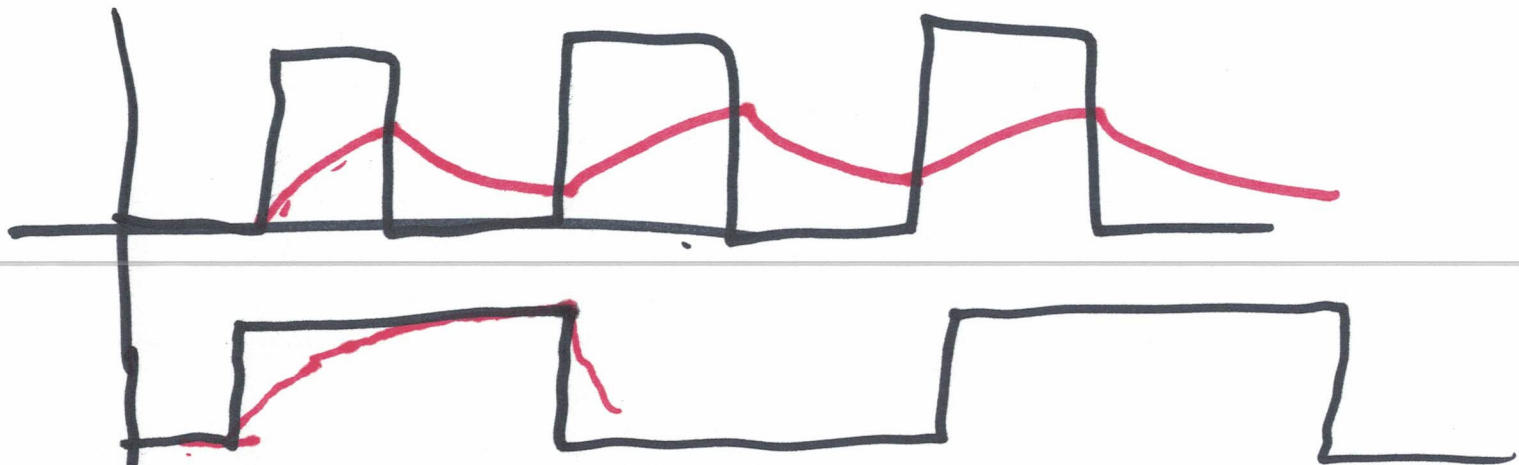


(4)

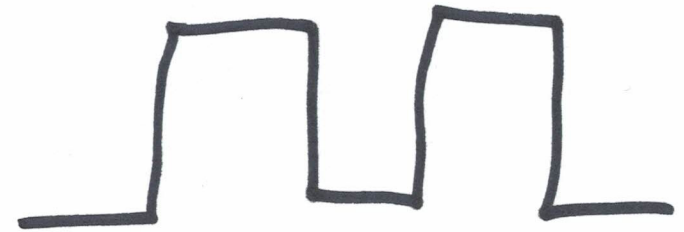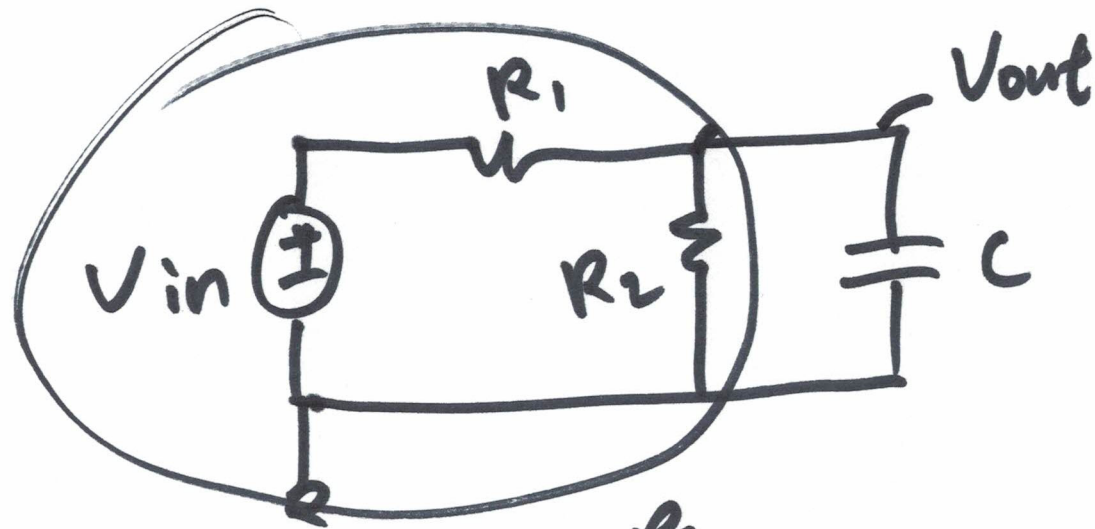


$$V_{TH} = V_{in} \cdot \frac{R_2}{R_1 + R_2}$$

$$R_{TH} = R_1 \parallel R_2$$

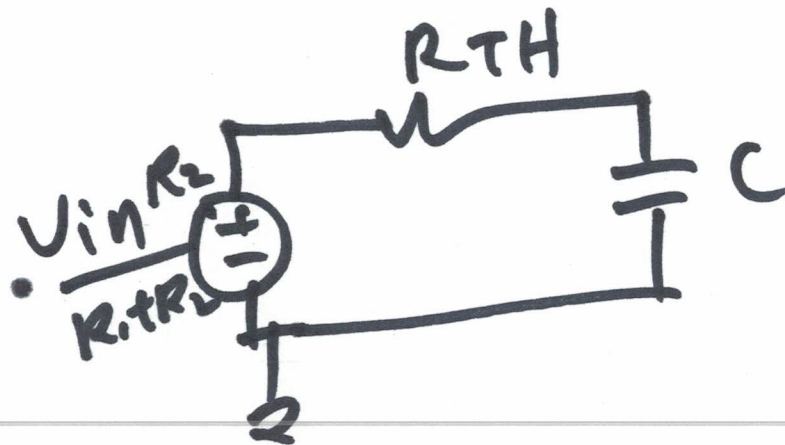


⑤

Superposition

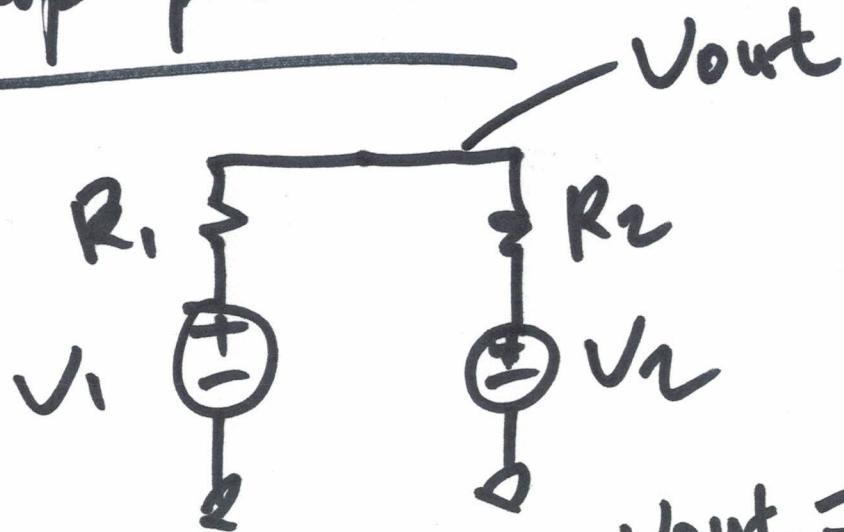


$$V_{out} = V_1 \frac{R_2}{R_1 + R_2}$$

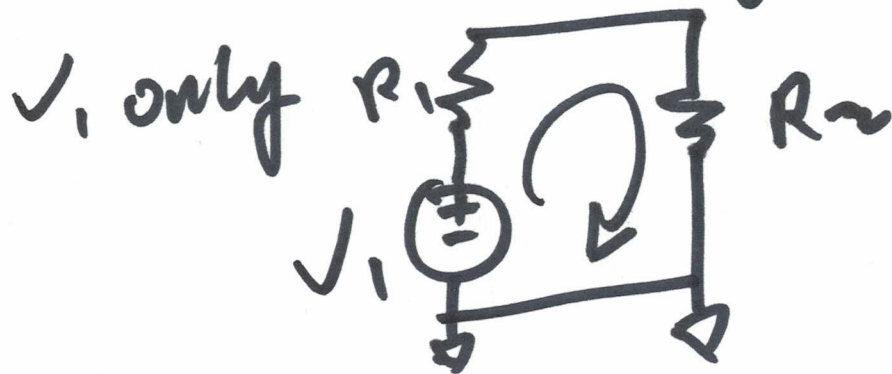

$$V_{out} = V_2 \frac{R_1}{R_1 + R_2}$$

V_2 only

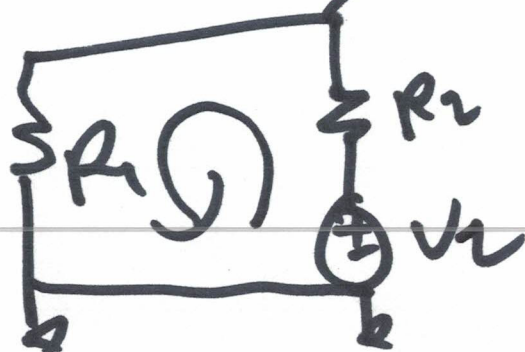

Overall:

$$V_{out} = V_1 \frac{R_2}{R_1 + R_2} + V_2 \frac{R_1}{R_1 + R_2}$$

⑥