

Data types, operators, combinational logic

Calvin Reese
cjreese@fortlewis.edu

2/10/22

1 Introduction

This HW, we worked on refreshing our binary logic and uploading/testing some example codes to an FPGA.

2 Materials and Methods

The tutorial for making these examples are in http://www.yilectronics.com/Courses/CE433/s2022/lectures/week2_dataTypes/week2_dataTypes.html


3 Results

3.1 Task 3

Vector Example Code

```
1 timescale 1ns / 1ps
2 ////////////////////////////////////////////////////
3
4 module vector_defn(num1,res1,res2,res3);
5 input[7:0] num1;
6 output res1;
7 output [3:0] res2;
8 output [0:7] res3;
9
10 assign res1=num1[2];
11 assign res2=num1[7:4];
12 assign res3=num1;
13 endmodule
14
15 module vecor_defn_tb;
16 reg[0:7] in1;
17
18 wire out1;
19 wire[3:0] out2;
20 wire[0:7] out3;
21
22 vector_defn UUT(.num1(in1),.res1(out2),.res3(out3));
23
24 initial begin
25     in1 = 8'hFA;
26     #100;
27 end
28 endmodule
29
30
```

Vector Example Sim

 

3.2 Task 4

14.1 Code

```

1 timescale 1ns / 1ps
2 //////////////////////////////////////////////////
3 module homeAlarm_top(sw,led);
4 input [4:0] sw;
5 output [0:0] led;
6 homeAlarm UUT(.a(led),.s(sw[3:0]),.m(sw[4]));
7 endmodule


```

```


1 timescale 1ns / 1ps
2 //////////////////////////////////////////////////
3 module homeAlarm(a,s,m);
4 input m;
5 input[3:0]s;
6 output a;
7 assign a=(s[0]|s[1]|s[2]|s[3])&m;
8 endmodule

```


14.1 FPGA Output 00000

 


14.1 FPGA Output 01000

 


14.1 FPGA Output 00010

 


14.1 FPGA Output 00100

 

14.1 FPGA Output 10010

 

14.1 FPGA Output 10100

 

14.2 Code


```
1 timescale 1ns/1ps
2
3 module digitalSafe_top(sw,led);
4 input [3:0] sw;
5 output [1:0] led;
6 digitalSafe UUT(.l(led),.s(sw));
7 endmodule

1 timescale 1ns/1ps
2
3 module digitalSafe(l,s);
4 input[3:0] s;
5 output [1:0] l;
6 parameter p=4'b0101;
7 assign l[0] = ~(s[0]^p[0]) & ~(s[1]^p[1]) & ~(s[2]^p[2]) & ~(s[3]^p[3]);
8 assign l[1] = ~l[0];
9 endmodule
```

14.2 FPGA Output 0000



14.2 FPGA Output 1010

 


14.3 Code


```
1 timescale 1ns/1ps
2 //////////////////////////////////////
3 module parkingCount_top(sw,led);
4 input [2:0] sw;
5 output [1:0] led;
6 parkingCount UUT(.c(led),.s(sw));
7 endmodule

1 timescale 1ns/1ps
2 //////////////////////////////////////
3 module parkingCount(c,s);
4 input [2:0] s;
5 output [1:0] c;
6 assign c[0]=(~s[0]&~s[1]&s[2])+(~s[0]&s[1]&~s[2])+(s[0]&~s[1]&~s[2])+(s[0]&s[1]&s[2]);
7 assign c[1] = (~s[0]&s[1]&s[2])+(s[0]&~s[1]&s[2])+(s[0]&s[1]&~s[2])+(s[0]&~s[1]&~s[2]);
8 endmodule
```


14.3 FPGA Output 000

 

14.3 FPGA Output 001

 

14.3 FPGA Output 011

 

14.3 FPGA Output 111



4 Discussion

All of this was fairly simple just to follow your tutorial. I now understand the difference between $[0:7]$ and $[7:0]$ and I am feeling confident in my ability. 41.1 would light up if bit 5 and any other bit was high. 14.2 would have led 2 lit if it was anything besides 1010. 14.3 could give the bit sequence of how many of the 3 switches were high regardless of the sequence.

Task 1

a)

$$\begin{array}{r} 0000\ 0000\ 0001\ 0100,0100\ 0000\ 0000\ 0000 \\ 0000\ 0000\ 1000\ 0000,1000\ 0000\ 0000\ 0000 \\ 0000\ 0000\ 0000\ 0000 + 0010\ 0000\ 0000\ 0000 \\ 1000\ 0000\ 0010\ 0110,0010\ 0000\ 0000\ 0000 \\ 1000\ 0000\ 0011\ 0010,1010\ 0000\ 0000\ 0000 \end{array}$$

b)

$$\begin{array}{r} 0\ 01100\ 0010000011 \\ 0\ 10000\ 1101000000 \\ 1\ 10010\ 1110100000 \end{array}$$

Task 2

$$\begin{array}{r} 0000\ 1111,0100 \\ + 0000\ 0100,0010 \\ \hline 0001\ 0011,0110 \\ 19,375 \end{array} \quad \begin{array}{r} 0000\ 1111,0100 \\ + 1111\ 1011,1110 \\ \hline 10000\ 1011,0010 \\ 11,125 \end{array}$$