

State and Output Equations

Calvin Reese
cjreese@fortlewis.edu

3/1/22

1 Introduction

This HW, we worked on designing and testing state and output equations.

2 Materials and Methods

The tutorial for making these examples are in http://www.yilelectronics.com/Courses/CE433/s2022/lectures/week5_sequentialCircuit/week5_sequentialCircuit.html


3 Results

3.1 Task 2

Sequence Detector Code

```
23 module sequenceDetector(y,q1,q2,x,clk,clr);
24 input x,clk,clr;
25 output reg y;
26 output reg q1=0;
27 output reg q2=0;
28
29 always @(posedge clk)
30     if(clr==1)
31         begin
32             q1<=1'b0;
33             q2<=1'b0;
34         end
35     else
36         begin
37             q1<=~(q1^q2)*x+(~x*~q1*q2);
38             q2<=(x*q1*~q2)+(~q1*q2);
39             y<=(x*q1*q2);
40         end
41 endmodule
42
43 module sequenceDetector_tb;
44 wire y,q1,q2;
45 reg x=0;
46 reg clk=0;
47 reg clr=1;
48 integer i;
49
50 sequenceDetector UUT(.y(y),.q1(q1),.q2(q2),.x(x),.clk(clk),.clr(clr));
51 initial begin
52     for(i=0;i<20;i=i+1)begin
53         clk=~clk;
54         if(i>5&i<10)begin
55             clr=0;
56             x=1;
57         end
58         else if(i==11) x=0;
59         else if(i==12) x=1;
60         else x=0;
61         #10;
62     end
63 end
64 endmodule
```

Sequence Detector Sim

 

3.2 Task 3


siso Code

```

21 module siso(clk,si,so);
22 input clk,si;
23 output so;
24 reg [3:0] q=0;
25 always @(posedge clk)
26 begin
27     q[3]<=si;
28     q[2]<=q[3];
29     q[1]<=q[2];
30     q[0]<=q[1];
31 end
32 assign so=q[0];
33 endmodule
34
35 module siso_tb;
36 reg clk;
37 reg si;
38 wire so;
39 siso U(.clk(clk),.si(si),.so(so));
40 initial begin
41     clk=0;
42     si=1;
43     #10
44     si=0;
45     #10
46     si=0;
47     #10
48     si=1;
49 end
50 always #5 clk=~clk;
51 endmodule

```

siso Sim

 


siso Code

```

55 module sipo(clk,si,po);
56 input clk,si;
57 output [3:0] po;
58 reg [3:0] tmp;
59 always @(posedge clk)
60 begin
61     tmp={si,tmp[3:1]};
62 end
63 assign po=tmp;
64 endmodule
65
66 module sipo_tb;
67 reg clk;
68 reg si;
69 wire [3:0] po;
70 sipo U(.clk(clk),.si(si),.po(po));
71 initial begin
72     clk=0;
73     si=1;
74     #10
75     si=1;
76     #10
77     si=0;
78     #10
79     si=1;
80 end
81 always #5 clk=~clk;
82 endmodule
    
```


siso Sim

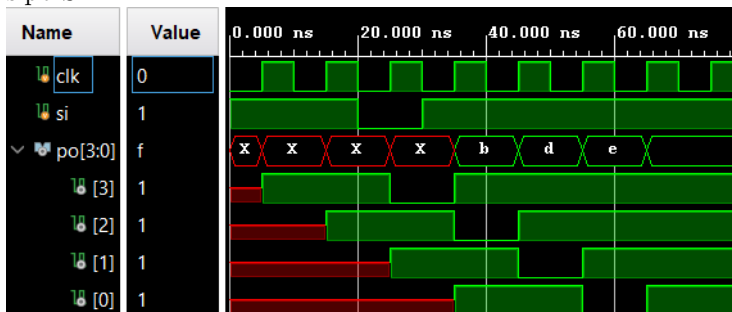

piso Code

```
86 module piso(clk,pi,load,so);
87 input clk,load;
88 input [3:0] pi;
89 output reg so;
90 reg [3:0] tmp;
91 always @(posedge clk)
92 begin
93     if(load) tmp<=pi;
94     else
95     begin
96         so<=tmp[0];
97         tmp<={1'b0,tmp[3:1]};
98     end
99 end
00 assign po=tmp;
01 endmodule
02
03 module piso_tb;
04 reg clk;
05 reg [3:0] pi=4'b1101;
06 wire so;
07 reg load;
08 piso U(.clk(clk),.pi(pi),.so(so),.load(load));
09 initial begin
10     clk=0;
11     load=1;
12     #10;
13     load=0;
14 end
15 always #5 clk=~clk;
16 endmodule
```


piso Sim

 

pip0 Code

```
120 module pip0(clk,pi,po);
121 input clk;
122 input [3:0] pi;
123 output reg [3:0] po;
124 always @(posedge clk)
125 begin
126     po=pi;
127 end
128 endmodule
129
130 module pip0_tb;
131 reg clk;
132 reg [3:0] pi=4'b1101;
133 wire [3:0] po;
134 pip0 U(.clk(clk),.pi(pi),.po(po));
135 initial begin
136     clk=0;
137     #10;
138 end
139 always #5 clk=~clk;
140 endmodule
```

pip0 Sim

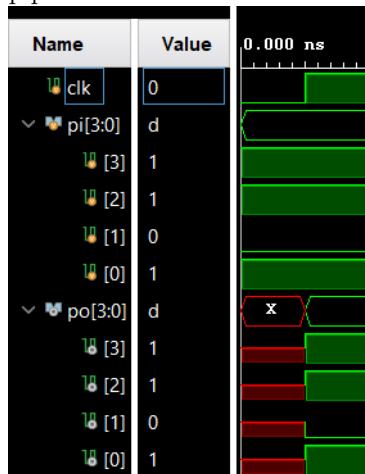


3.3 Task 4

Counter Code

```
23 module Counter(x,clk,q,y);
24 input x,clk;
25
26 output reg [1:0] q;
27 output reg y;
28
29 initial begin
30 q<=1'b00;
31 y<=1'b0;
32 end
33 always @(negedge clk)
34 if (x==1) {y,q} <= q+1'b1;
35 endmodule
36
37 module Counter_tb;
38 reg x,clk;
39 wire [1:0] q;
40 wire y;
41 Counter U(.clk(clk),.x(x),.q(q),.y(y));
42 initial begin
43 clk<=1'b0;
44 x<=1'b1;
45 end
46 always #5 clk=~clk;
47 endmodule
```

Counter Sim

 


3.4 Task 5

State Output Code

```
23 module stateOutput(clk,q,x,z);
24 input x,clk;
25 output z;
26 output reg [1:0] q;
27 assign z=q[0]&x;
28 always @(posedge clk)
29 begin
30     q[0]<=q[0]&x|q[1]&x;
31     q[1]<=~q[0]&x&~q[1];
32 end
33 endmodule
34
35 module stateOutput_tb;
36 reg x,clk;
37 wire [1:0] q;
38 wire y;
39 stateOutput U(.clk(clk),.q(q),.x(x),.z(y));
40 initial begin
41     clk<=1'b0;
42     x<=1'b1;
43     #20;
44     x<=1'b0;
45     #20;
46     x<=1'b1;
47     #20;
48     x<=1'b0;
49     #20;
50     x<=1'b1;
51     #5;
52     x<=1'b0;
53     #5;
54     x<=1'b1;
55     #5;
56     x<=1'b0;
57     #5;
58     x<=1'b1;
59 end
60 always #5 clk=~clk;
```


State Output Sim

 


4 Discussion

All of this was fairly simple just to follow your tutorial. I had no trouble figuring out the problems. The only difference might be that the siso code and output is based on 1001 instead of 1101.

Task 1

		q_1, q_2			
		00	01	11	10
x	0	0	1	0	0
	1	1	0	1	0
 
$$x \cdot (q_1 \oplus q_2) + \bar{x} \cdot \bar{q}_1 \cdot q_2$$



y

		q_1, q_2			
		00	01	11	10
x	0	0	0	0	0
	1	0	0	1	0

