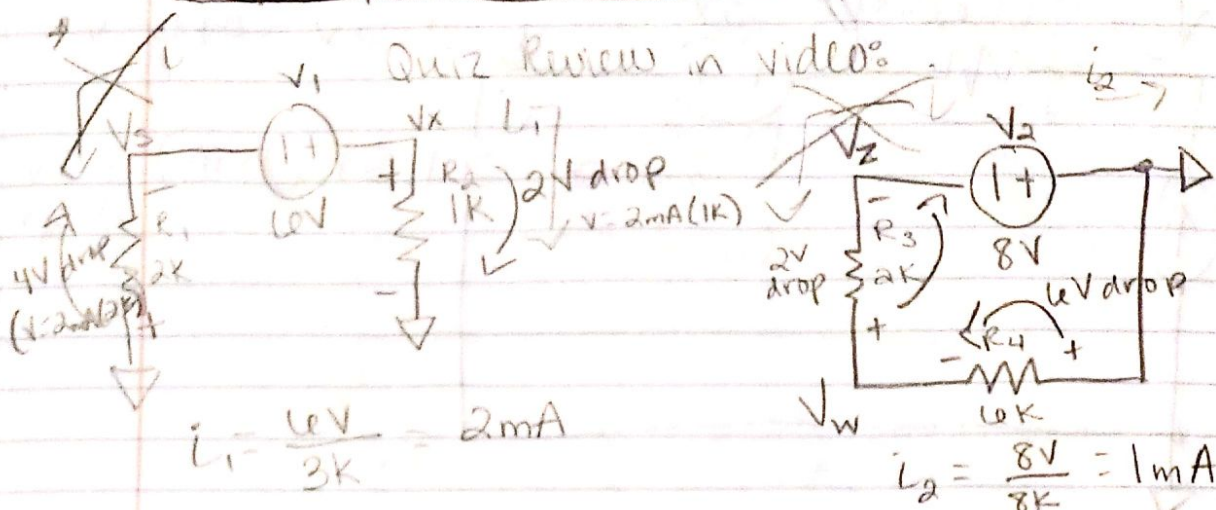


Superposition Notes




$V_S = 0 - 4 = -4$ $V_x = 2V = 0 - -2V = 2V$ $V_w = 0 - 6 = -6V$
 $V_z = 0 - 8 = -8V$

Active components will not pass current through itself

Passive components will only pass current through itself

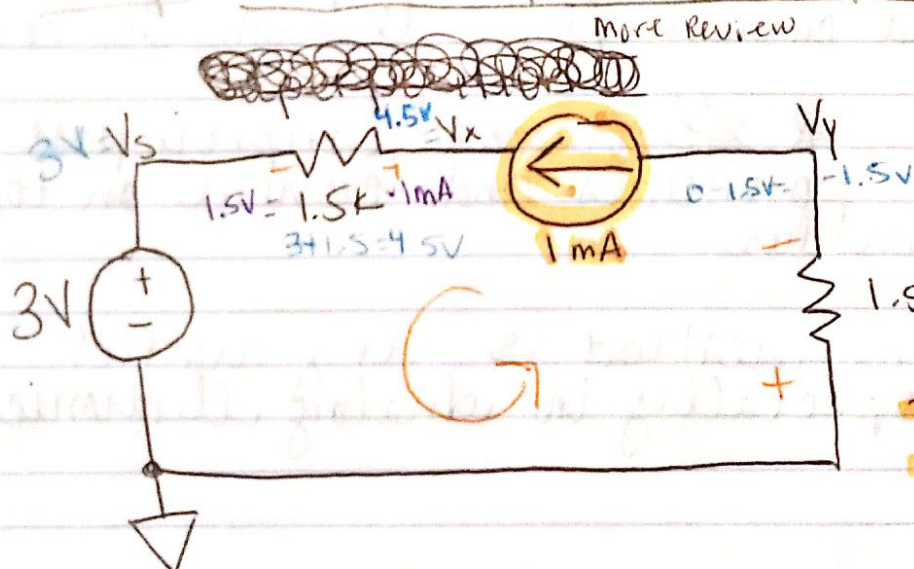
voltage of a node relies on the voltage drop over the passive component



Current sources will truncate current value in ideal situations

they also have an external power supply not shown in the diagrams!

Boost, so
 $-1.5 + 1.5 = 0$

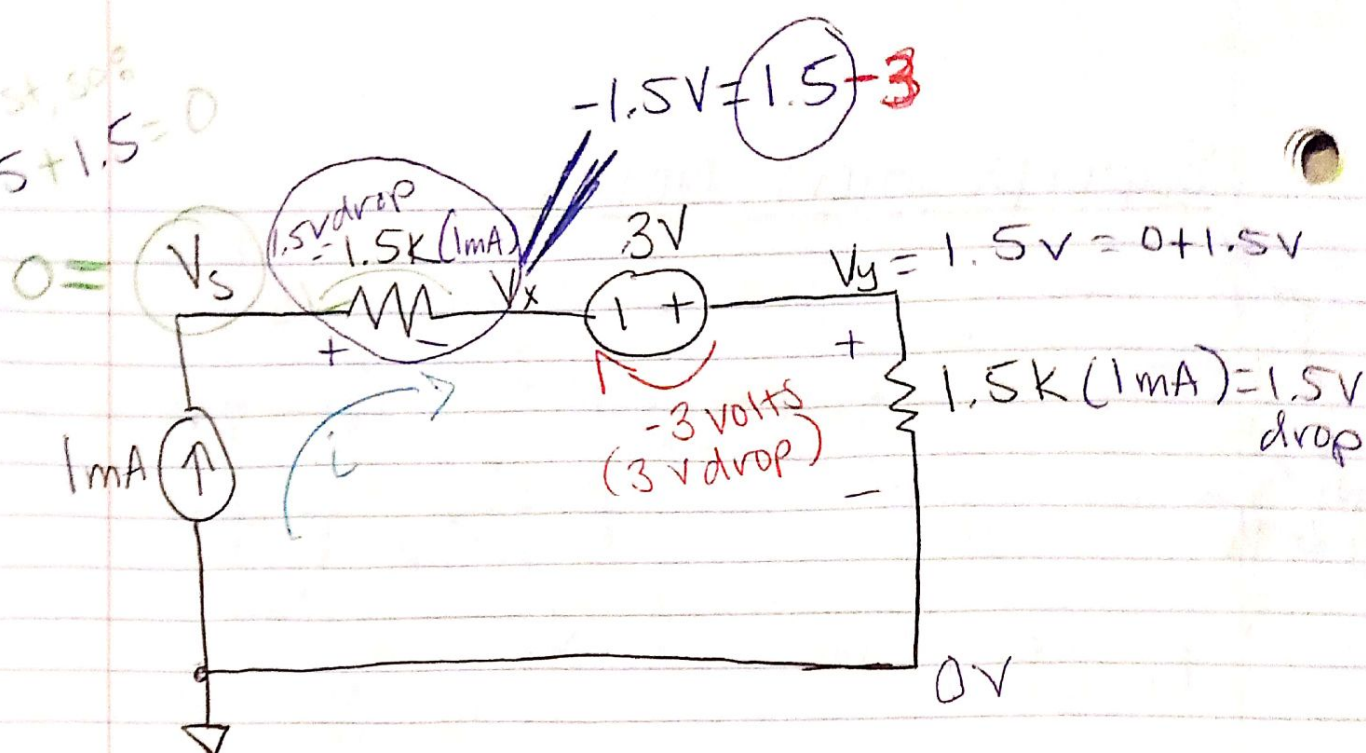


(Superposition Theorem) Superposition I

Analysis method:

- * Eliminate all but one source of power within a network at the time
- * Calculate the potential drops and current flows through the components
- * Algebraically superimpose the potentials and current on top of each other

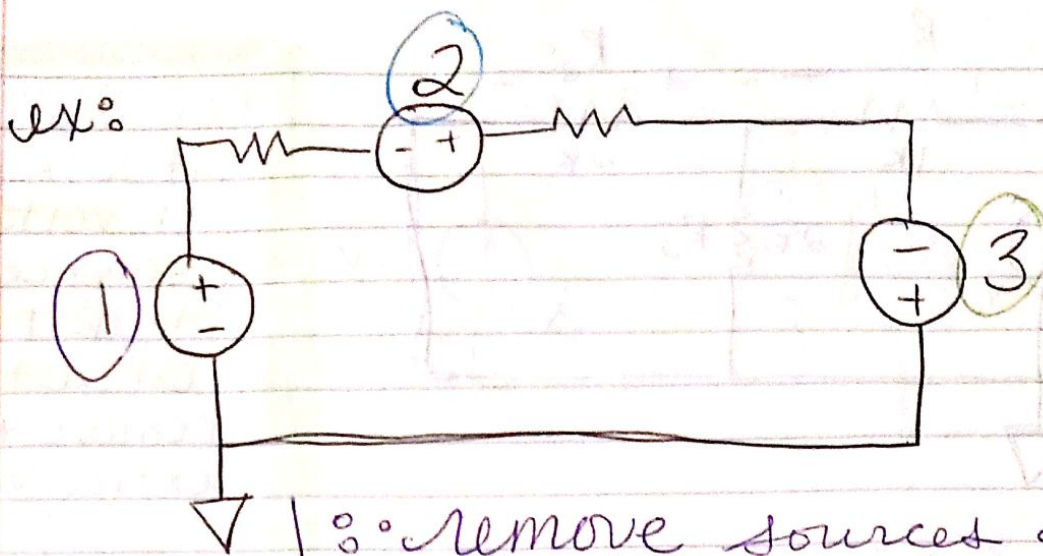This method is very useful (especially in analog electronics)



1: remove sources 2 and 3
 • calculate current & potential drops through all components

• Proceed to 2


2: remove all sources except source 2

• calculate through all components that aren't the power sources

• Proceed to 3

3: Repeat steps

• Superimpose the values

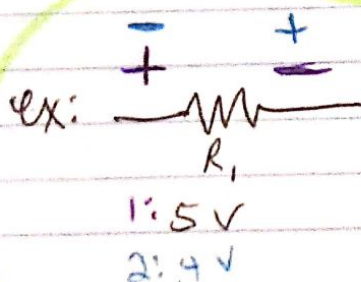


takes direction of highest potential

superimposed:



direction not changed

$$5V + 4V = 9V$$

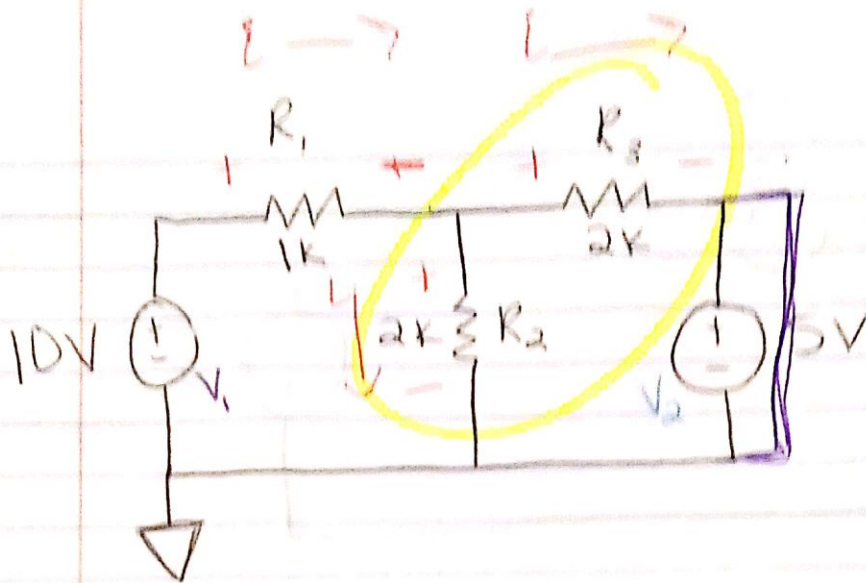

For Superpos,
if looking
at **voltage**
source,
SHORT the
circuit to
remove the
extra sources;


if looking at
current sources,
disconnect the
circuit

V_1 Only: define current direction
and polarity

in $\parallel$

$$\frac{2k \cdot 2k}{2k + 2k} = \frac{4k}{4k} = 1k$$

Circuit now:

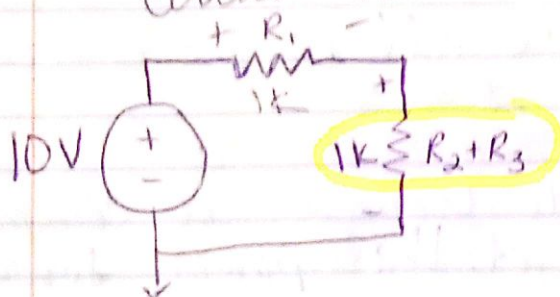

$$V_{R1} = \frac{10V}{2} = 5V$$


$$I_{R1} = \frac{V_{R1}}{R1} = \frac{5V}{1k} = 5mA$$

Voltage divider: $10V \cdot \frac{1k}{2k} = 10V \cdot \frac{1}{2}$

$V_2 = 5V$ bc $R1$ has 5V drop
 $I_{R2} = \frac{V_{R2}}{R2} = \frac{5V}{2k} = 2.5mA$ $R2$ connects to GND (0V)
 $10V - 5V - V_{R2} = 0$
 $= 5V + V_{R2} = 15V$
 $- 5V$


$R3$: $V_{R3} = 5V$ b/c in $\parallel$
 $I_{R3} = \frac{V_{R3}}{R3} = \frac{5V}{2k} = 2.5mA$

V_2 only:

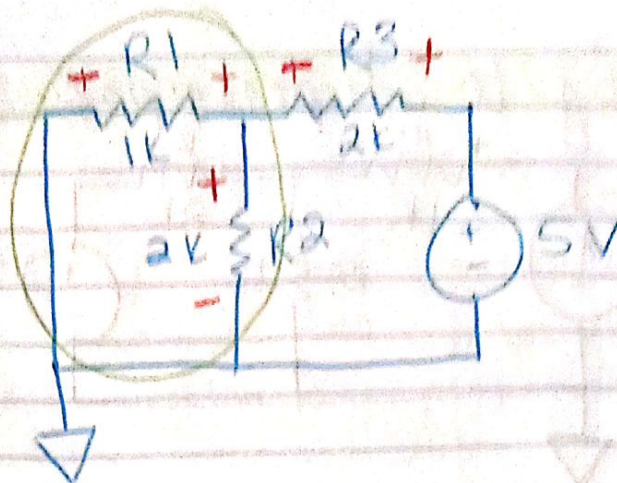

$$\frac{1k \cdot 2k}{1k + 2k} \cdot \frac{2}{3} = 0.67$$

V_{R1} :

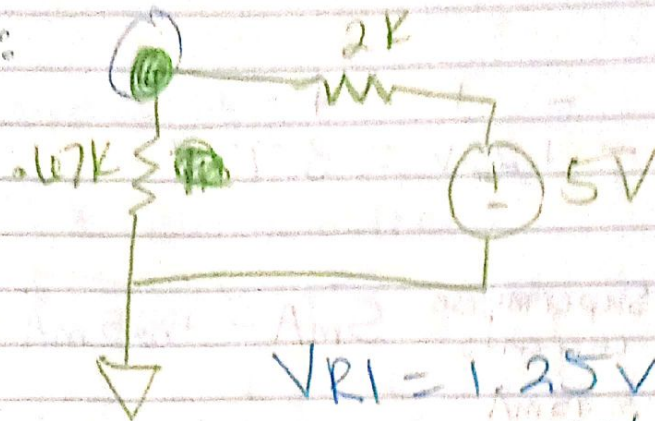

$$5V \left(\frac{0.67}{2k + 0.67k} \right)$$

$$= 5V \left(\frac{0.67}{2.67k} \right)$$


$$= 1.25V$$

$$V_{R1} = 1.25V$$

$$= 0.11.25V \quad 0$$

$$I_{R1} = \frac{V_{R1}}{R1} = \frac{1.25V}{1k} = 1.25mA$$

$$V_{R2} = 1.25V$$

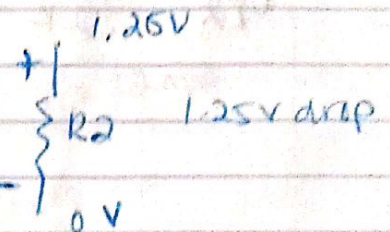


$$I_{R2} = \frac{V_{R2}}{R2} = \frac{1.25V}{2k} = 0.625mA$$

$$V_{R3} = 5V - 1.25V = 3.75V$$

$$I_{R3} = \frac{V_{R3}}{R3} = \frac{3.75V}{2k} = 1.875mA$$

Ready to Superimpose 3

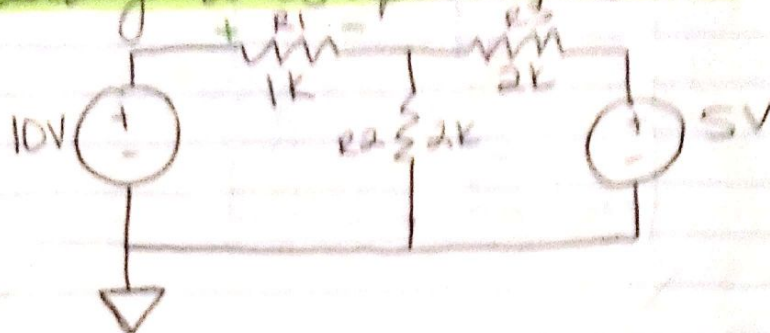

$$R1: 5V - 1.25V = 3.75V$$

$$I_{R1} = \frac{V_{R1}}{R1} \text{ or Superimpose currents } 5mA - 1.25mA = 3.75mA$$

$$\frac{3.75V}{1k} = 3.75mA$$

$$R2: 5V + 1.25V = 6.25V$$

$$I_{R2}: \frac{6.25V}{2k} = 3.125mA$$

add them
b/c same current,
direction for both.

$$R3: 5V - 3.75 = 1.25V$$

$$I_{R3}: 2.5mA - 1.875mA = 0.625mA$$


Am 2

Superposition II : review notes on back
(very helpful!)

rest of video reworks
the example in Superposition I
lecture AND verifies the
solution in LTSpice

Superposition III :

Review problem :

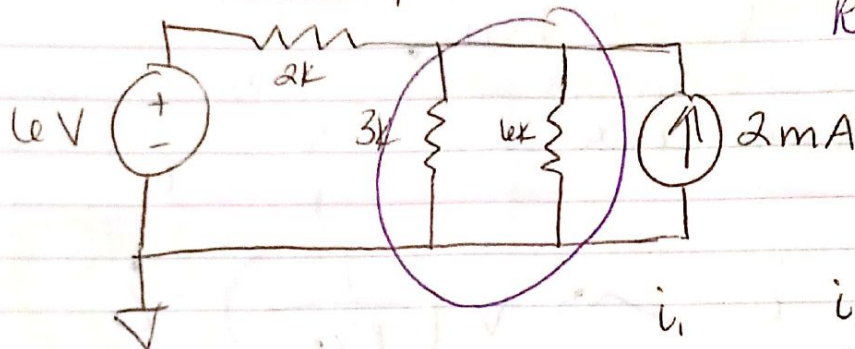


$$R_{eq} = \frac{3k \cdot 6k}{3k + 6k} = \frac{18k}{9k} = 2k$$

1: redraw:

2: label nodes

■ = 6V ▲ = 0V (GND)
● = V_x

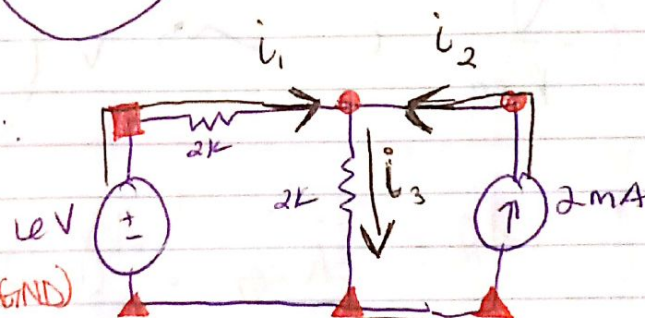

equations:

$$1) \quad i_1 + i_2 = i_3$$

$$2) \quad i_1 = \frac{V}{R} = \frac{6V - V_x}{2k} =$$

$$3) \quad i_2 = 2mA \text{ (from current source)}$$


$$4) \quad i_3 = i_1 + i_2 = \left(\frac{6V - V_x}{2k} \right) + 2mA \quad \text{OR} \quad \frac{V_x - 0}{2k}$$

Kirchoff's
Current Law

Ohm's Law

$$V \left(\frac{1}{R_{eq}} \right) = I$$

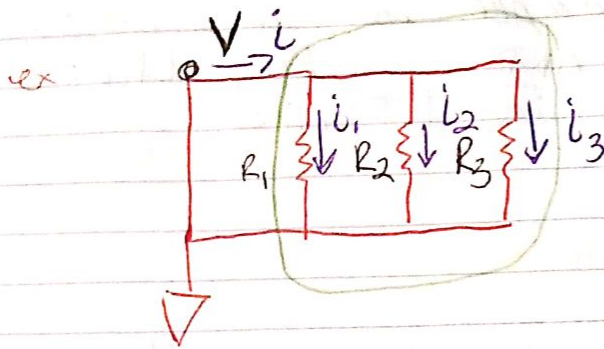Why $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$
(for $\parallel$ only)



K. Current Law says $i = i_1 + i_2 + i_3$

Ohm's Law says

$$V = i(R)$$

R_{eq} b/c V and i both are divided w/o all 3
* applying Ohm's Law

$$\frac{V}{R} = i$$

$$\frac{V}{R_{eq}} = i \rightarrow V \left(\frac{1}{R_{eq}} \right) = i$$

So... $\frac{1}{R_{eq}}$ yay!! Thank you Dr. Lee!

* R_{eq} is like treating the $\parallel$ resistors as a black box

$$i_1 = \frac{V}{R_1} \quad i_2 = \frac{V}{R_2} \quad i_3 = \frac{V}{R_3}$$

$$i = V \left(\frac{1}{R_1} \right) + V \left(\frac{1}{R_2} \right) + V \left(\frac{1}{R_3} \right)$$

Superposition ~~III~~ (continued)

$$i_1 + i_2 = i_3 - i_1$$

$$(2k) \quad 2mA = \frac{V_x}{2k} - \frac{10V - V_x}{2k}$$

$$\rightarrow 4mA = V_x - 10V - V_x$$

$$\rightarrow 4mA = -10V - 0$$

watch
your
Algebra

3: find currents 10V

$$i_1 + i_2 = i_3$$

$$i_1 = \frac{10V - V_x}{2k}$$

$$i_2 = 2mA$$

$$i_3 = \frac{V_x - 0}{2k}$$

$$\rightarrow \frac{10V - 5V}{2k} = \frac{5V}{2k} = 2.5mA$$

$$\rightarrow \frac{5V - 0V}{2k} = \frac{5V}{2k} = 2.5mA$$

$$(2k) \quad \frac{10V - V_x}{2k} + 2mA = \frac{V_x - 0}{2k}$$

$$i_1 = 2.5mA \quad i_2 = 2mA \quad i_3 = 2.5mA$$

$$10V - V_x + 4V = V_x - 0$$


$$\frac{10V}{2} = \frac{2V_x}{2}$$

$$V_x = 5V$$


Convert circuit to a simpler one,
do calculations,
then convert it back (and forth)
when needed

Next Example:

Original Circuit:

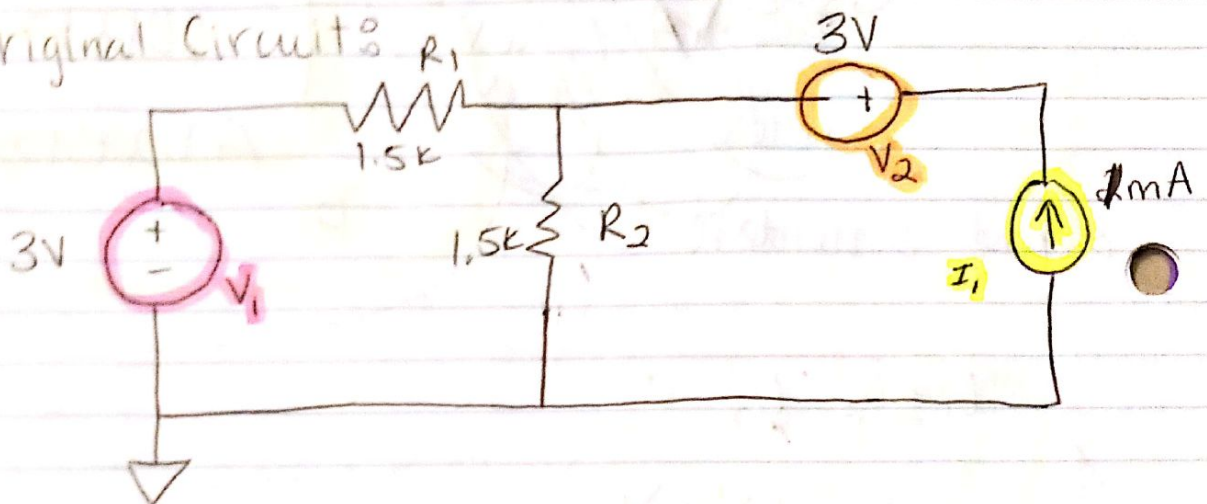

V_1 Only:

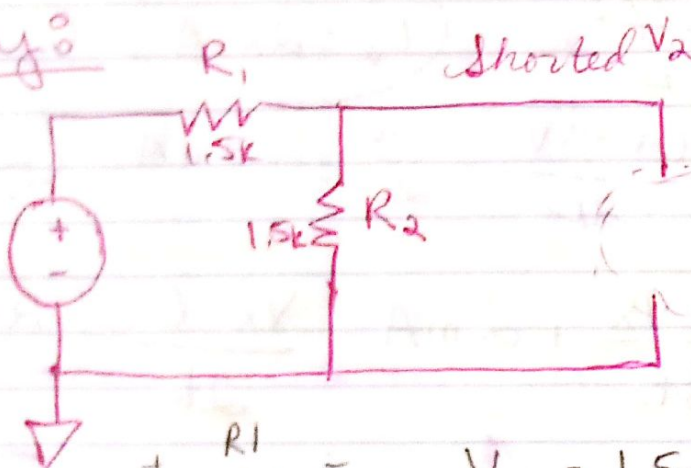

removed I_1 ,
(leave open!)

$$V_{R1} = 1.5V$$


$$I_{R1} = \frac{V_{R1}}{R_1} = \frac{1.5V}{1.5K} = 1mA$$

$$V_{R2} = 1.5V$$

$$I_{R2} = \frac{V_{R2}}{R_2} = \frac{1.5V}{1.5K} = 1mA$$

voltage divider!


V₂ Only:

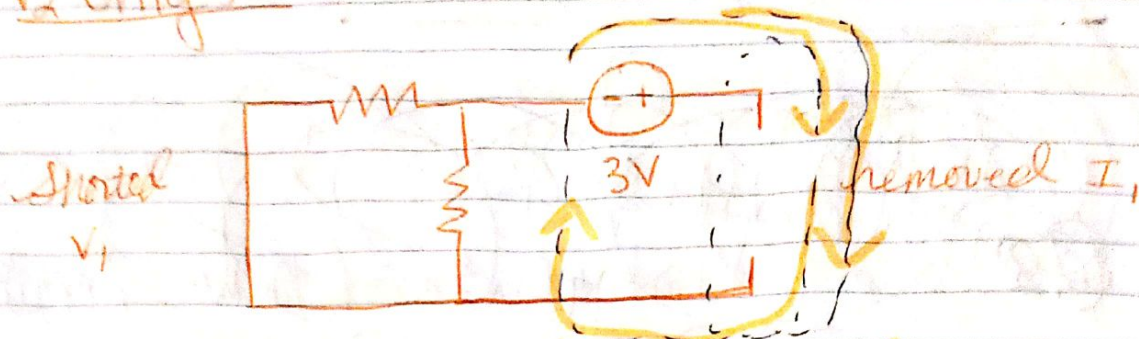


nothing happens here,
no arc will form to
complete the circuit, so all
values are 0 for this
version of the circuit

!!

I₁ only:

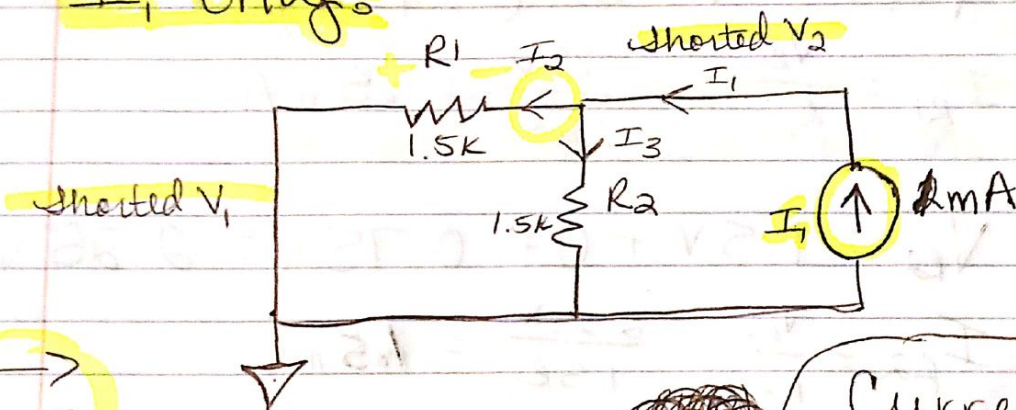

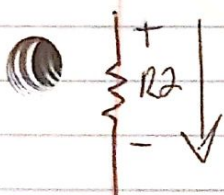opposite direction!
 $I_{R1} = -0.5 \text{ mA}$



$$V_{R2} = I_{R2} \cdot R_2 = 0.5 \text{ mA} (1.5 \text{ k}) = 0.75 \text{ V}$$

$$I_{R2} = 0.5 \text{ mA}$$

Current Divider

$$I_2 = I_1 \left(\frac{R_2}{R_1 + R_2} \right) = 1 \text{ mA} \left(\frac{1.5 \text{ k}}{1.5 \text{ k} + 1.5 \text{ k}} \right) = 1 \left(\frac{1.5 \text{ k}}{3 \text{ k}} \right) = 0.5 \text{ mA}$$

$$I_3 = I_1 \left(\frac{R_1}{R_1 + R_2} \right) = 1 \text{ mA} \left(\frac{1.5 \text{ k}}{1.5 \text{ k} + 1.5 \text{ k}} \right) = 1 \left(\frac{1.5 \text{ k}}{3 \text{ k}} \right) = 0.5 \text{ mA}$$

Now Superimpose:

~~Watts fused~~
 ~~$I_{R1} = 1\text{mA} + 5\text{mA} + 10\text{mA} = 16\text{mA}$~~

~~from superposition~~
 ~~$I_{R1} = -5\text{mA}$~~

$$\rightarrow V_{R1} = 1.5\text{V} + 0 + (-0.75\text{V}) = 0.75\text{V}$$

$$I_{R1} = \frac{V_{R1}}{R_1} = \frac{0.75\text{V}}{1.5\text{k}} = 0.5\text{mA}$$

$$V_{R2} = 1.5\text{V} + 0 + 0.75\text{V} = 2.25\text{V}$$

$$I_{R2} = \frac{V_{R2}}{R_2} = \frac{2.25\text{V}}{1.5\text{k}} = 1.5\text{mA}$$

Reason behind short vs. disconnect:

Ideally, internal resistance of a Voltage source is 0, so shorting the wires does not hinder Req

The internal resistance of a Current source is ~~finite~~ Infinite, so shorting

the wires to remove would be inconsistent to the original circuit


So always short the circuit to remove the voltage source and open the circuit to remove a current source.

SPICE Code Refresher

Circuit design:

this code →

component name	task	High node	Low node	ANDC type	quant-atts
V1	1	0	0	dc	5V
R1	1	2	2	N/D SPACE	3K
R2	2	0	0		2K

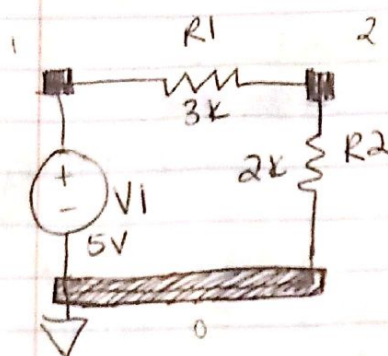

← makes this circuit

SPICE Commands

Command start stop interval (sec)

• tran 0 1 .1

transient analysis in time domain

source start stop interval (V)

• dc V1 0 10 .01

dc sweep (voltage domain)

(linear sweep by default)

sweep will ignore user set value to a power supply and simulate whatever is put into sweep command parameters


+ for time domain

dc for voltage domain


Thevenin's Equivalent

Watch before lab on
Tuesday morning!


Any linear circuit can be
simplified to:

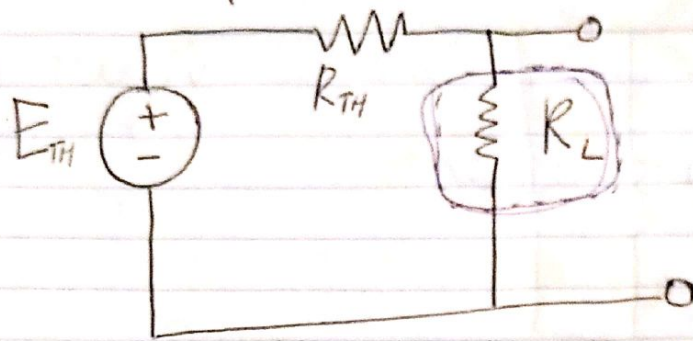

load &
can be treated
as a black
box

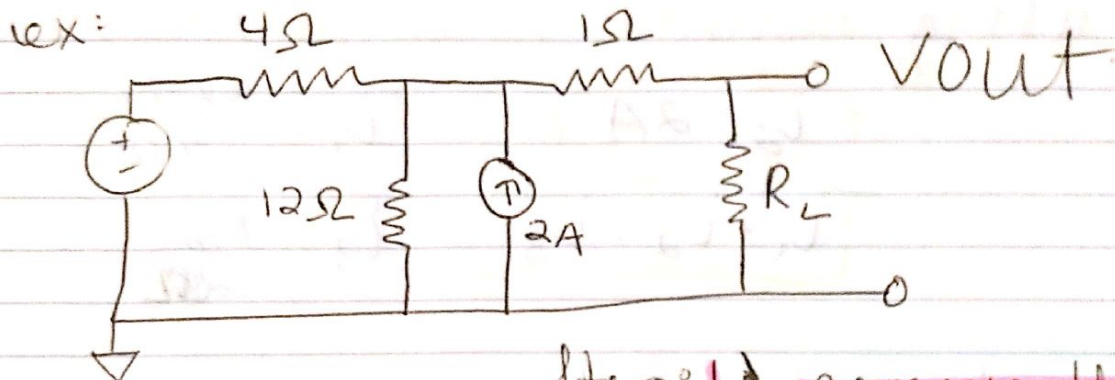

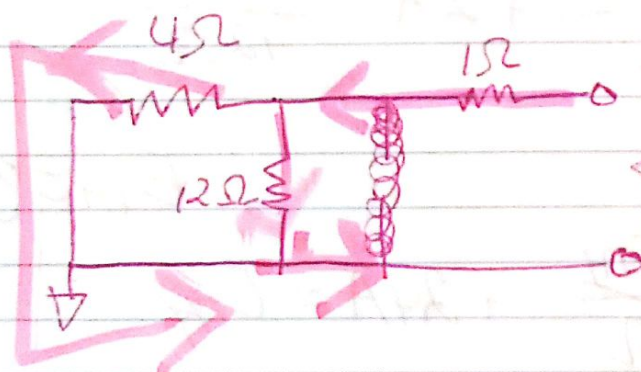
Step: 1) remove the load
2) short voltage source,
disconnect current
source



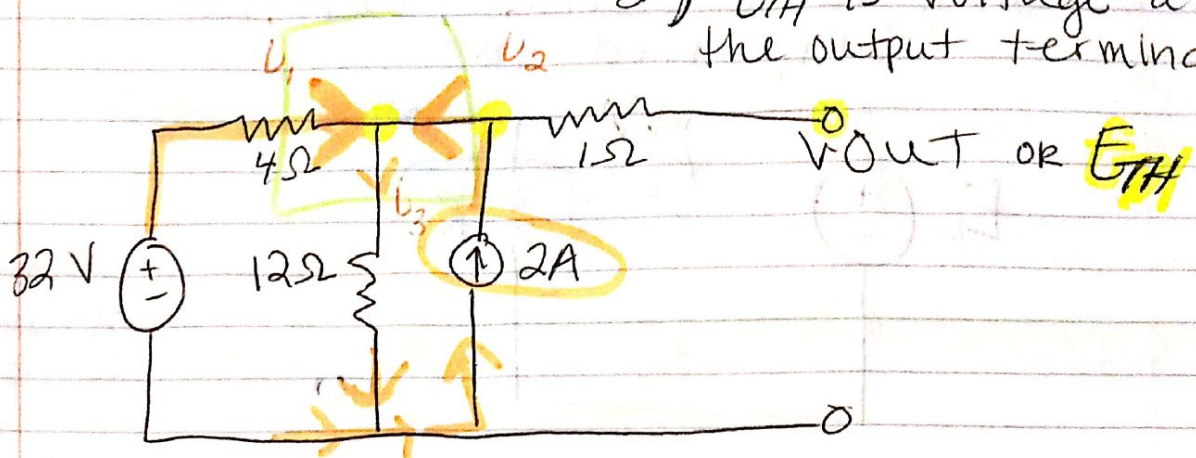3) solve for R_{TH}

$$\begin{aligned} R_{TH} &= 1\Omega + (4\Omega \parallel 12\Omega) \\ &= 1\Omega + \frac{4(12)\Omega}{(4+12)\Omega} = \frac{48\Omega}{16} + 1\Omega = 4\Omega \end{aligned}$$

E_{TH} : Step: 1) Remove R_L
 2) E_{TH} is voltage at the output terminal



using current node method:

$$I_2 = 2A$$

$$I_1 = \frac{32 - E_{TH}}{4\Omega}$$

$$I_1 + I_2 = I_3$$

$$I_3 = \frac{E_{TH}}{12\Omega}$$

so:

$$\frac{32 - E_{TH}}{4\Omega} + 2A = \frac{E_{TH}}{12\Omega}$$


$$E_{TH} = 30V$$

$$\rightarrow 90 - 3E_{TH} + 24A = E_{TH}$$

$$\rightarrow 120 - 3E_{TH} = E_{TH}$$


$$\rightarrow \frac{120}{4} = \frac{4E_{TH}}{4}$$

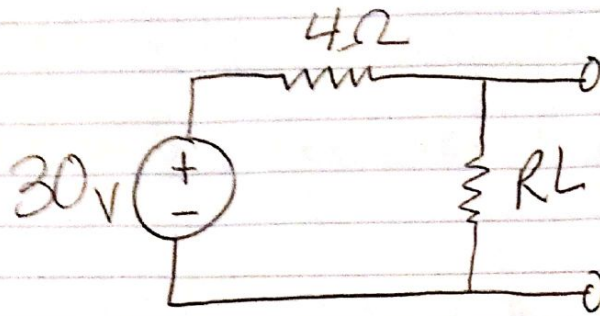So, the Thevenin's equivalent circuit for this circuit is



Quick Review

Superposition -

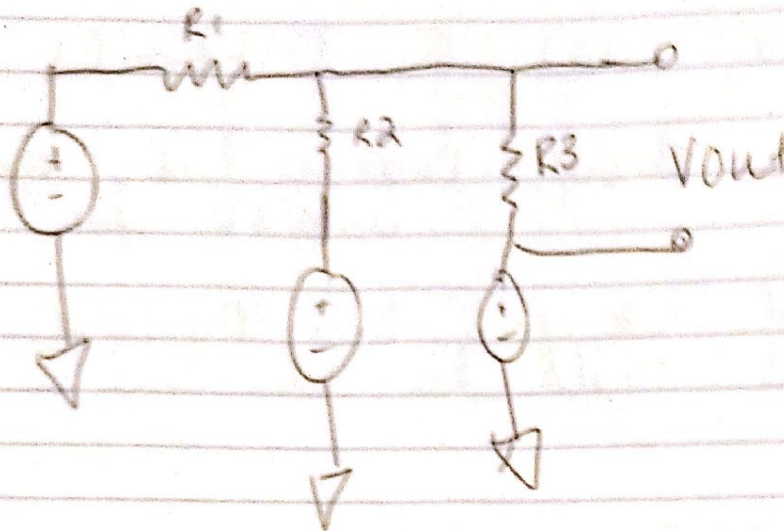


V_1 only:

$$R_2 \parallel R_3$$

now it's a voltage divider.



$$V_{out} = V_1 \left(\frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} \right)$$

V_2 only:

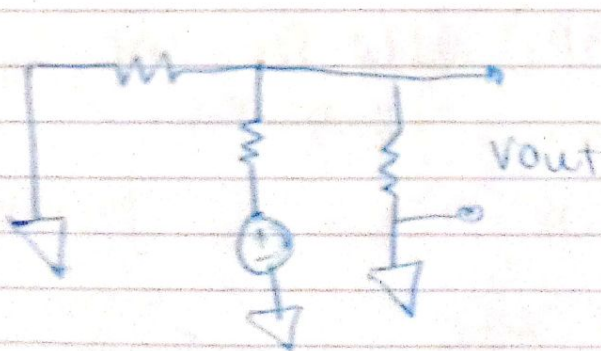

$$V_{out} = V_2 \left(\frac{R_1 \parallel R_3}{R_2 + R_1 \parallel R_3} \right)$$

V_3 only:

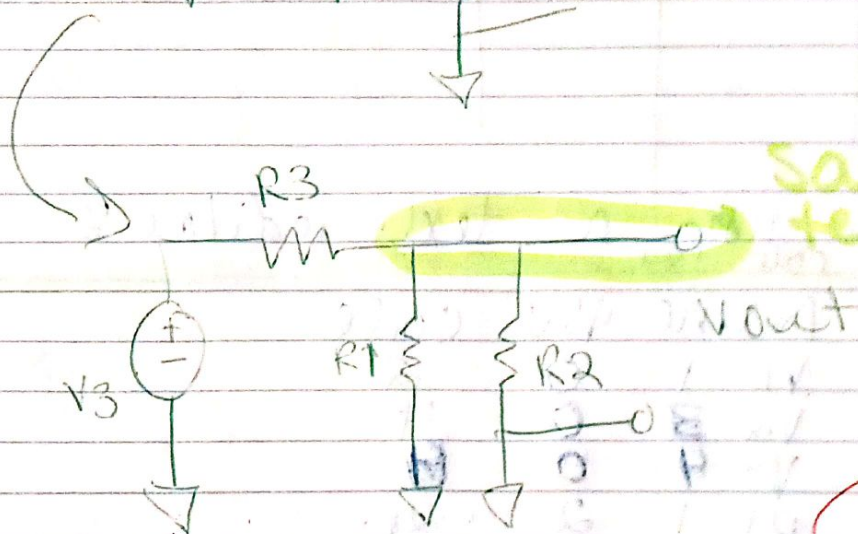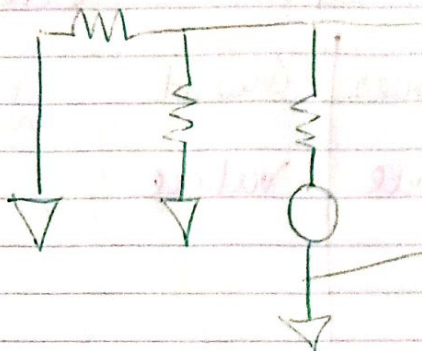

same terminal,
still V_{out}

$$V_{out} = V_3 \left(\frac{R_1 \parallel R_2}{R_3 + R_1 \parallel R_2} \right)$$

$$R_2 \parallel R_3 = \frac{R_2 R_3}{R_2 + R_3}$$

Now super impose

$$V_{out} = V_{out1} + V_{out2} + V_{out3}$$

$$V_{out} = V_1 \left(\frac{R_2 \parallel R_3}{R_1 + (R_2 \parallel R_3)} \right) + V_2 \left(\frac{R_1 \parallel R_3}{R_2 + (R_1 \parallel R_3)} \right) + V_3 \left(\frac{R_1 \parallel R_2}{R_3 + (R_1 \parallel R_2)} \right)$$

ex with values: $V_1 = 2V$ $V_2 = 4V$ $V_3 = 6V$
 $R_1 = 2K$ $R_2 = 4K$ $R_3 = 1K$

Spice Code

Component Node

V1

0

Node

0

Quant

code

Component	higher	lower	Quant
name	node	node	Value

just use a text editor?


code.txt

Name the code


V1	1	0	2
V2	3	0	4
V3	4	0	4
R1	1	2	2k
R2	2	3	4k
R3	2	4	6k

open txt file in LT Spice

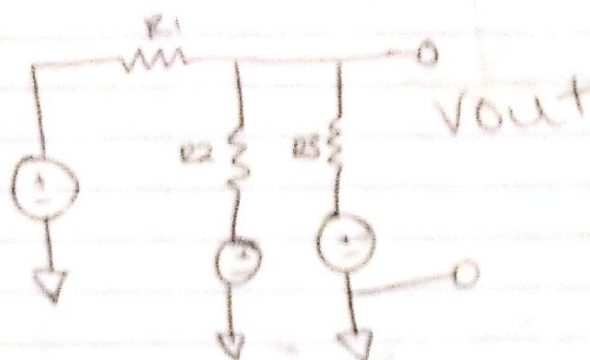Thevenin's Equivalent converting the same circuit




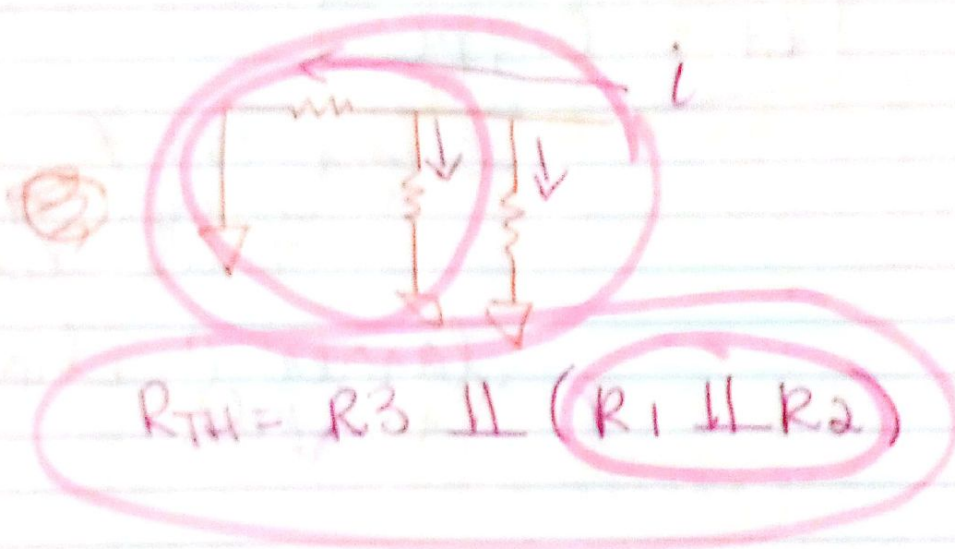1- look backwards and remove power sources



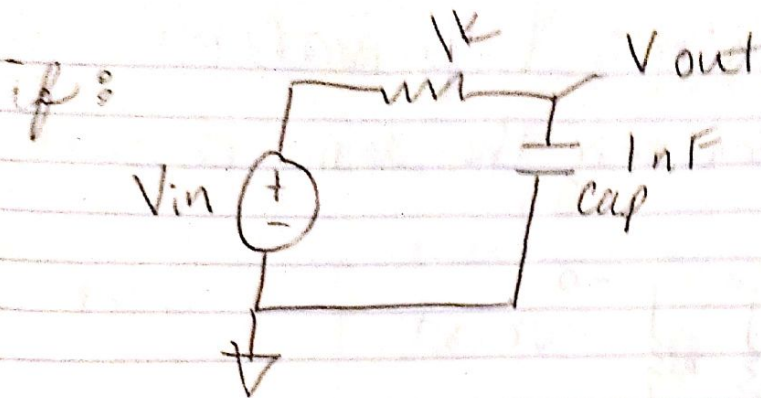0-5 pulse voltage is fine

• pulse low high time delay rising time falling time d period



$$t_d = 0.7RC$$

larger the R , the
larger the
time delay

larger C has more
to fill

$$\tau = RC \text{ (time constant)}$$

$$R \circ C = \text{time (micro seconds)}$$